


Student Name:..... Student Number:..... Section:..... Date: March. 23th, 2011..... time allowed: 1 1/4 h

Problem 1: A wrought iron bar is 30 cm long and 2 cm in diameter is bent into a circular shape as shown in Fig. 2. It is then wound with 500 turns of wire. Calculate the current required to produce a flux of 0.5 mWb in the magnetic circuit in each of the following cases:

- The structure has no air gap and $\mu_r = 4000$ (assumed constant)
- The structure has an air gap of 1 mm, and $\mu_r = 4000$ (assumed constant)
- The structure has an air gap of 1 mm, and B-H characteristics are given in the table below.

The structure has an air gap of 1 mm, and B-H characteristics are given in the table below.

H (At/m)	2500	3000	3500	4000
B (Tesla)	1.550	1.590	1.600	1.615

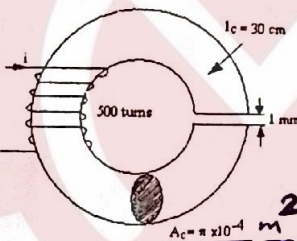

Solution:

$$400i = 94.988$$

$$\Rightarrow i = 0.2374 \text{ A} \# 1)$$

$$\phi = 0.5 \times 10^{-3} = B \cdot A = B \times \pi \times 10^{-4}$$

$$\therefore B = 1.591 \text{ T}$$

$$R_l = \frac{L_c}{\mu_0 \mu_r A} = 189977.21$$

$$R_{\text{gap}} = \frac{L_g}{\mu_0 A} = \frac{1 \times 10^{-3}}{4\pi \times 10^{-7} \times \pi \times 10^{-4}}$$

$$= 2533029.59$$

$$R_{\text{Tot}} = 2723006.8$$

$$400i = 0.5 \times 10^{-3} (2723006.8)$$

$$i = 3.403 \text{ A} \#$$

$$\phi = 0.5 \times 10^{-3} \text{ wb} = \frac{B \cdot A}{\mu_r}$$

$$N = 500 \text{ turn.}$$

$$F_i = Ni = \phi R = \frac{\phi L}{\mu_r \mu_0 \mu_r A}$$

$$400i = 0.5 \times 10^{-3} R = \frac{0.5 \times 10^{-3} (0.3)}{\mu_0 \mu_r \pi \times 10^{-4}}$$

$$400i = \frac{0.5 \times 10^{-3} (0.3)}{4\pi \times 10^{-7} \times 4000 \times \pi \times 10^{-4}}$$

$$F_i = Ni = H_g L_g + H_c L_c$$

$$\text{from } B_c = 1.59 \approx 3000 \frac{\text{At}}{\text{m}}$$

$$\therefore B_c = B_g = 1.59 \Rightarrow$$

$$H_g = \frac{B}{\mu_0} = \frac{1.59}{4\pi \times 10^{-7}}$$

$$\therefore H_g = 1265281.7 \frac{\text{At}}{\text{m}}$$

$$400i = [1265281.7 \times 10^{-3}] + [3000 \times 0.3]$$


$$400i = 2165.28$$

$$I = 5.413 \text{ A} \#$$

$$F_i = Ni = HL = H 2\pi r = \frac{LB}{\mu} = \phi R = \frac{\phi l}{\mu A}$$

Problem 2 Figure show $\phi = f(t)$ on the left and Flux ϕ versus MMF on right. Assume ~~500~~¹ Turns.

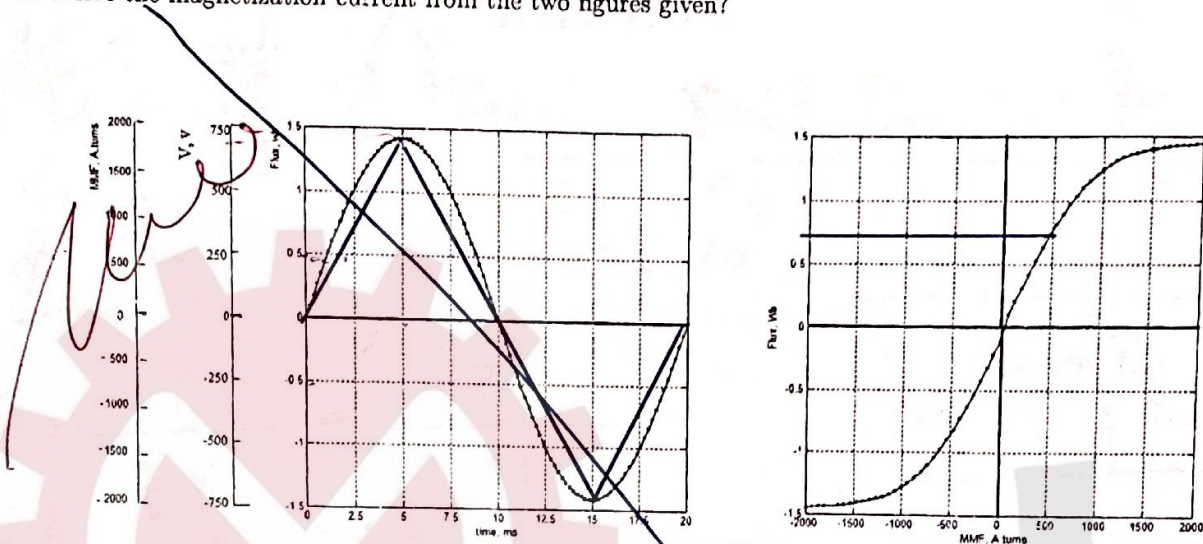1. Draw the $v(t)$ on the appropriate place.
2. Drive the magnetization current from the two figures given?



$$I = N \frac{d\phi}{dt}$$


$$= 1 \frac{1.45 - 0}{5 - 0} = 0.29$$

اللجنة الأكاديمية في قسم هندسة الميكانيك - الجامعة الأردنية

$$R + jX \quad V_s / I_s \cos^{-1} \text{p.f.}$$

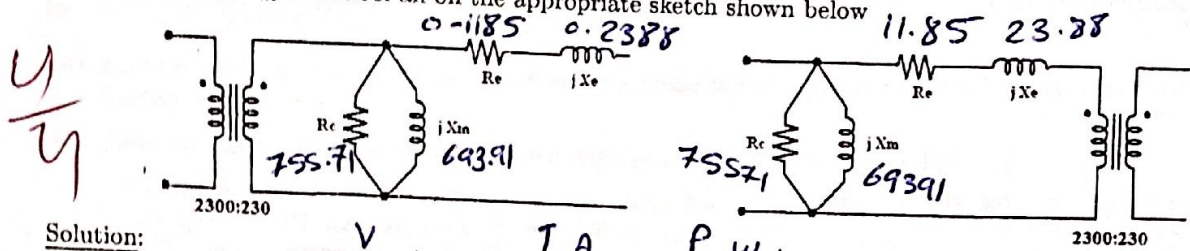Problem 3 The following data were obtained from tests carried out on a 10 kVA, 2300/230 V 50 Hz distribution transformer: Open circuit test: 230 V, 0.45 A, 70 W. Short circuit test: 120 V, 4.5 A, 240 W.

Find R_e , X_e , R_c , X_m and label all on the appropriate sketch shown below



Solution:

for open circuit:- $V = 230 \text{ V}$, $I = 0.45 \text{ A}$, $P = 70 \text{ W}$.

$$\text{p.f.} = \frac{P_{oc}}{I_{oc} V_{oc}} = \frac{70}{0.45(230)} = 0.6763$$

$$\begin{aligned} \therefore T &= \frac{1}{R_c} + \frac{1}{jX_m} J = \frac{I_0}{V_0} \angle -\cos^{-1} \text{p.f.} \\ &= \frac{0.45}{230} \angle -\cos^{-1} 0.6763 \\ &= 1.32325 \times 10^{-3} - j1.4411 \times 10^{-3} \text{ J} \end{aligned}$$

$$\therefore \frac{1}{R_c} = 1.32325 \times 10^{-3} \Rightarrow R_c = 755.71 \Omega \quad \#$$

$$\frac{1}{jX_m} J = -j1.4411 \times 10^{-3} \Rightarrow X_m = 693.91 \Omega \quad \#$$

for short circuit:-

$$R_c' = R_c \left(\frac{N_1}{N_2} \right)^2 = 755.71 \left(\frac{2300}{230} \right)^2 = 75571 \Omega \quad \#$$

$$X_m' = X_m (10)^2 = 69391 \Omega \quad \#$$

for short circuit:- $\text{p.f.} = \frac{P_{sc}}{I_{sc} V_{sc}} = \frac{240}{120(4.5)} = 0.445$

$$\therefore Z_{eq} = R_{eq} + jX_{eq} = \frac{V_{sc}}{I_{sc}} \angle \cos^{-1} \text{p.f.} = \frac{120}{4.5} \angle \cos^{-1} 0.445$$

$$\therefore R_{eq} = 11.85 \Omega, X_{eq} = 23.88 \Omega \quad \#$$

Problem 4: A single-phase, 3 kVA, 220/110 V, 50 Hz transformer has a HV winding resistance of 0.3Ω , a LV winding resistance of 0.06Ω , a HV leakage reactance of 0.8Ω and a LV leakage reactance of 0.2Ω . The core loss at rated voltage is 45 W. The copper loss at rated load is 100 W. Neglect the exciting current of the transformer and use the *per unit* circuit to:

- Find the per-unit voltage regulation when the transformer is supplying full load at 110 V and 0.9 lagging power factor.
- Calculate the transformer efficiency when delivers 2.7 kW at 0.90 lagging PF.
- Find the all-day efficiency for the following loading: 3.5 kVA , 0.95 PF for 3 H; 3.0 kVA , 0.9 PF for 8 H; 2.4 kVA , 0.8 PF for 4 H; 1.0 kVA , 0.95 PF for 9 H.

Solution:

$$2) \eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss}} = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + P_{oc} + I_2^2 R_{eq}^2}$$

$$I_{f2} = \frac{3000}{110} = 27.27$$

$$\eta = \frac{(110)(0.9)(27.27)}{(27.27)(110)(0.9) + 2700 + 100} = 35.71\%$$

$$\eta = \frac{23700}{68000} = 34.85\%$$

$$\therefore P_{oc} = P_c = 45\text{ W}$$

$$2.7/3 = 90\% \text{ of full load } \Rightarrow P_{cu} = \frac{I_2^2 R_{eq}}{100} (0.9)^2 = 81$$

$$P_{core} = (1.16^2 \times 3 \times 10^{-3} \times 8) + (0.8^2 \times 3 \times 10^{-3} \times 4) + (0.33^2 \times 3 \times 10^{-3} \times 9) = 0.0467 \text{ kWh}$$

$$3) \eta_{AD} = \frac{\sum P_{out}}{\sum P_{in}}$$

$$\text{percent} = 116\%, 100\%, 80\%, 33\%$$

$$\sum_{24} = (3 \times 0.95 \times 3 \times 1.16) + (3 \times 0.9 \times 8 \times 1) + (2.4 \times 0.8 \times 4 \times 0.8) + (1 \times 0.95 \times 9)$$

$$= (3.5 \times 0.95 \times 3) + (3 \times 0.9 \times 8) + (2.4 \times 0.8 \times 4) + (1 \times 0.95 \times 9)$$

$$= 9.475 + 21.6 + 7.68 + 8.55 = 47.805$$

$$= (1.16^2 \times 3 \times 4) + ($$

$$P_{cu} = \frac{100}{1000} \times 24 = 2.4 \text{ kWh}$$

$$\eta_{day} = \frac{47.805}{47.805 + 2.4 + 0.0467} = 95.13\%$$

$$V_s > V_L \rightarrow$$


Problem 5: A 10 kVA 480/100 V conventional (isolated winding) transformer is to be as auto transformer. The source voltage is 480 V, the load operates at 380 V.

- Sketch the transformer connection that will do the required job.
- Find the kilo-volt-ampere rating of the transformer in the configuration
- Find the maximum primary and secondary currents under these configuration

$$S = 10 \text{ kVA}, V_{\text{source}} = 480 \text{ V}, V_{\text{load}} = 380 \text{ V}.$$

$$480/100$$

4
4

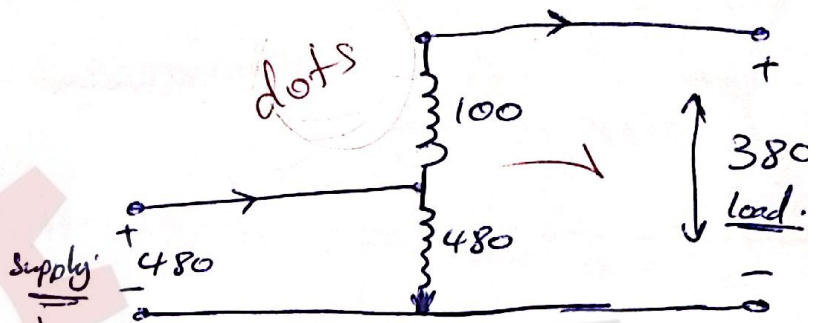

$$S_{\text{auto}} = S \left(\frac{380}{100} \right) = 10 \left(\frac{380}{100} \right) = 38 \text{ kVA}.$$

$$I_{\text{max @ 480}} = \frac{38000}{480} = 79.1667 \text{ A}$$

$$I_{\text{max @ 380}} = \frac{38000}{380} = 100 \text{ A}$$

$$I_R = \frac{10000}{480} = 20.83 \text{ A}$$

$$= \frac{10000}{100} = 100 \text{ A}$$