

**University of Jordan
School of Engineering
Electrical Engineering Department**

**EE 204
Electrical Engineering Lab**

EXPERIMENT 1 REPORT & PRE Lab

**INTRODUCTION OF
MEASUREMENT DEVICES**

Section # _____ Group #

	Student Name	ID
1.		
2.		
3.		
4.		

PROCEDURE A - VOLTAGE AND CURRENT DIVISION

1. Use theoretical analysis to determine the expected current I . What equation did you use?

2. Using the theoretical current, what is the voltage divider equation for the voltage across R_1 ?

Table 1

<i>I point a (mA)</i>	<i>I point b (mA)</i>	<i>I point c (mA)</i>

Table 2

V_{ab} (V)	V_{bc} (V)	V_{ce} (V)	$V_{ab}+V_{bc}+V_{ce}$

3. Remove R_2 from the circuit, connect it in any place on the breadboard and use the DMM to measure its resistance value.

4. Use theoretical analysis to determine the expected currents I_1 , I_2 , I_3 and I . What is the current divider equation for the current in resistor R_1 ?

5. Use DMM to measure the currents I_1 , I_2 , I_3 and I . Record these values in Table 3.

Table 3

I_1 (mA)	I_2 (mA)	I_3 (mA)	$I_1+I_2+I_3$	I (mA)