

**University of Jordan
School of Engineering
Electrical Engineering Department**

**EE 204
Electrical Engineering Lab**

**EXPERIMENT 2 REPORT & PRE-LAB
DC CIRCUITS**

Section # _____ Group # _____

Student Name ID

- 1.
- 2.
- 3.
- 4.

EXPERIMENT 2

DC CIRCUITS

PROCEDURE A – CAPACITORS AND INDUCTORS IN DC CIRCUITS

3. What is the current divider equation for the current in resistor R_1 ?

.....

Table 1

	I_1 (mA)	I_2 (mA)	I_3 (mA)	$I_1 + I_2 + I_3$	I (mA)	V_{ae} (V)
Theory						
Measured						

5. What happens to inductors in DC circuits?

.....

6. What happens to capacitors in DC circuits?

.....

PROCEDURE B – NODAL AND MESH ANALYSIS

3. What was the nodal equation you wrote at node b ?

.....

Table 2

	V_{ae} (V)	V_{be} (V)	V_{ce} (V)	V_{de} (V)
Theory				
Measured				
Deviation (%)				

5. What was the mesh equation you wrote for the *left* mesh?

.....

Table 3

	I_1 (mA)	I_2 (mA)	I_3 (mA)	I_4 (mA)
Theory				
Measured				
Deviation (%)				

CONCLUSIONS

Summarize in clear but concise format what you learned from this experiment:

** End **