

University of Jordan
Electrical Engineering Department
Electrical Engineering (EE 203)/ 1st Exam
(Form b)

20

Student Name (Arabic) المستشفى الكائن في الجامعة الأردنية

Student #: 01178411

Instructor: Eng. Reem Al-Debs

Section:


1
8.00 - 9.10

2
10.20 - 11.30

	a	b	c	d	e
1			X		
2				X	
3		X			
4	X				
5			X		
6				X	
7		X			
8				X	
9		X			
10				X	
11					X
12					X
13		X			
14			X		
15			X		
16		X			
17			X		
18			X		
19					X
20					X

the most correct answer (one mark each)

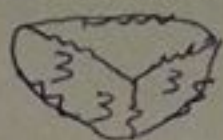1. Three 3Ω resistors are connected as Y connection. The equivalent delta connection consists of:
- three 3Ω resistors
 - three 6Ω resistors
 - three 9Ω resistors
 - three 1Ω resistors
 - 3Ω , 6Ω and 9Ω resistors



$$\frac{3 \times 3 + 3 \times 3 + 3 \times 3}{3}$$

2. If the voltage across a resistor is $0.3V$, and $R=200\Omega$, the current flowing through the resistor is:

$$I = \frac{V}{R}$$



- $60A$
- $60mA$
- $666.7A$
- $1.5mA$
- $1.5\mu A$

$$2 = I \times 0.5$$

$$I = 4$$

3. For the circuit shown, use the current division law to find I_1 if $I_3=8A$:

- $8A$
- $14A$
- $2A$
- $1.75A$
- $32A$

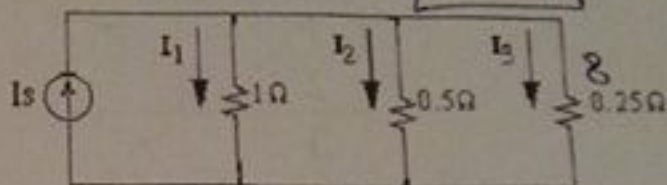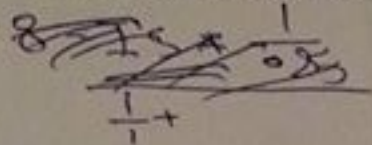


4. Power absorbed by any resistor is considered:

- positive
- zero
- negative
- could be positive or negative
- None of the above

5. The equivalent resistance R_{eq} (in ohms) at terminals a and b in the following circuit is:

- 15Ω
- 18Ω
- 5Ω
- 60Ω
- 0Ω

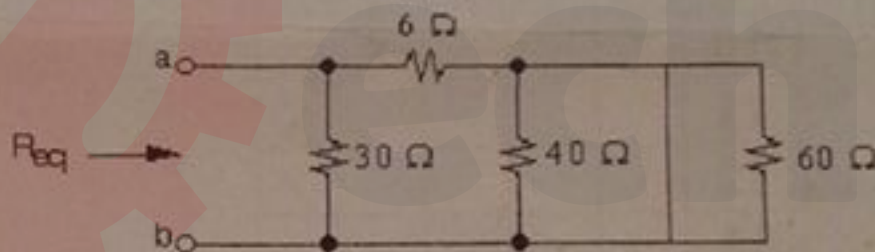

6. V_{ab} in the following circuit equals:


- $15V$
- $6V$
- $9V$
- $3V$
- $0V$

$$7 \times 15 = 15 \times 1$$

$$7 \times 15 = 15 \times 1$$


$$6 \times 1 = 5 \times 1 = 1$$

$$25 \times 1 = 25$$

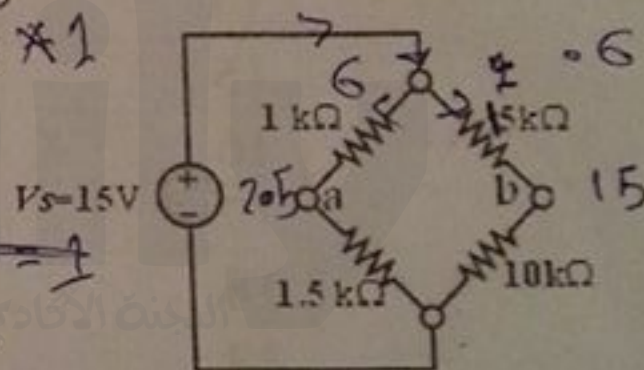


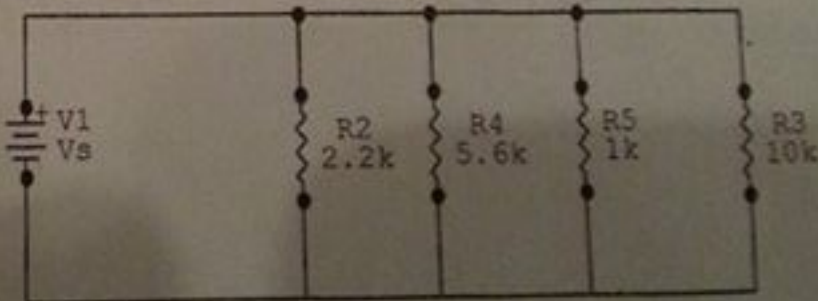7. For the following circuit, if $V_s \neq 0$:

- the maximum current pass through $5.6k\Omega$
- the maximum current pass through $1k\Omega$
- the maximum current pass through $10k\Omega$
- the maximum current pass through $2.2k\Omega$
- V_s is unknown, so we can not know



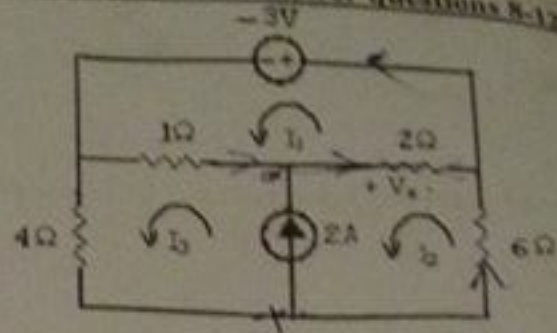• Use Mesh analysis in the circuit shown in the following figure to answer questions 8-12



8. Which of the following is correct equation:

- a. $I_2 = -2$
- b. $I_3 = 2$
- c. $I_2 - I_3 = 2$
- d. $I_3 - I_2 = 2$**
- e. $I_2 + I_3 = 2$

9. The equation due to the first mesh is:

- a. $I_1 = 3$
- b. $3I_1 - 2I_2 - I_3 = 3$**
- c. $3I_1 + 2I_2 - I_3 = -3$
- d. $3I_1 = -3$
- e. $3I_1 = 3$

10. The equation due to the super mesh is:

- a. $8I_2 + 5I_3 = 0$
- b. $8I_2 + 5I_3 = 2$
- c. $-2I_1 + 8I_2 + 5I_3 = 3$
- d. $-3I_1 + 8I_2 + 5I_3 = 0$**
- e. $-6I_2 + 4I_3 = 3$

11. V_x is:

- a. $V_x = 2I_2$
- b. $V_x = 2I_1$
- c. $V_x = 2(I_2 + I_1)$
- d. $V_x = 2(I_2 - I_1)$
- e. $V_x = 2(I_1 - I_2)$**


12. The generated power by the (2A) source equals:

- a. 20 W
- b. 32 W
- c. 13.2 W
- d. 11.88 W
- e. None of the above**

• Use Nodal analysis for the circuit shown in the following figure to answer questions (13-16)

13. Nodal equation at node 1 is:

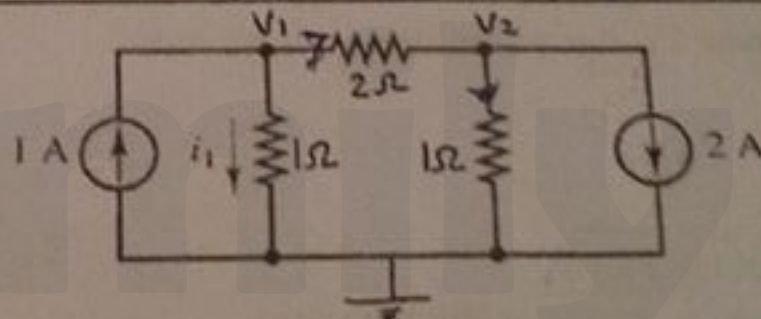- a. $V_1 - V_2 = 3$
- b. $3V_1 - V_2 = 2$**
- c. $V_1 - 3V_2 = 3$
- d. $V_1 - 2V_2 = 2$
- e. None of the above



$$1 = \frac{V_1 - 0}{1} + \frac{V_1 - V_2}{2} \quad 2 = 2V_1 + V_2$$

14. Nodal equation at node 2 is:

- a. $-V_1 + V_2 = 3$
- b. $V_1 - 3V_2 = 3$
- c. $V_1 - 3V_2 = 4$**
- d. $V_1 - V_2 = 3$
- e. $V_1 + 3V_2 = 4$

$$2 + V_2 = \frac{V_1 - V_2}{2} \quad 3V_1 - V_2 = 2$$

$$4 + 2V_2 = V_1 - V_2 \quad -3V_1 + 9V_2 = -2$$

$$4 = V_1 - 3V_2 \quad +8V_2 = -\frac{10}{3}$$

$$V_2 = -\frac{10}{24}$$

$$3V_1 + \frac{10}{8} = 2$$


$$V = 0.25$$

15. The current I_x is:
- 0.5 A
 - 0 A
 - 0.25 A
 - 2 A
 - 4 A

16. The dissipated (absorbed) power by 2A source equals:

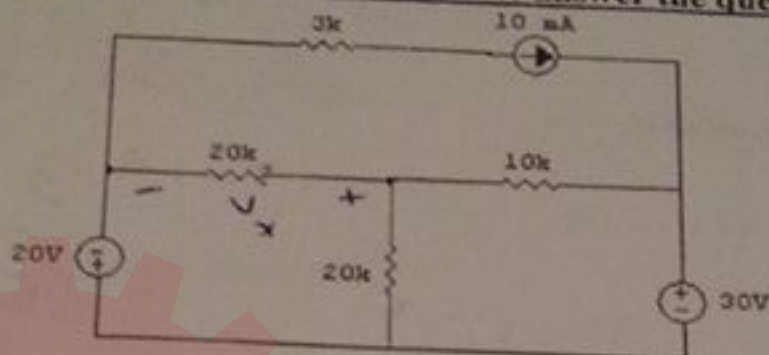- 2.5 W
- 2.5 W
- 1.25 W
- 1.25 W
- None of the above

• Use superposition Method in the following circuit to answer the questions (17-20)



17. find the voltage V_x due to the 20V source only:

- 20 V
- 10 V
- 15 V
- 12 V
- None of the above

18. find the voltage V_x due to the 30V source only:

- 20 V
- 10 V
- 15 V
- 12 V
- None of the above

19. find the voltage V_x due to the 10mA source only:

- 10 V
- 5 V
- 20 V
- 100 V
- None of the above

20. find the voltage V_x in the original circuit:

- 35
- 130
- 22
- 70
- None of the above

