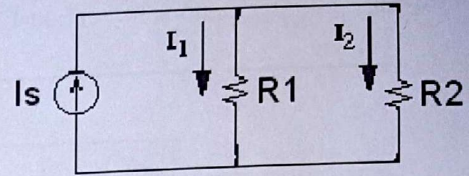


Q1) (20 marks) Choose the correct answer and fill it in the answer sheet

1. For the circuit shown, the current division formula to evaluate I_2 :

- a. $I_2 = I_s \frac{R_1}{R_1 + R_2}$
- b. $I_2 = I_s \frac{R_2}{R_1 + R_2}$
- c. $I_2 = I_s \frac{R_1 \times R_2}{R_1 + R_2}$
- d. $I_2 = I_s \frac{R_1 + R_2}{R_1 \times R_2}$
- e. $I_2 = \frac{R_2}{R_1 + R_2}$


$$I_2 = I_s \times \frac{R_1}{R_1 + R_2}$$



2. For the circuit shown, the power absorbed/delivered in component A is:

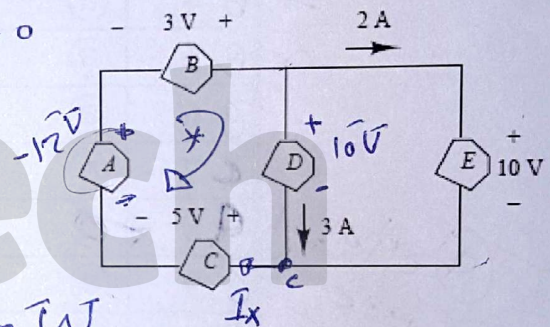- a. 60W (delivered)
- b. 60W (absorbed)
- c. 30W (delivered)
- d. 30W (absorbed)
- e. None of the above

$$\begin{aligned} \sum V @ * &= 0 \\ -3V + 10V + 5V + V_A &= 0 \\ V_A &= 3 - 10 - 5 \\ V_A &= -12V \end{aligned}$$




@ node C

$$\begin{aligned} I_{in} &= I_{out} \\ 2A + 3A &= I_x \\ I_x &= 5A \end{aligned}$$

$$\begin{aligned} P_A &= (I)(V) \\ &= -(5A)(-12V) = 60W \end{aligned}$$

3. For the circuit shown; if $I_0 = -2A$, $I_1 = -4A$, $I_s = 8A$, and $V_s = 12V$, then the current I_3 is

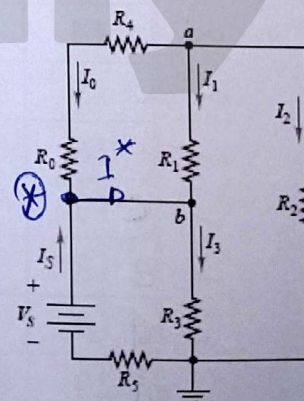- a. 4A
- b. -2A
- c. 2A
- d. -4A
- e. None of the above



@ node *

$$\begin{aligned} \sum I_{in} &= \sum I_{out} \\ -2 + 8 &= I^* \\ I^* &= 6A \end{aligned}$$


@ node B

$$\begin{aligned} \sum I_{in} &= \sum I_{out} \\ 6 - 4 &= I_3 \\ 6 - 4 &= 2A \end{aligned}$$

For the circuit shown, answer the questions (4-5)

4. If node a is the reference node, then the nodal voltage at d is:

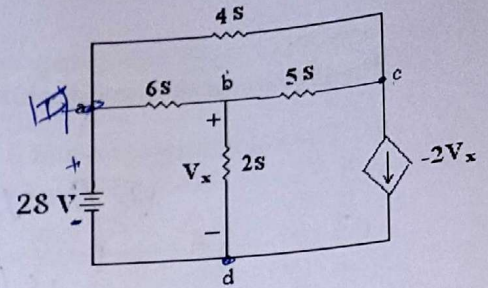- a. 0V
- ☒ b. -28V
- c. 28V
- d. -2V
- e. None of the above



5. If node d is the reference node, then the nodal equation at node c is:

a. $\frac{v_b}{9} - \frac{v_c}{5} = 0$

b. $\frac{v_b}{9} + \frac{v_c}{5} = 0$

c. $-7v_b + 9v_c = 112$

d. $-7v_b - 9v_c = 112$

☒ e. None of the above

$$\frac{V_c - 28}{\frac{1}{4}} + \frac{V_c - V_b}{\frac{1}{5}} - 2\left(\frac{V_b - 0}{\frac{1}{2}}\right) = 0$$

$$\frac{V_c - 28}{1/4} + \frac{V_c - V_b}{1/5} - \frac{2V_b}{1/2} = 0$$


$$4V_c - 112 + 5V_c - 5V_b - 4V_b = 0$$

$$4V_c + 5V_c - 5V_b - 4V_b = 112$$

$$9V_c - 9V_b = 112$$

6. For the circuit shown, the equivalent resistance (R_{eq}) is:

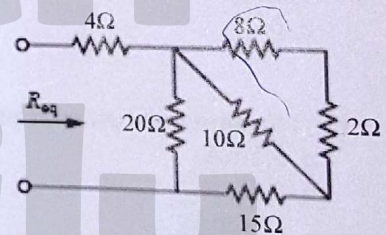- a. 59Ω
- b. 22Ω
- c. 8Ω
- d. 10Ω
- ☒ e. 14Ω



$$(8, 2) \text{ series} = 8 + 2 = 10$$

$$10 // 10 = \frac{10 \times 10}{10 + 10} = \frac{100}{20} = 5\Omega$$

$$(5, 15) \text{ series} = 5 + 15 = 20\Omega$$


$$(20 // 10) = \frac{20 \times 10}{20 + 10} = \frac{200}{30} = 6.67\Omega$$

$$(6.67, 4) \text{ series} = 10.67\Omega$$

For the circuit shown; if $V_s = 18V$, answer the questions (7-8)

7. The equivalent resistance seen from the source is:

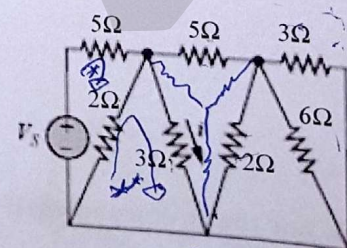- a. 1Ω
- b. 5.5Ω
- ☒ c. 6Ω
- d. 26Ω
- e. None of the above



$$I_s = \frac{18}{6} = 3A$$

$$18 \times \frac{1}{3} = 6V$$

$$18 \times \frac{1}{6} = 3A$$

$$18 \times \frac{1}{9} = 2A$$

$$18 \times \frac{1}{12} = 1.5A$$

$$18 \times \frac{1}{18} = 1A$$

$$18 \times \frac{1}{24} = 0.75A$$

$$18 \times \frac{1}{30} = 0.6A$$

$$18 \times \frac{1}{36} = 0.5A$$

$$18 \times \frac{1}{42} = 0.43A$$

$$18 \times \frac{1}{48} = 0.375A$$

$$18 \times \frac{1}{54} = 0.33A$$

$$18 \times \frac{1}{60} = 0.3A$$


$$18 \times \frac{1}{66} = 0.27A$$

$$18 \times \frac{1}{72} = 0.25A$$

$$18 \times \frac{1}{78} = 0.23A$$

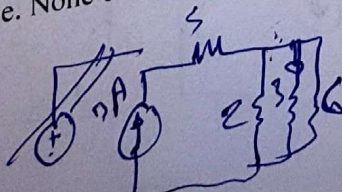8. The current i in the circuit is:

- ☒ a. 1A
- b. 0.5A
- c. 1.5A
- d. 3
- e. None of the above



$$I_3 = \frac{18}{3} = 6A$$

$$I_3 = \frac{18}{3} = 6A$$

For the circuit shown, if $V_s = 15V$. Answer the questions (9 - 12)


9. The voltage across A and B (V_{AB}) is:

- a. 9V
- b. -9V
- c. 4V
- d. -4V
- e. 0V

$$V_s \frac{1.5}{2.5} = V_s \frac{3}{9}$$

$$15 \left(\frac{1.5}{2.5} \right) = 15 \left(\frac{3}{9} \right)$$

$$9 - 5 = 4$$

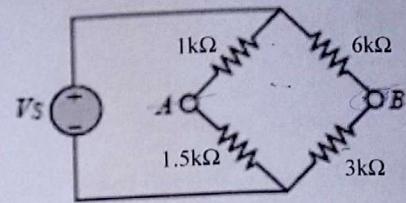

10. The Thevinin resistance seen from A and B is:

- a. 1.96kΩ
- b. 2.74kΩ
- c. 0Ω
- d. inf
- e. 2.6kΩ

11. The maximum power transferred through A and B is:

- a. 1.54mW
- b. 3.46mW
- c. 4.59mW
- d. 2.04mW
- e. 0

12. The short circuit current through A and B is:

- a. 3.5mA
- b. 3.3mA
- c. 1.46mA
- d. 1.54mA
- e. inf


13. For the circuit shown, if $I_s = 4A$, then the current I_3 is:

- a. 1A
- b. -1A
- c. 2A
- d. -2A
- e. None of the above

$$I_3 = \frac{4A}{5} \frac{20/3}{20 + 20/3}$$

$$I_3 = 4 \times \frac{20/3}{80/3}$$


$$= 4 \times \frac{1}{4} = 1A$$

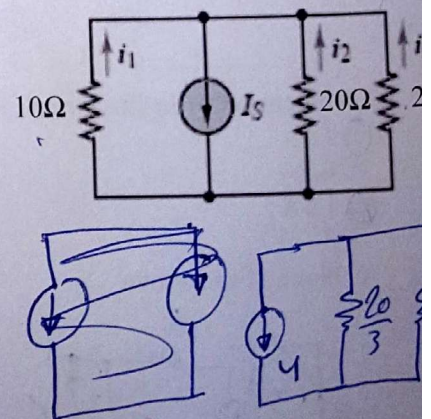

For the circuit shown below, if the current i through the voltage source was 20mA and after the disconnection of the current source the current i through the voltage source becomes 40mA. Then answer the questions (14 - 16)

14. The value of the current source (I) is:

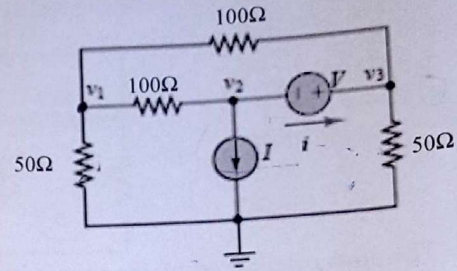- a. 8mA
- b. 16mA
- c. 20mA
- d. 24mA
- e. None of the above



15. The value of the voltage source (V) is:

- a. 4V
- b. 6V
- c. 8V
- d. 10V
- e. None of the above

16. The power delivered by the voltage source is:

- a. 80mW
- b. 160mW
- c. 120mW
- d. 240mW
- e. None of the above

$$\frac{V_1 - V_3}{100} + \frac{V_1 - 0}{50} + \frac{V_1 - V_2}{100} = 0$$

$$\left(\frac{1}{100} + \frac{1}{50} + \frac{1}{100}\right)V_1 - \frac{1}{100}V_2 - \frac{1}{100}V_3 = 0$$


V_2 and V_3 are super node

$$V_3 - V_2 = 40 \text{ mA} \times 50 \Omega \text{ A} \quad \text{--- (1)}$$

$$\frac{V_3 - 0}{50} + \frac{V_3 - V_1}{100} +$$

17. For the circuit shown, the voltage across the current source is:

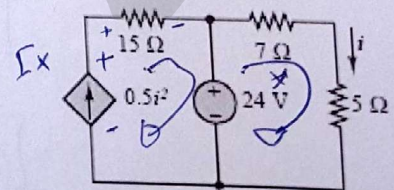- a. 2V
- b. 24V
- c. 54V
- d. 27V
- e. None of the above



$$\sum V @ \text{node} = 0$$

$$-24 + 7i + 5i = 0$$

$$12i = 24$$

$$\Rightarrow i = \frac{24}{12} = 2 \text{ A}$$

$$(2 \times 15) + 24 - V_{ix} = 0$$

$$V_{ix} = 30 + 24 = 54 \text{ V}$$

$$i_x = 0.5(2)^2$$


$$= 0.5(4)$$

$$= 2$$

For the circuit shown, answer the questions (18- 19)

18. The equivalent resistance seen by the source is:

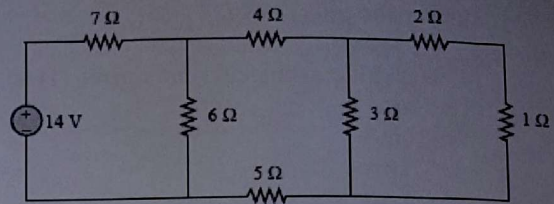- a. 28Ω
- b. 3.8Ω
- c. 9.9Ω
- d. 2.5Ω
- e. 10.8Ω




$1, 2 \text{ series} = 3$
 $(3 || 3) = \frac{3 \times 3}{3 + 3} = \frac{9}{6} = \frac{3}{2}$
 $\frac{3}{2} + 4 = 10.5$

19. The power delivered by the source is:


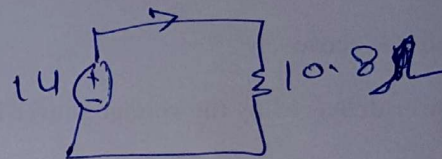
- a. 78.4W
- b. 51.6W
- c. 19.8W
- d. 18.15W
- e. 7W

$V_s = I_s R_{eq}$
 $I_s = \frac{V_s}{R_{eq}}$
 $= \frac{14}{10.81}$
 $I_s = 1.29$




20. By using source transformation for the circuit shown below, the values of V_s and R on the right circuit are:

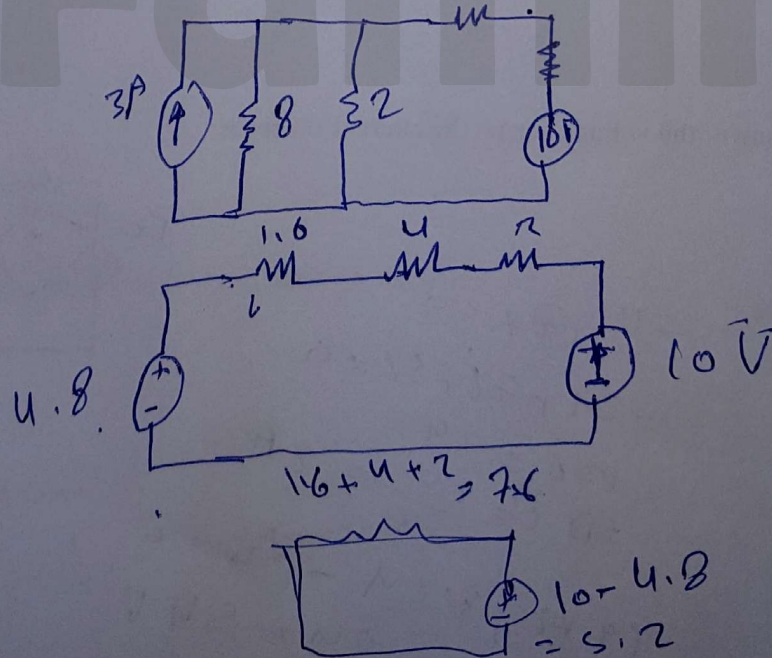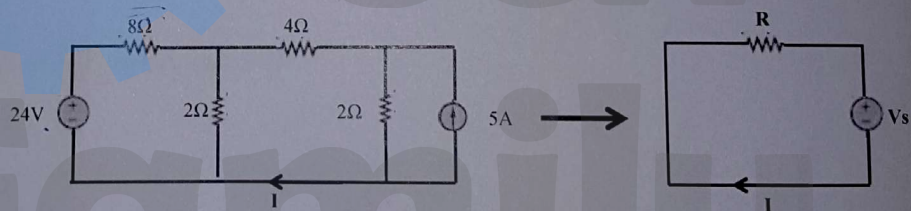- a. $5.2\text{ V}, 7.6\Omega$
- b. $14.8\text{V}, 7.6\Omega$
- c. $34\text{V}, 13\Omega$
- d. $13\text{V}, 34\Omega$
- e. None of the above



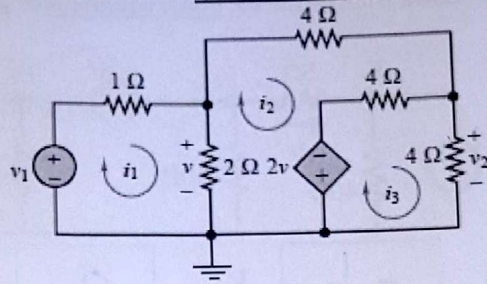Q2) (5 marks) For the circuit shown below write the mesh equations as given below:



3.5 / 5

$$\boxed{3} i_1 + \boxed{-2} i_2 + \boxed{0} i_3 = \boxed{v_1}$$

$$\boxed{-6} i_1 + \boxed{6} i_2 + \boxed{-4} i_3 = \boxed{0}$$

$$\boxed{4} i_1 + \boxed{-8} i_2 + \boxed{8} i_3 = \boxed{\text{zero}}$$

mesh

$$i_1(1) + (i_1 - i_2)2 - v_1 = 0 \Rightarrow i_1 + 2i_1 - 2i_2 - v_1 = 0$$

$$3i_1 - 2i_2 - v_1 = 0 \Rightarrow 3i_1 - 2i_2 = v_1$$

$$2i_2 - 2i_1$$

$$2(i_2 - i_1) + 4i_2 + 4(i_2 - i_3) - 4(i_1 - i_2) = 0$$


$$2i_2 - 2i_1 + 4i_2 + 4i_2 - 4i_3 - 4i_1 + 4i_2 = 0$$

$$4(i_2 - i_1) + 4i_3 + 4(i_1 - i_2) = 0$$

$$4i_3 - 4i_2 + 4i_3 + 4i_1 - 4i_2 = 0$$

$$8i_3 - 8i_2 + 4i_1$$

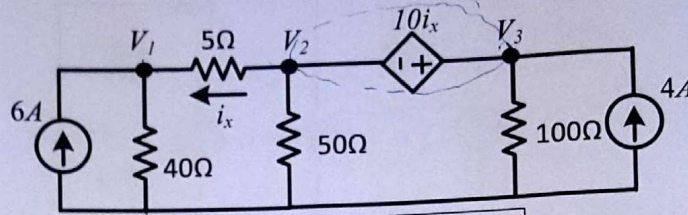Q3) (5 marks) For the circuit shown below write the nodal equations as given below:



$$\left(\frac{1}{40} + \frac{1}{5}\right) V_1 + \left(-\frac{1}{5}\right) V_2 + 0 V_3 = 6A$$

$$2 V_1 + (-3) V_2 + 1 V_3 = 2V_1$$

$$\left(-\frac{1}{5}\right) V_1 + \left(\frac{1}{5} + \frac{1}{50}\right) V_2 + \left(\frac{1}{100}\right) V_3 = 4A$$

@ node 1

$$-6A + \frac{V_1 - 0}{40} + \frac{V_1 - V_2}{5} = 0 \Rightarrow \left(\frac{1}{40} + \frac{1}{5}\right) V_1 - \frac{V_2}{5} = 6A \quad (1)$$

node 2 and node 3 are supernode

$$V_3 - V_2 = \frac{10(V_2 - V_1)}{5}$$

$$V_3 - V_2 = 2V_2 - 2V_1 \Rightarrow V_3 - 3V_2 + 2V_1 = 0 \quad (2)$$

$$\frac{V_2 - V_1}{5} + \frac{V_2 - 0}{50} + \frac{V_3 - 0}{100} - 4A = 0 \Rightarrow \frac{V_2}{5} + \frac{V_2}{50} - \frac{V_1}{5} + \frac{V_3}{100} - 4A = 0$$

$$\left(\frac{1}{5} + \frac{1}{50}\right) V_2 + \frac{V_3}{100} - \frac{V_1}{5} = 4A \quad (3)$$