

Question 1:

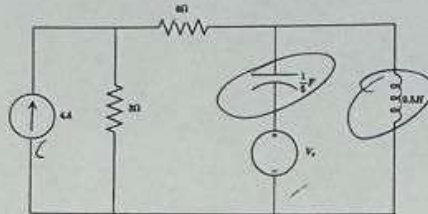


Figure: Q1

For the circuit shown in Fig. Q1, the correct first step for DC steady-state analysis is:

- A: replace both by open circuits B: replace both by short circuits **C: replace the capacitor by an open circuit and the inductor by a short circuit** D: None of them E: replace the capacitor by a short circuit and the inductor by an open circuit

Question 2:

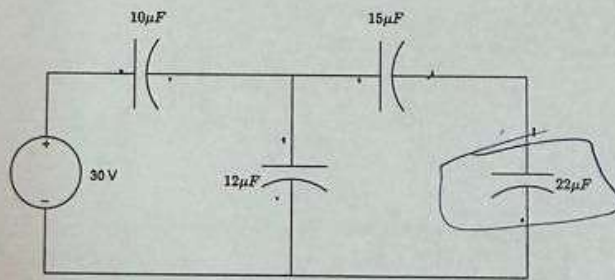


Figure: Q2

For the circuit shown in Fig. Q2, let $V_s = 30\text{ V}$. The charge on the $22\ \mu\text{F}$ capacitor is:

- A: $66\ \mu\text{C}$ B: $203\ \mu\text{C}$ **C: None of them** D: $9.7\ \mu\text{C}$ E: $86.5\ \mu\text{C}$

Question 3: Fig. Q3 shows a parallel RLC circuit.

The admittance seen by the source is:

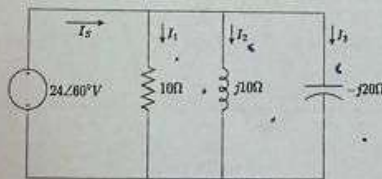


Figure: Q3

Handwritten calculations for Question 3:

$$1.1 + 0.99j$$

$$\frac{1}{10} + \frac{1}{j10} + \frac{1}{-j20} = Y$$

Handwritten calculations for Question 3:

$$\frac{10 \cdot (10j)}{10 + 10j} = \frac{20j}{10 + 10j}$$

$$\frac{(1+i)(-j20)}{1-19j} = \frac{20-20i}{20-20i}$$

- A: None of them **B: $Y = 0.1 + j0.05\ \text{S}$** **C: $Y = 0.1 - j0.05\ \text{S}$** D: $Y = 0.112\angle 26.6^\circ\ \text{S}$ E: $Y = 0.05 - j0.1\ \text{S}$

Question 4: For the circuit shown, the voltage across the capacitor V_C is expressed as:

$$\frac{V_C - V_1}{70} = 100 \angle 60^\circ$$

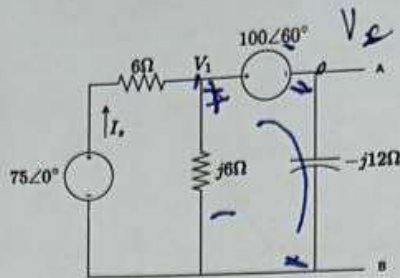


Figure: Q4

- A: $V_C = 100 \angle 60^\circ - V_1$ B: None of them C: $V_C = V_1 - 100 \angle 60^\circ$ (D) $V_C = V_1 + 100 \angle 60^\circ$ E: $V_C = V_1$

Question 5: A sinusoidal source is given by

$$v_s(t) = 10 \sin(1000t) \text{ V.}$$

It is applied to a series R-L-C circuit such that

$$Z_L + Z_C = 0$$

$$R = X_C, \quad X_L = 2X_C$$

$$X_L = 2X_C$$

$$j \cdot 2X_C - j \cdot X_C = 0$$

$$X_C = 0$$

Which of the following statements is correct regarding the voltage across the inductor V_L ?

- A: V_L leads the source voltage by 45° . B: V_L lags the source voltage by 45° . C: None of these.
 (D) V_L lags the current by 90° . E: V_L is in phase with the current.


Question 6:

pure capacitance

$$\theta = -90^\circ \text{ الجزء}$$

$$\frac{V_L}{I_L} + \frac{V_C}{I_C} = 0$$
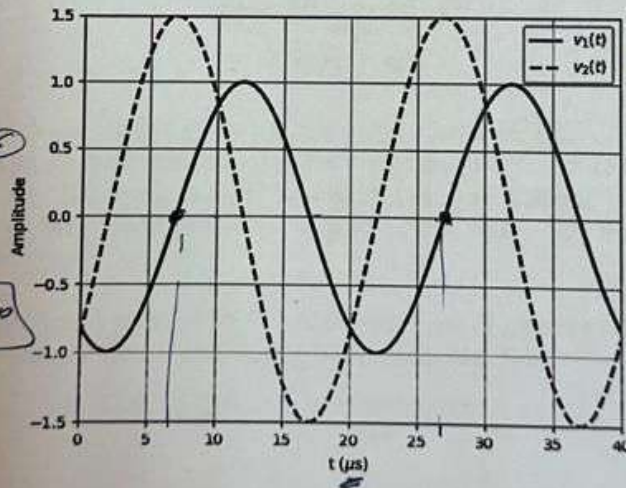
$$4 \angle 90^\circ + 4 \angle -90^\circ = 0$$



$$\omega = 1000$$

$$C = \infty$$

$$27 - 7 = 20$$

$$20 \rightarrow 360^\circ$$

The frequency of the signals is: A: 5 kHz B: 20 kHz (C) 50 kHz D: None of them E: 100 kHz

Question 7: The voltage waveform across a 1 mF capacitor is shown in Fig. Q7.

$$f = \frac{1}{T} = \frac{1}{20 \times 10^{-6}} = \frac{10^6}{20}$$

$$T = 20 \times 10^{-6} \text{ s}$$

$$V_0 = V(2) = -4 + 8 = 4$$

$$V(t) = (4, 0)$$

$$C = 1 \times 10^{-3} \text{ F}$$

$$V(t) = \frac{0-4}{2}t + 8$$

$$|V_H| = -2t + 8$$

$$\frac{dV}{dt} = -2$$

$$\frac{dV}{dt} = -8 + b \quad b = +8$$

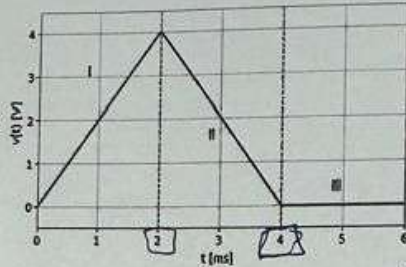


Figure: Q7

$$i_c = C \frac{dV}{dt}$$

$$i_c = 10^{-3} (-2) \Rightarrow +4$$

$$i_c = -2 \times 10^{-3} + 4$$

$$3.998 \approx 4$$

is:

A: 0 A. B: -2 A. C: +2 A. D: None of these. E: -4 A.

Question 8: The figure shows the voltage waveform applied to a load.

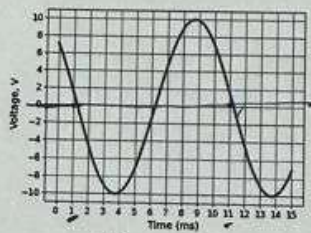


Figure 3: Q8


$$10 \sin\left(\frac{2\pi}{T}t - 1^\circ\right)$$

$$10 \cos\left(\frac{2\pi}{10}t - 90^\circ\right)$$

$$-90 - 75 = -$$

The current through the load is given by: $i(t) = 2 \cos(\omega t + 75^\circ) \text{ A}$. Determine the type of load and its equivalent parameters. A: R-C load, with $R = 4.33 \Omega$ and $C = 636.6 \mu\text{F}$ B: R-L load, with $R = 4.33 \Omega$ and $L = 3.98 \text{ mH}$ C: Purely resistive load, with $R = 5 \Omega$ D: Purely capacitive load, with $C = 318.3 \mu\text{F}$ E: Purely inductive load, with $L = 7.96 \text{ mH}$

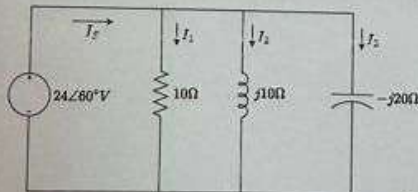Question 9: Fig. Q9 shows a parallel RLC circuit and a set of phasors labeled A_1 to A_4 . Which phasor represents the current through the capacitor I_C ?



$$I_C = \frac{24 \angle 60^\circ}{10 + 10j + -j20} = \frac{24 \angle 60^\circ}{10 + 10j} = 339.4 \angle 105^\circ$$

$$I_C = 23.9 \angle 150^\circ$$


It is applied to a series $R-L-C$ circuit such that

$R = X_C, \quad X_L = 2X_C$

Find the phasor angle of the voltage across the inductor V_L .

- A: None of these. B: -135° . C: $+45^\circ$. D: -90° . E: -45° .

Question 17:

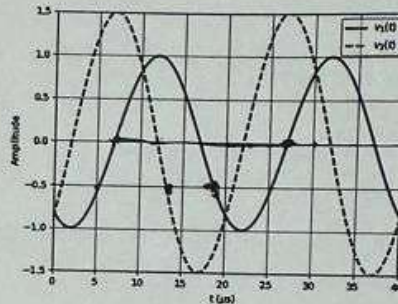

$\phi = 180^\circ$
 2π

$\phi_V = ? \quad \phi = +90^\circ$


~~$V_L = ?$~~

$\phi_V - \phi_i = -90$

$\frac{1}{45} =$
 $20 \mu s$

The time shift between the two signals is approximately: A: $15 \mu s$ B: $5 \mu s$ C: None of them D: $10 \mu s$ E: $2 \mu s$

Question 18:

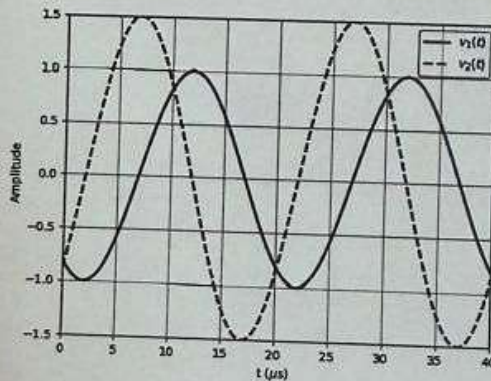

$20 \rightarrow 360^\circ$
 $50 \rightarrow \phi$
 v_1^3
 90


The phase difference defined as $\angle v_1(t) - \angle v_2(t)$ is:

- A: 120° B: -90° C: 180° D: 90° E: None of them

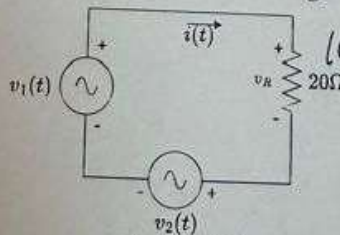Question 19: The sources in the circuit are:

$v_1(t) = 6 \cos(300t - 45^\circ), \quad v_2(t) = 10 \sin(120t + 30^\circ)$

Determine the current through the resistor.



$6 \angle -45^\circ$
 $10 \angle -60^\circ$

Figure: Q19

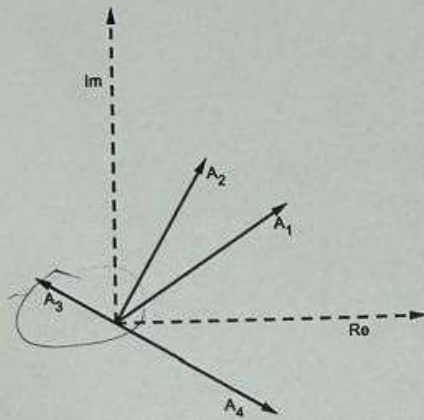


Figure: Q9

A: None of them (B) A_3 C: A_2 D: A_1 E: A_4

Question 10: For the circuit shown, the phase relation between V_s and I_s is:


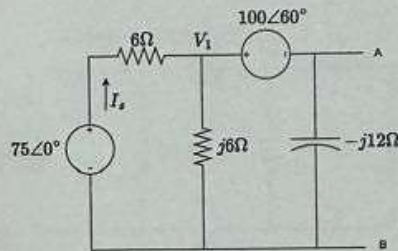


Figure: Q10

A: They are in phase B: I_s lags V_s by 60° C: I_s leads V_s by 28.7° D: I_s lags V_s by 28.7° E: None of them

Question 11: Fig. Q11 shows a parallel RLC circuit and its phasor diagram. Which phasor represents the total source current I_S ?

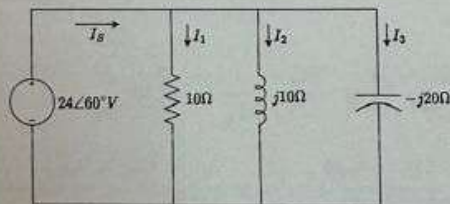

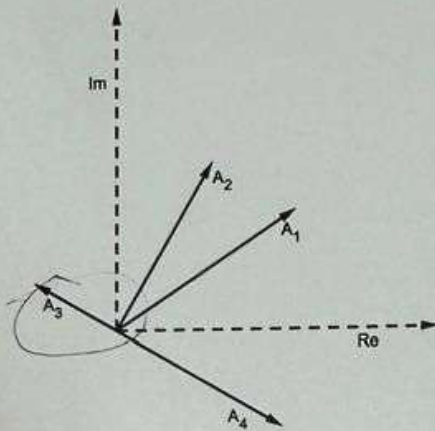


Figure: Q9

A: None of them (B) A_3 C: A_2 D: A_1 E: A_4

Question 10: For the circuit shown, the phase relation between V_s and I_s is:


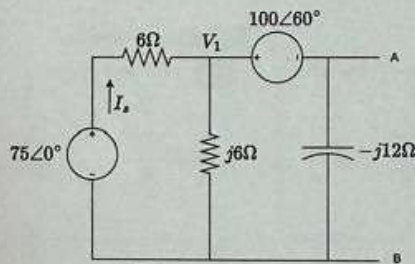


Figure: Q10

A: They are in phase B: I_s lags V_s by 60° C: I_s leads V_s by 28.7° D: I_s lags V_s by 28.7° E: None of them

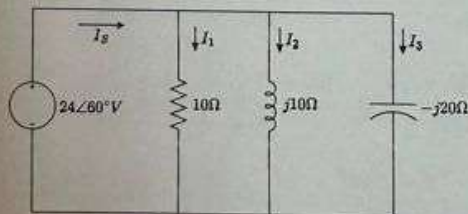Question 11: Fig. Q11 shows a parallel RLC circuit and its phasor diagram.

Which phasor represents the total source current I_S ?



$$L = 2 \times 10^{-3} \text{ H}$$

Figure: Q13

The inductor voltage $v_L(t)$ during the interval

$$2 \leq t \leq 4 \text{ ms}$$

is:

- A: None of these. **B: -4 V.** C: +4 V. D: -8 V. E: 0 V.

Question 14: The circuit shown in Fig. Q14 can be solved using one supermesh equation together with the current-source constraint equation. Which of the following equations correctly describes the supermesh in terms of i_x ?

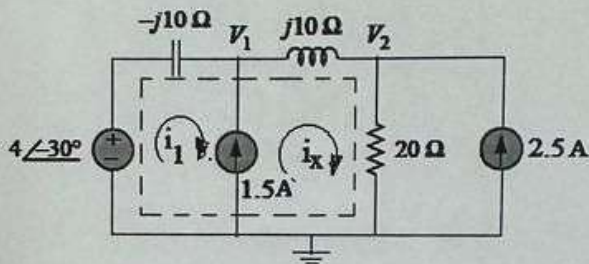


Figure: Q14

A:

$$-4\angle -30^\circ + j10(i_x - 1.5) + j10i_x + 20(i_x + 2.5) = 0$$

B:

$$4\angle -30^\circ - j10(i_x - 1.5) + j10i_x + 20(i_x + 2.5) = 0$$

C: None of these. D:

$$-4\angle -30^\circ - j10(i_x - 1.5) + j10i_x + 20(i_x + 2.5) = 0$$

E:

$$-4\angle -30^\circ - j10(i_x + 1.5) + j10i_x + 20(i_x - 2.5) = 0$$

Question 15:

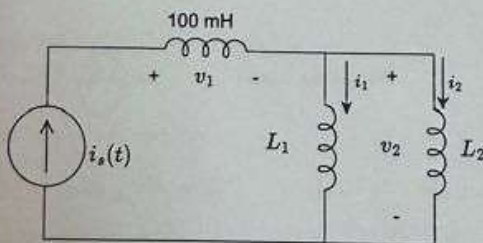


Figure: Q15

For the circuit shown in Fig. Q15, let $i_s(t) = 6(1 - e^{-5t})$ mA, with $i_2(0) = 0$, $L = 100$ mH, $L_1 = 20$ mH, and $L_2 = 40$ mH. The current $i_2(t)$ is:

- A: $4(1 - e^{-5t})$ mA B: $2e^{-5t}$ mA C: $2(1 - e^{-5t})$ mA D: None of them E: $6(1 - e^{-5t})$ mA

Question 16: A sinusoidal source is given by

$$v_s(t) = 10 \sin(1000t) \text{ V.}$$

$$-90^\circ$$



- A: $i(t) = 0.3 \cos(300t - 45^\circ) + 0.5 \sin(120t + 30^\circ)$ A B: $i(t) = 0.3 \cos(300t - 45^\circ) - 0.5 \sin(120t + 30^\circ)$ A
 C: $i(t) = 0.5 \sin(120t + 30^\circ) - 0.3 \cos(300t - 45^\circ)$ A D: $i(t) = 6 \cos(300t - 45^\circ) - 10 \sin(120t + 30^\circ)$ A
 E: None of them

Question 20: For the circuit shown, the source current I_s is:

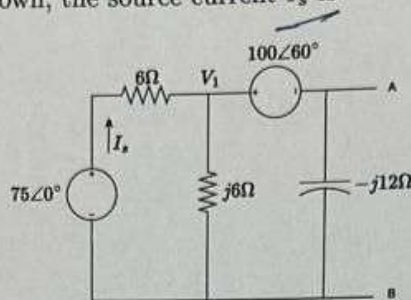


Figure: Q20

- A: $11.33 \angle -28.7^\circ$ A B: $5.37 \angle 26.6^\circ$ A C: $6.02 \angle -25.2^\circ$ A D: $11.33 \angle 28.7^\circ$ A E: None of them

$$I_s = \frac{75 \angle 0^\circ}{13.4 \angle 63.4^\circ}$$

$$Z_{total} = \frac{(j12)(6j)}{6j} + 6 \quad I_s = \boxed{5.59 \angle -63.4^\circ}$$

$$= \frac{-72}{6j} + 6 = 13.4 \angle 63^\circ$$

$$I_s = \frac{100 \angle 60^\circ}{13.4 \angle 63^\circ} = 7.46 \angle -3^\circ$$

$$\underline{41.7 \angle 190.2^\circ}$$

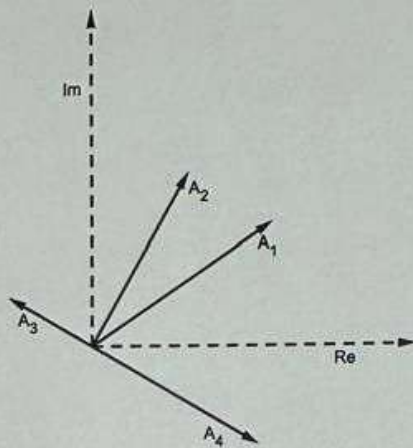


Figure: Q11

A: A_1 B: A_2 C: A_3 D: A_4 E: None of them

Question 12: For the circuit shown in Fig. Q12, which of the following equations correctly represents the supernode equation written in terms of V_1 ?

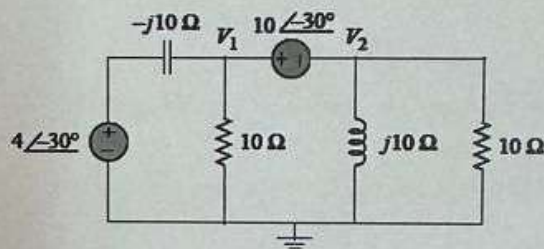


Figure: Q12

A:

$$\frac{V_1 - 4\angle -30^\circ}{-j10} + \frac{V_1}{10} + \frac{V_1 + 10\angle -30^\circ}{j10} + \frac{V_1 + 10\angle -30^\circ}{10} = 0$$

B: None of these. C:

$$\frac{V_1 - 4\angle -30^\circ}{-j10} + \frac{V_1}{10} + \frac{V_1 - 10\angle -30^\circ}{j10} + \frac{V_1 - 10\angle -30^\circ}{10} = 0$$

D:

$$\frac{V_1 - 4\angle -30^\circ}{j10} + \frac{V_1}{10} + \frac{V_1 + 10\angle -30^\circ}{j10} + \frac{V_1 + 10\angle -30^\circ}{10} = 0$$

E:


$$\frac{V_1 - 4\angle -30^\circ}{-j10} + \frac{V_1}{10} + \frac{V_1 - 10\angle -30^\circ}{10} = 0$$

$i(2) =$

Question 13: The current waveform through a 2 mH inductor is shown in Fig. Q13.

$$V_L = L \frac{di}{dt}$$

$$V_L = 2 \times 10^{-3} (-2) =$$

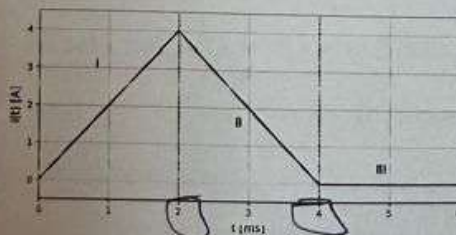

$$i(t) = \frac{-4}{2} t$$

$$\frac{di}{dt} = \boxed{-2}$$