

Introduction to Electrical Circuits




Motivation

Electrical circuits seem to be everywhere!






Electric Circuit

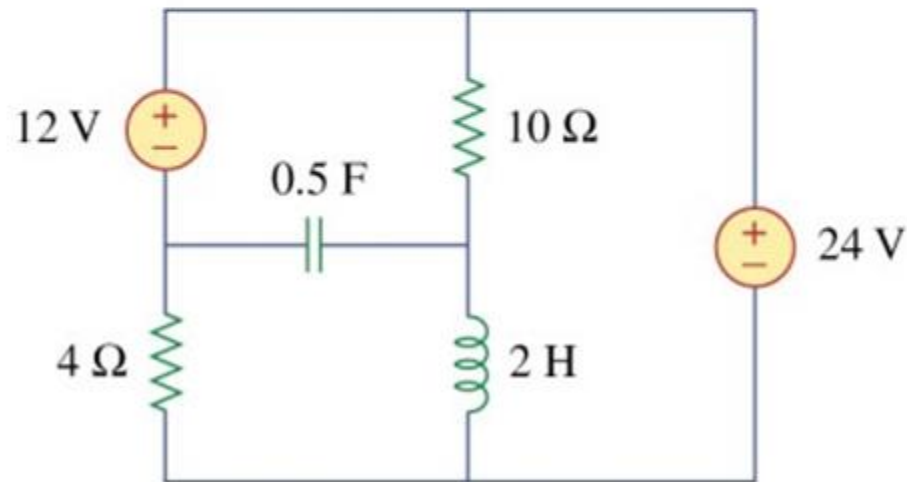- Electricity: physical phenomenon arising from the existence and interaction of electric charge.
- Electric circuit: interconnection of electrical components linked together in a closed path to allow electric charge to flow.



A Simple Circuits

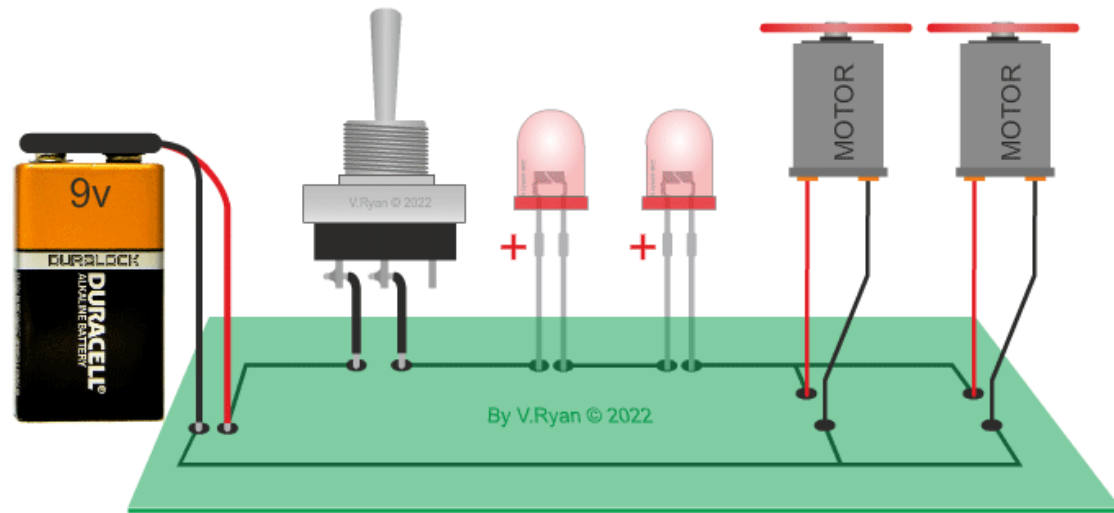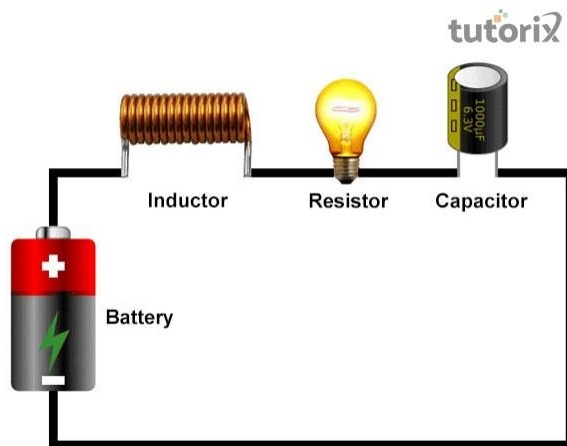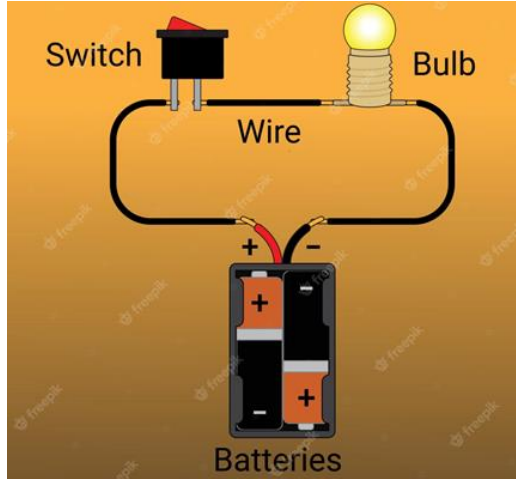


Electric Current (Charges in Motion!)

- **Current:** net flow of charge across any cross section of a conductor, measured in Amperes (Andre-Marie Ampere (1775-1836), a French mathematician and physicist)



- Current can be thought of as the rate of change of charge:

$$i = \frac{dq}{dt}$$

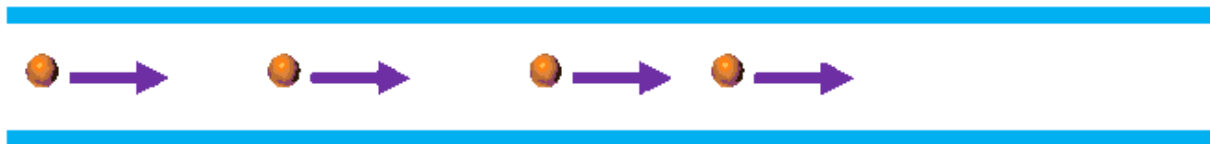


Electric Current

- Originally scientists (in particular Benjamin Franklin (1706-1790) an American scientist and inventor) thought that current is only due to the movement of positive charges.






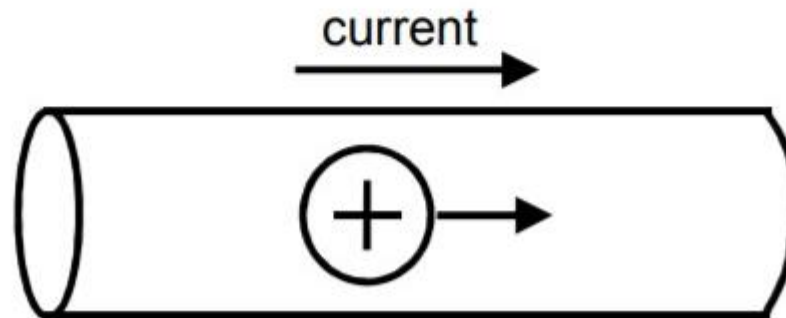- Thus the direction of the current was considered the direction of movement of positive charges.




Direction of Current

Direction of electron motion

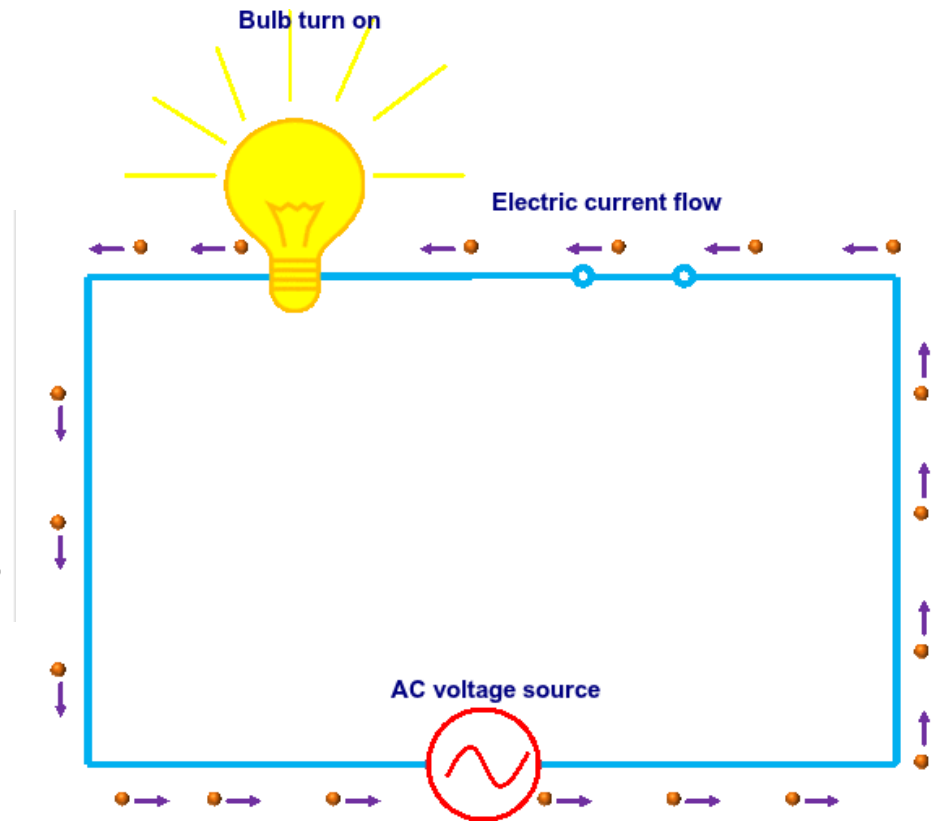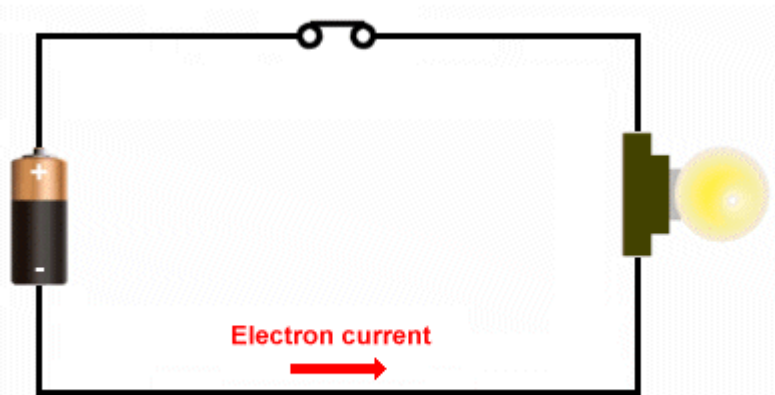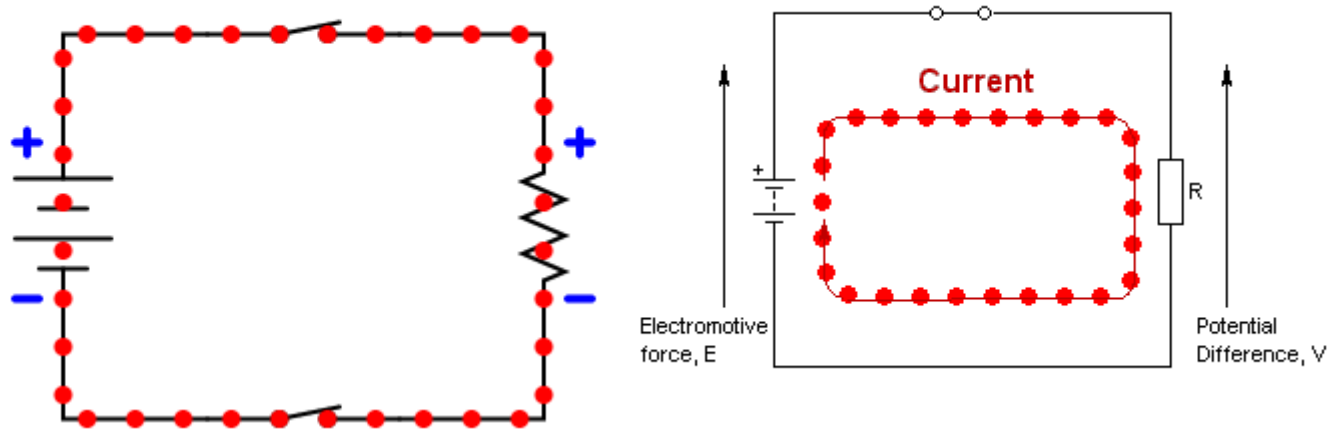

Electric Current



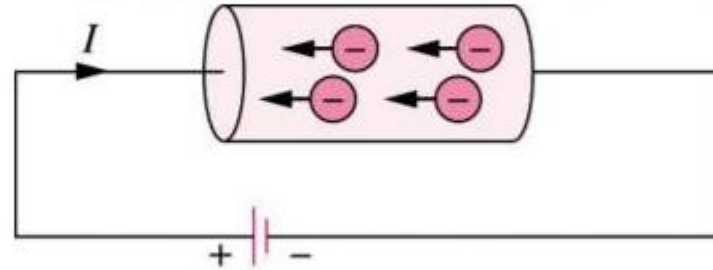
- In reality in metallic conductors current is due to the movement of **electrons**, however, we follow the universally accepted convention that current is in the direction of positive charge movement.






- Two ways of showing the same current:



Two Important Types of Currents

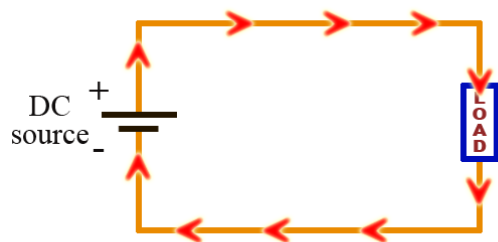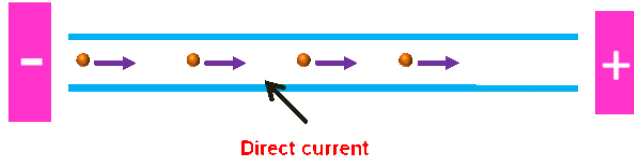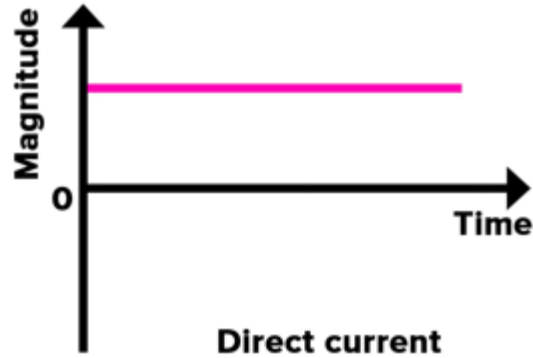


Direct Current

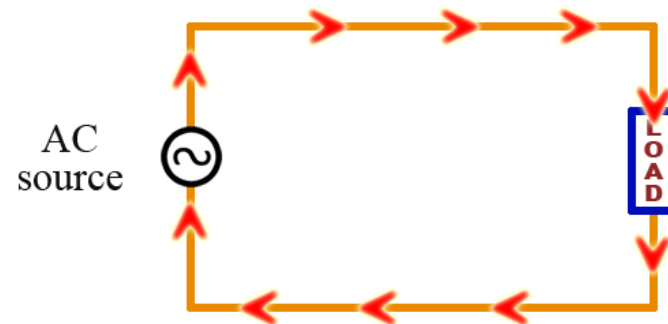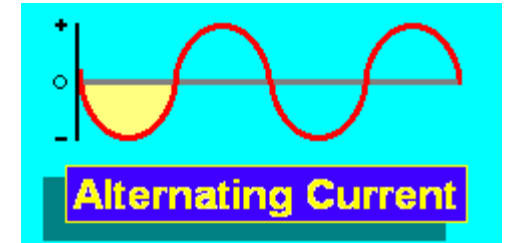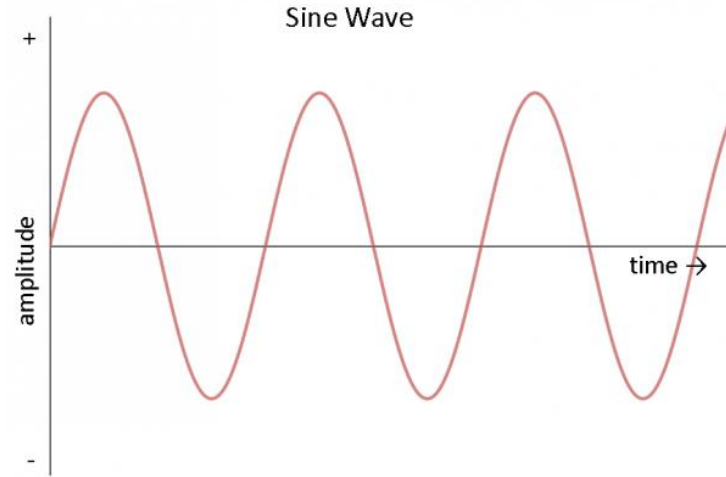


Alternating Current

Two Important Types of Currents

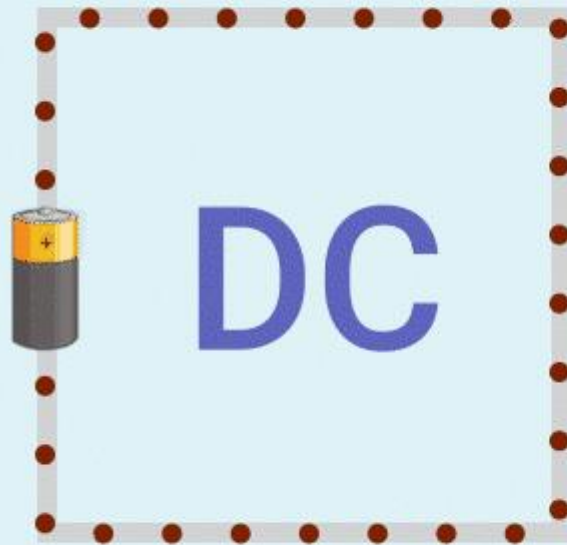


Direct Current

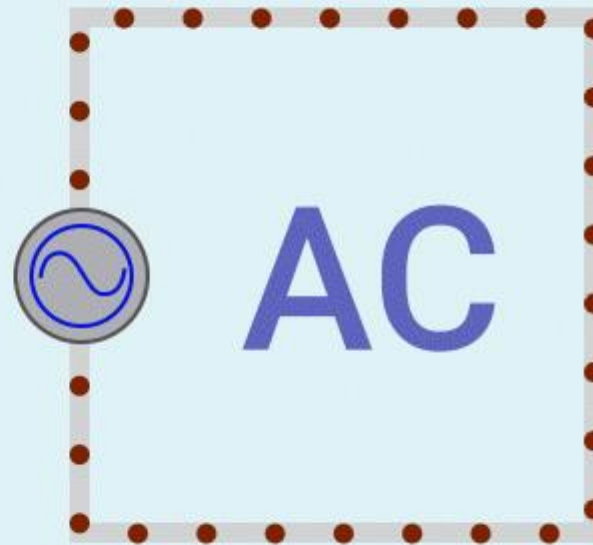


Alternating Current

Alternating Current: The Water Analogy

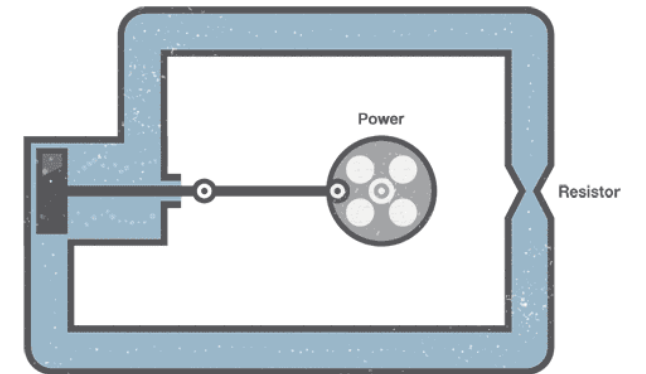


Alternating current

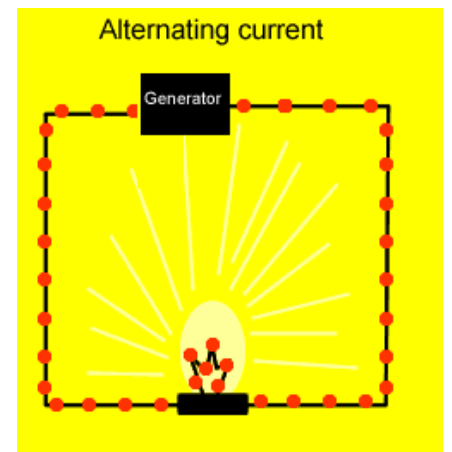


Voltage (Separation of Charges)

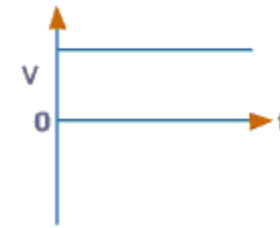- **Voltage** (electromotive force, or potential) is the energy required to move a unit charge through a circuit element, and is measured in Volts (Alessandro Antonio Volta (1745-1827) an Italian Physicist).




DC Source

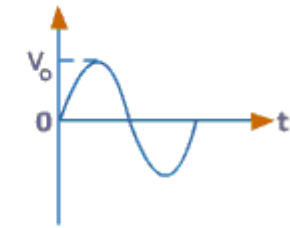

AC Source



$$v = \frac{dW}{dq}$$

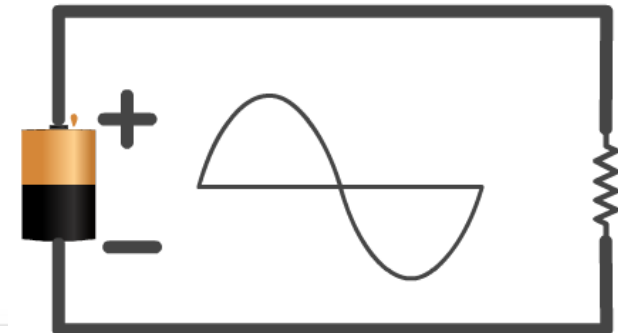- Similar to electric current, there are two important types of voltage: DC and AC



Voltage Polarity

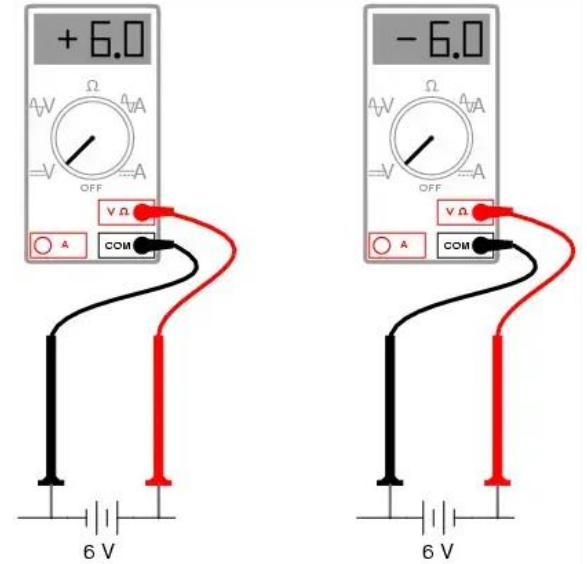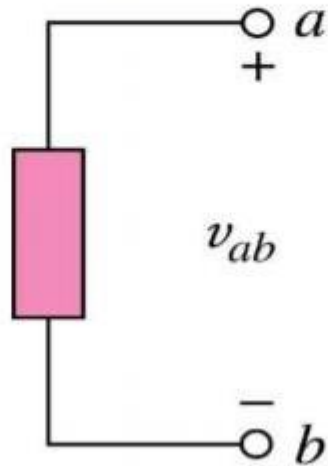
- The plus (+) and minus (-) sign are used to define voltage polarity.
- The assumption is that the potential of the terminal with (+) polarity is higher than the potential of the terminal with (-) polarity by the amount of voltage drop.




- The polarity assignment is somewhat arbitrary! Is this a scientific statement?!! What do you mean by arbitrary?!!!

Voltage Polarity

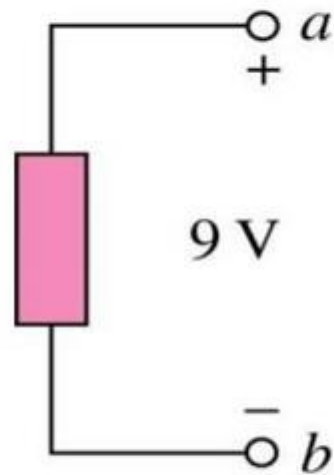- Figures (a) and (b) are two equivalent representation of the same voltage:




(a)

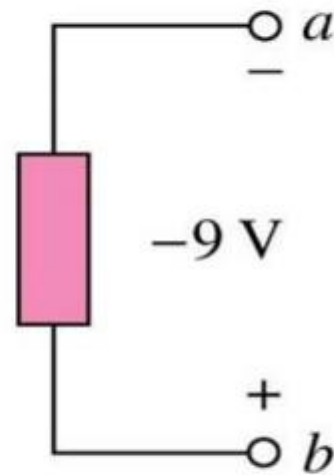


(b)

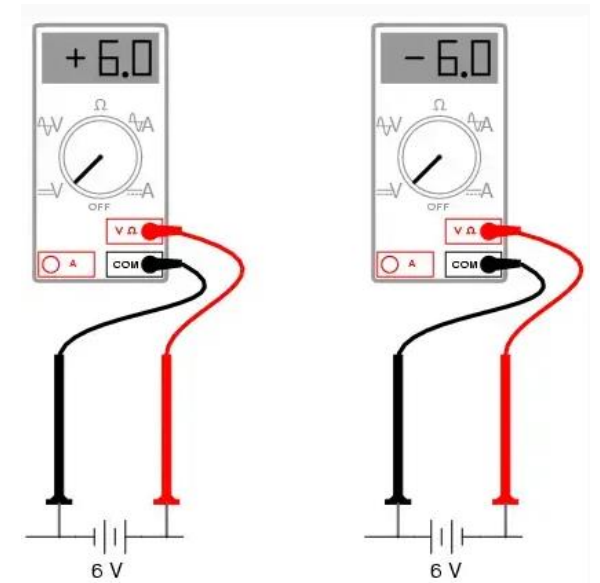
- Both show that the potential of terminal a is 9V higher than the potential of terminal b .




Circuit Elements


- Circuit components can be broadly classified as being either **active** or **passive**.
- An active element is capable of generating energy.
 - Example: current or voltage sources
- A passive element is an element that does not generate energy, however, they can either consume or store energy.
 - Example: resistors, capacitors, and inductors

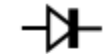 Diode

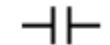 Capacitor


 Inductor

 Resistor

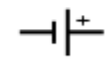 DC voltage source








 AC voltage source

Basic Circuit Elements

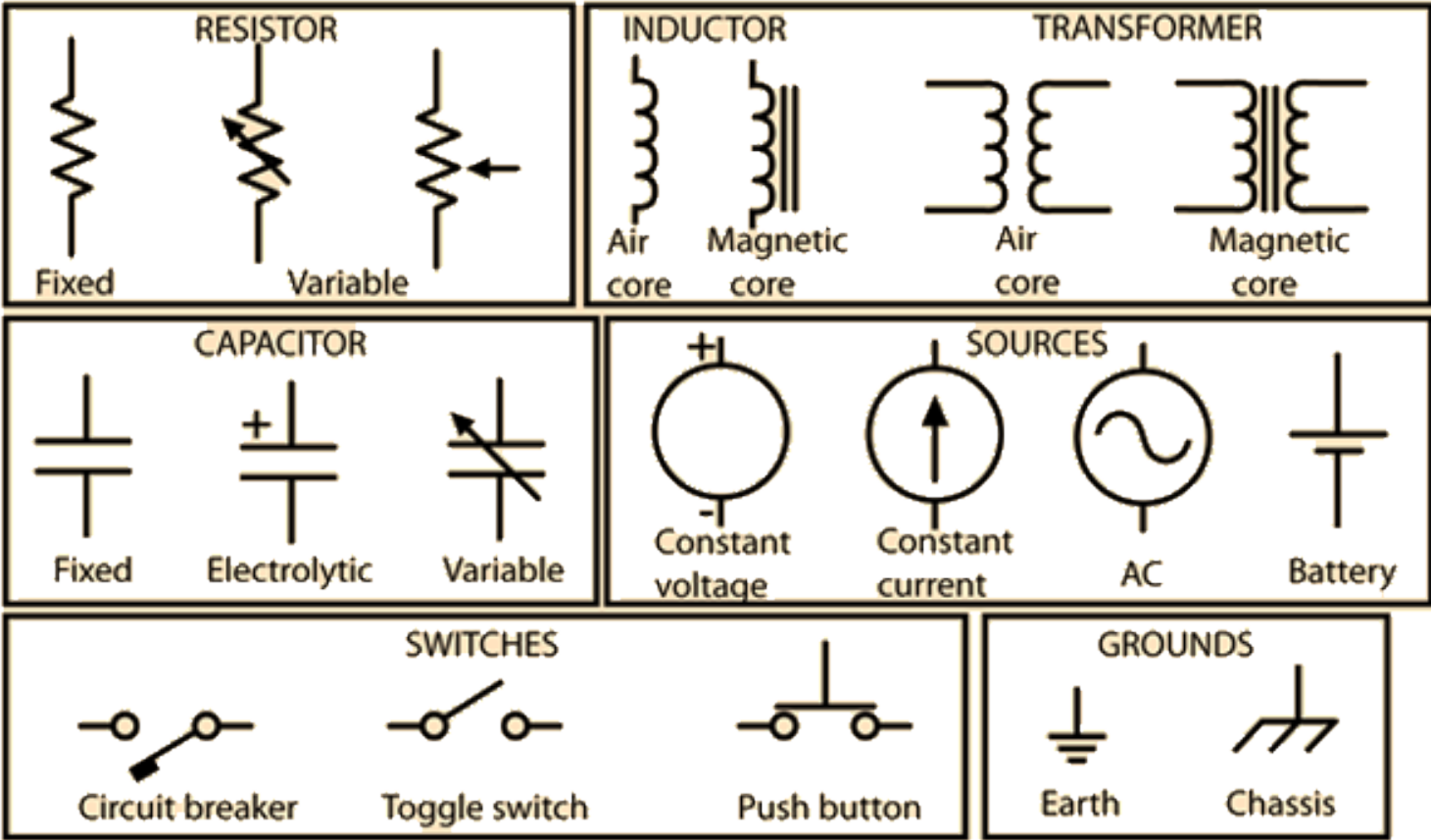


Ideal Voltage and Current Sources

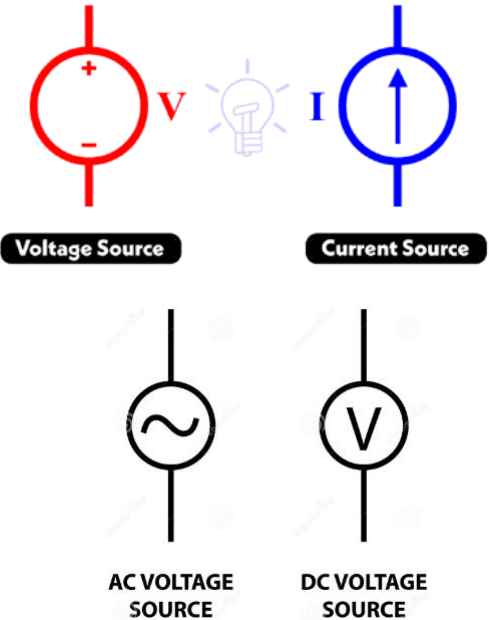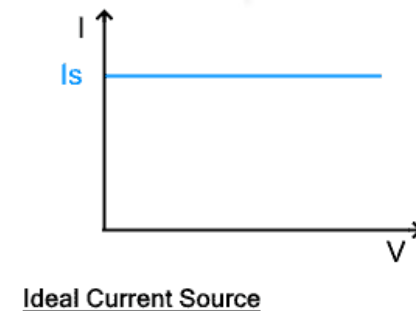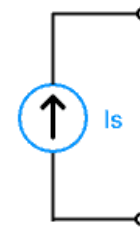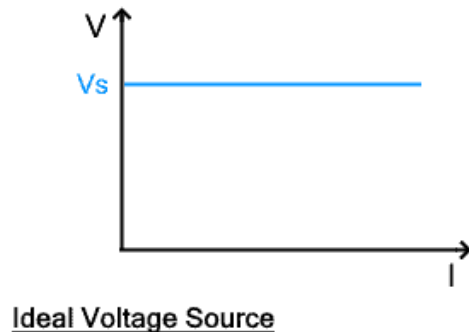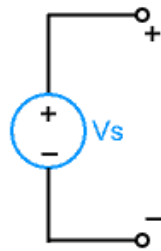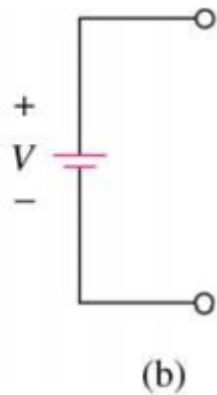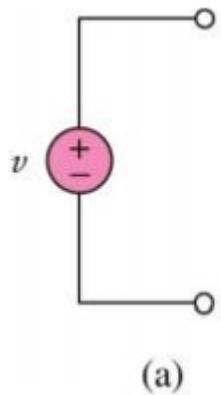- Independent sources: An (ideal) independent source is an active element that provides a specified voltage or current that is independent of other circuit elements and/or how the source is used in the circuit.
- Symbol for independent voltage source
 - Used for constant or time-varying voltage
 - Used for constant voltage (dc)




Ideal Voltage and Current Sources

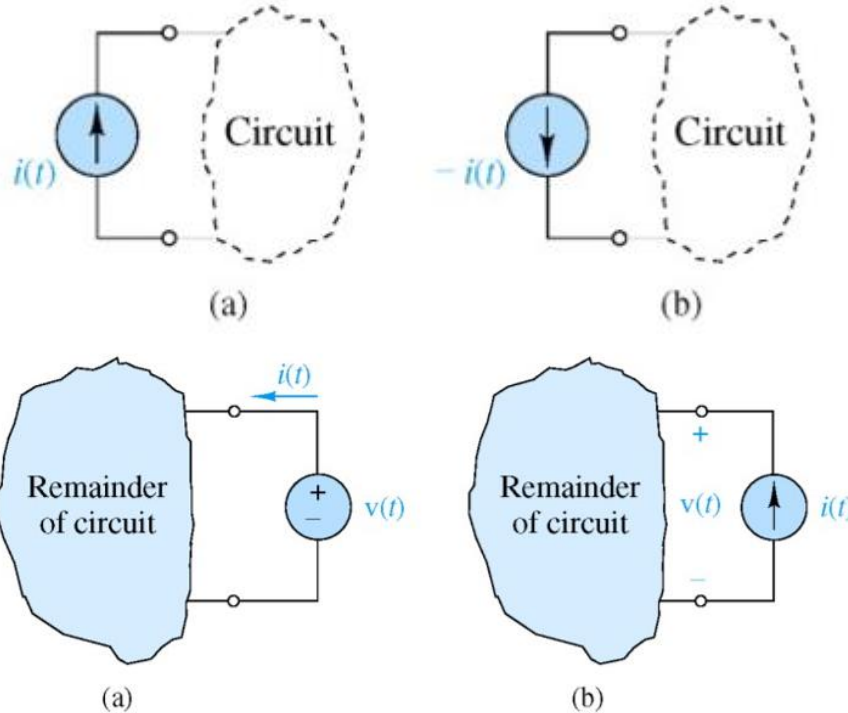
- Equivalent representation of ideal independent current sources whose current $i(t)$ is maintained under all voltage requirements of the attached circuit:



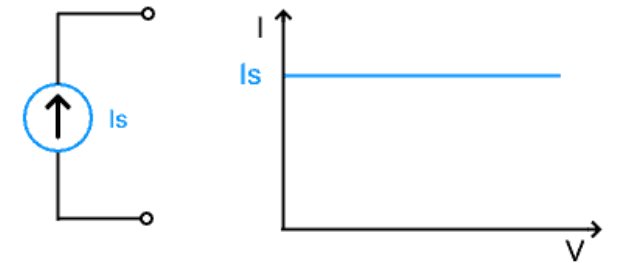Common Voltage and Current Source Labeling




Ideal Current Source

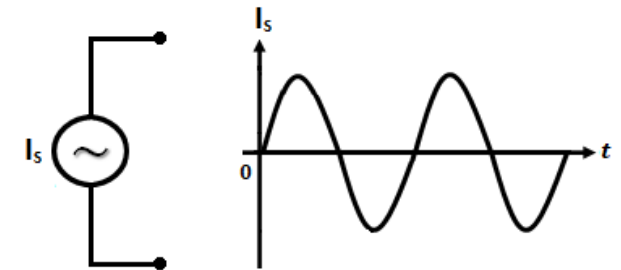

Alternating Current Source


Resistance

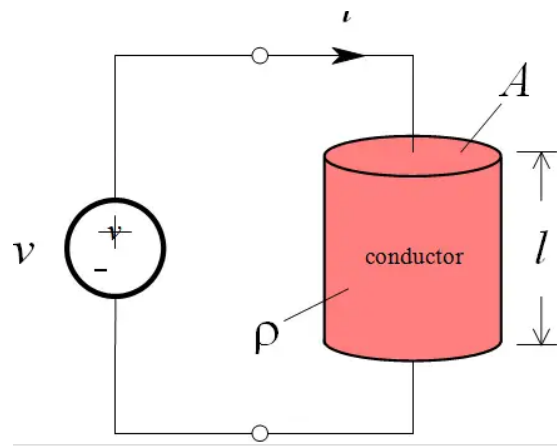- Different materials allow charges to move within them with different levels of ease. This physical property or ability to resist current is known as resistance.
- The resistance of any material with a uniform cross-sectional area A and length l is inversely proportional to A and directly proportional to l .



$$R \propto \frac{l}{A} \quad R = \rho \frac{l}{A}$$

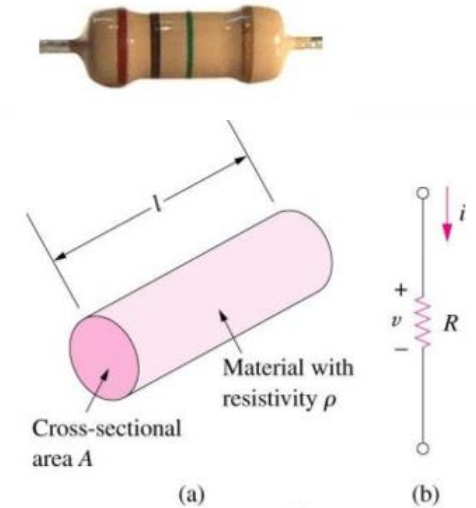A circuit diagram of a resistor R with current I flowing through it and voltage V across it.



- The constant of the proportionality is the resistivity of the material, i.e., ρ
- A conductor designed to have a specific resistance is called a resistor.
- In honor of George Simon Ohm (1787-1854), a German physicist, the unit of resistance is named Ohm (Ω).






Ohm's Law

- The voltage v across a resistor is directly proportional to the current i flowing through the resistor. The proportionality constant is the resistance of the resistor, i.e., $v(t) = Ri(t)$

- One can also write: $i(t) = \frac{1}{R}v(t) \Rightarrow i(t) = Gv(t)$

- Instantaneous power dissipated in a resistor
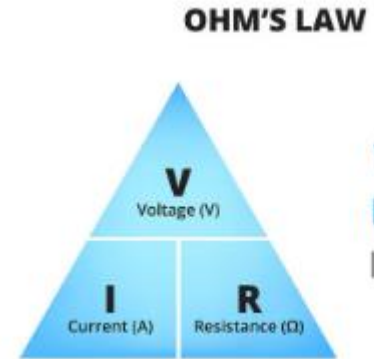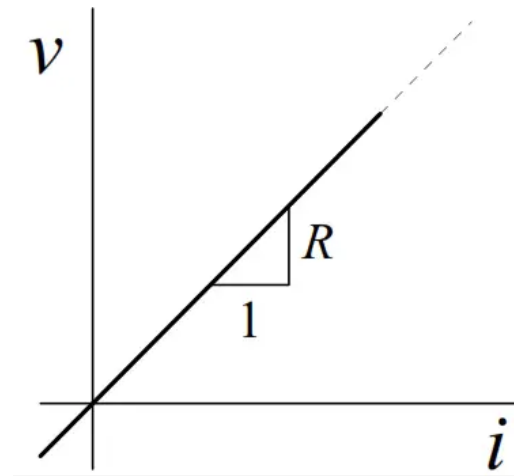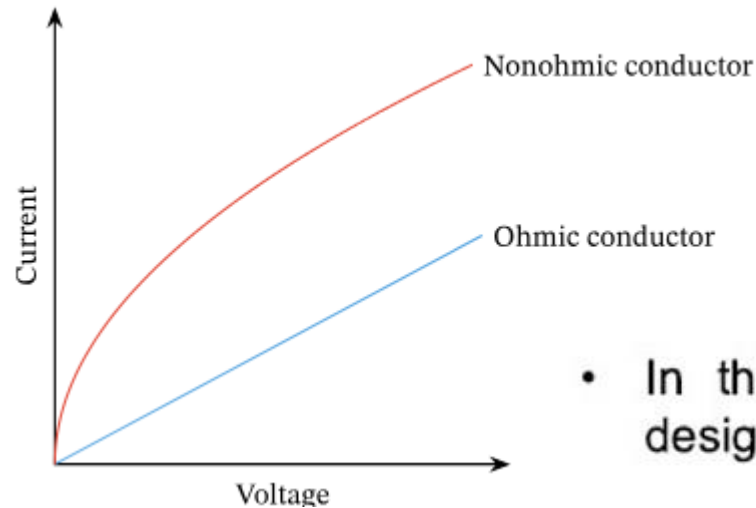
$$p(t) = v(t)i(t) = \frac{v^2(t)}{R} = Ri^2(t)$$



$$V = I \cdot R$$
$$R = V : I$$
$$I = V : R$$




$$I = \frac{V}{R}$$



- In this course, we assume that all the elements that are designated as resistors are linear (unless mentioned otherwise)


Fixed and Variable Resistors

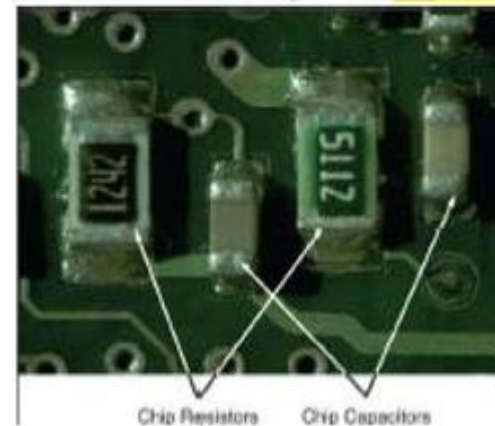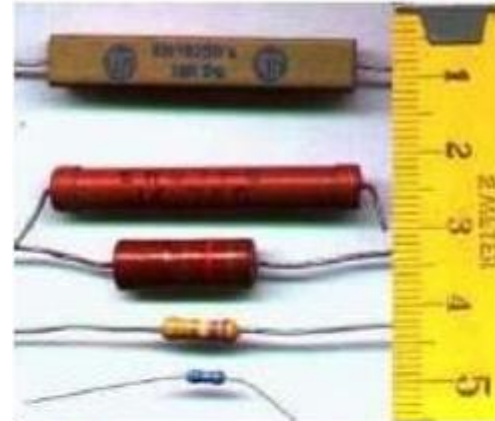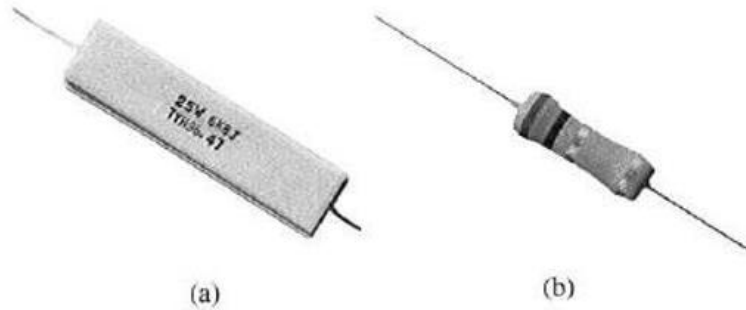- Fixed resistors have a resistance that remains constant.
- Two common types of fixed resistors are:
 - (a) wirewound
 - (b) composition (carbon film type)



Fixed Resistors

- Inside the resistor

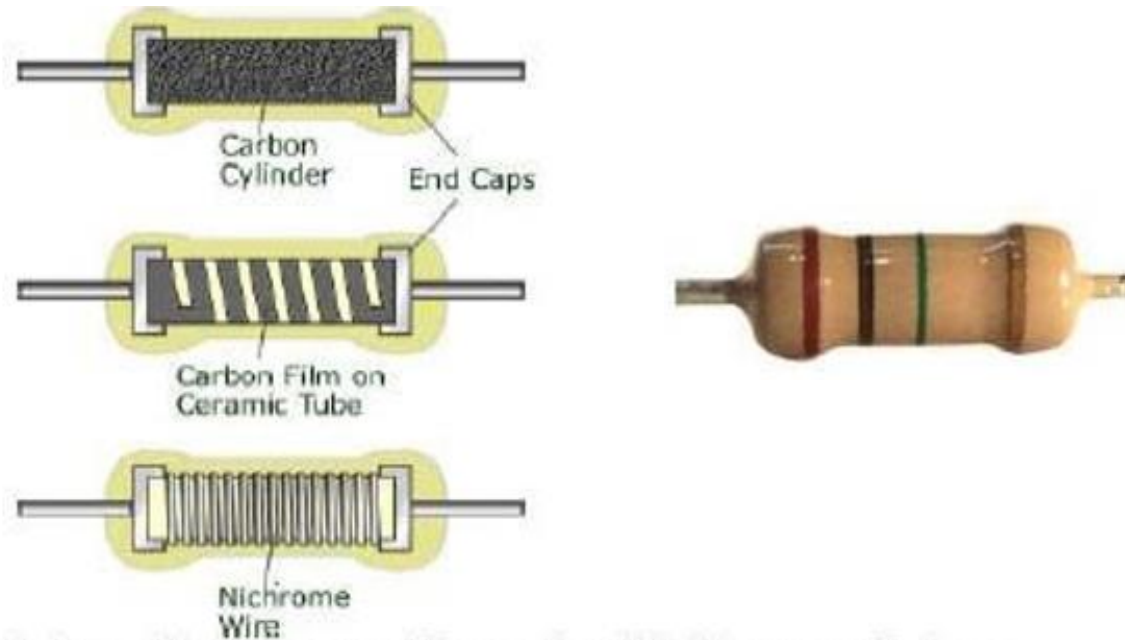


- A common type of resistor that you will work with in your labs:
- It has 4 color-coded bands (3 for value and one for tolerance)
 - How to read the value of the resistor?

Variable Resistors

- Variable resistors have adjustable resistance and are typically called potentiometer (or pot for short).
- Potentiometers have three terminals one of which is a sliding contact or wiper.



(a)

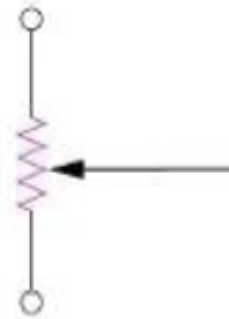


(b)




Conductance


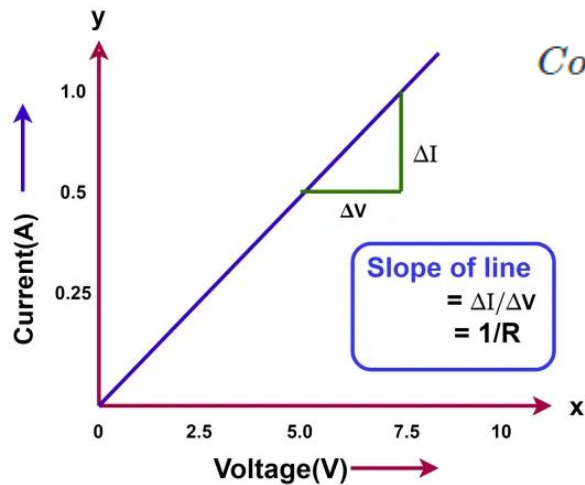
- $G=1/R$ is called the conductance of the element and is measured in siemens (S) or mho (\Uparrow).
- Conductance is the ability of an element to conduct current.
- A device with zero (no) resistance has infinite conductance and a device with infinite resistance has zero conductance.


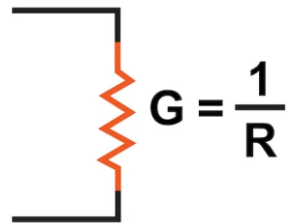
$$\text{Conductance (S)} = \frac{1}{\text{Resistance } (\Omega)}$$




Conductance and resistance

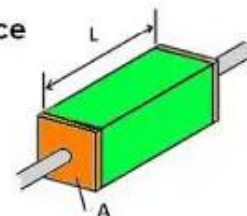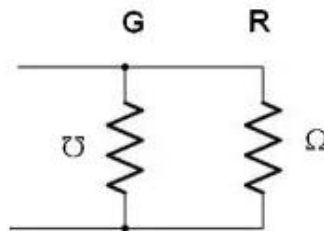


$$G = 1/R = l/V$$

$$G = (A\sigma)/L$$

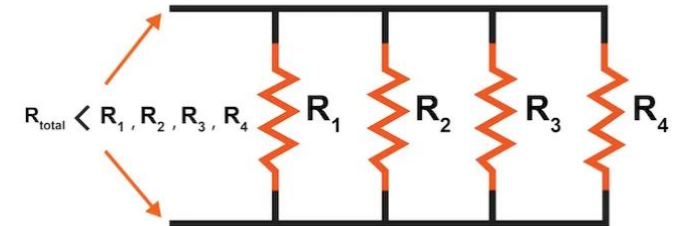German inventor
Ernst Werner von
(1816-1892)


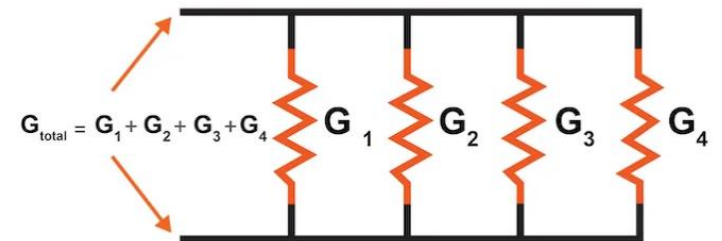
$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$





$$R_{total} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

Short Circuit and Open Circuit





- A device with zero resistance is called short circuit and a device with zero conductance (i.e., infinite resistance) is called open-circuit.

A **short circuit** is the one where components are connected with a very small or zero resistance wire.

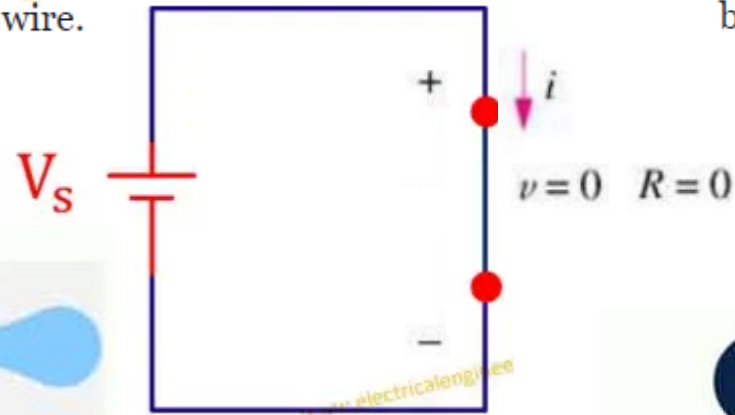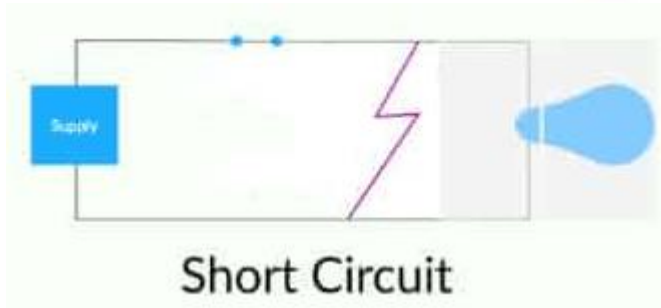An **open circuit** is the one having a disconnection between components.




Short circuit

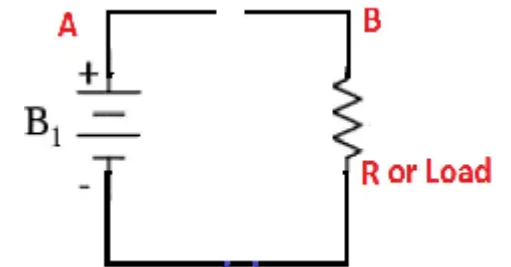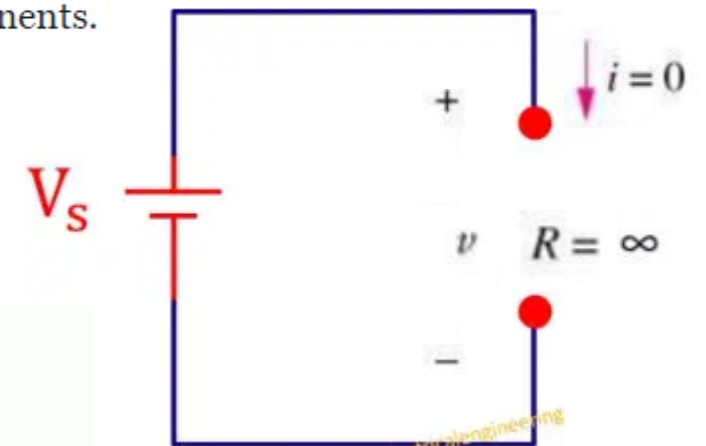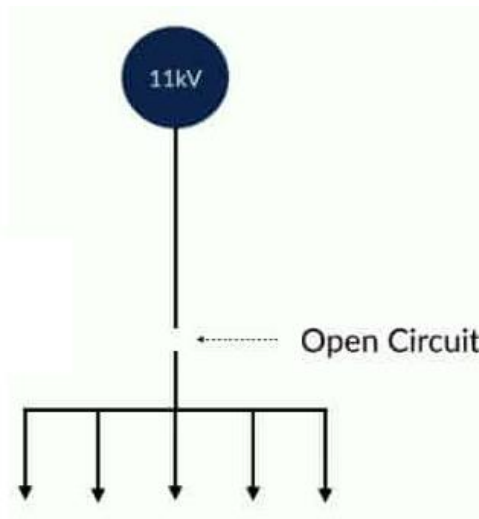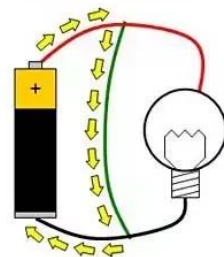


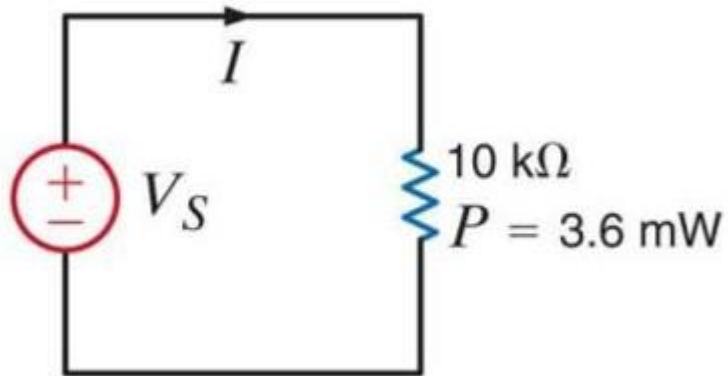Examples

- The power absorbed by the 10-k Ω resistor in the following circuit is 3.6 mW. Determine the voltage and the current in the circuit.



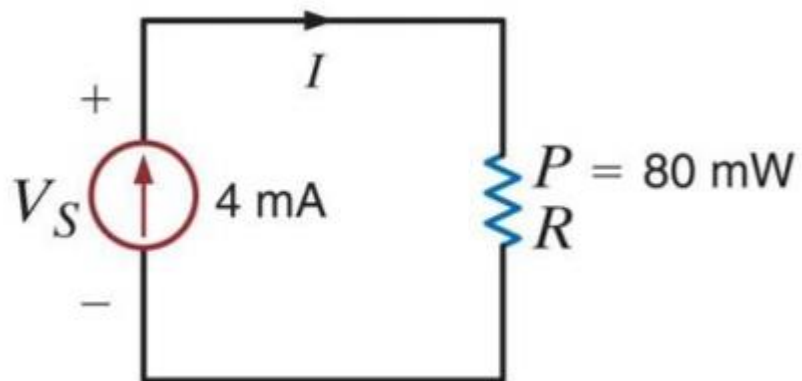- Given the following network, find R and V_S .



Electrical Power & Energy


- **Electrical Power**

- The rate of change of (expending or absorbing) energy per unit time, measured in Watts (James Watt (1736-1819) a Scottish inventor and mechanical engineer)




$$p = \frac{dW}{dt} = \frac{dW}{dq} \times \frac{dq}{dt} = vi \qquad \text{watt} = W = \frac{\text{joule}}{\text{second}} = \frac{J}{s}$$
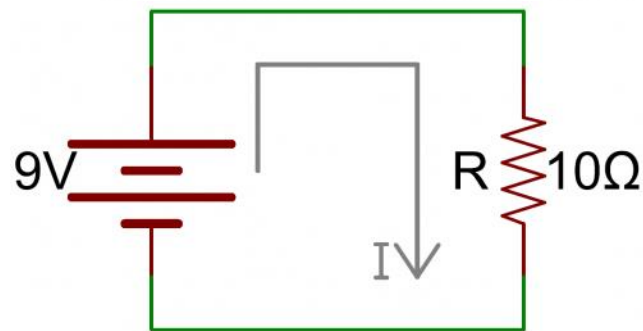
$$\text{power} = \text{volts} \times \text{amperes} = \frac{\text{joules}}{\cancel{\text{coulomb}}} \times \frac{\cancel{\text{coulomb}}}{\text{second}} = \text{watt}$$



$$I = \frac{V}{R} = \frac{9V}{10\Omega} = 0.9A = 900mA$$
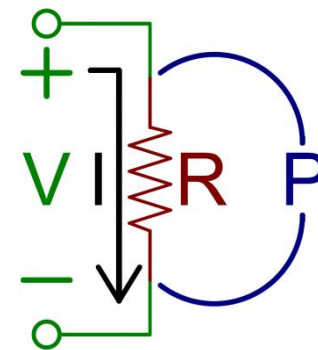
$$P = I \times V = 9V \times 0.9A = 8.1W$$



$$P = I^2 \times R$$

$$P = \frac{V^2}{R}$$


$$P = VI$$

Electrical Power & Energy

- **Electrical Energy**

- is the ability of an electrical circuit to produce work by creating an action. This action can take many forms, such as thermal, electromagnetic, mechanical, electrical, etc.
- Energy absorbed or supplied by an element from time t_0 to time $t > t_0$
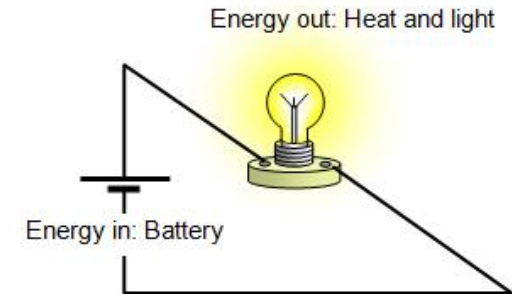
$$W = W(t_0, t) = \int_{t_0}^t p(\tau) d\tau = \int_{t_0}^t v(\tau) i(\tau) d\tau$$



- **Example**

- A 100 Watt light bulb is illuminated on for one hour only. How many joules of electrical energy have been used by the lamp.

$$\text{Electrical Energy} = \text{Power} \times \text{Time}$$

$$\text{Electrical Energy} = 100 \times (60 \times 60)$$

$$W = 360,000 \text{ joules (360 kJ)}$$

- **Example**

- How much energy does a 1200 W dishwasher use when it runs for 30 minutes (1800s)?

$$\text{Electrical Energy} = \text{Power} \times \text{Time}$$

$$\text{Electrical Energy} = 1200 \times (30 \times 60)$$


$$W = 2160,000 \text{ joules (2160 kJ) (2.16 MJ)}$$

Classification of Circuit Components

- One common classification for circuit components is to group them in two major groups:
 - 1) Passive components or passive elements
Components or elements that absorb power.
 - 2) Active components or active elements
Components that are not passive! that is, components that deliver power.

Passive Sign Convention

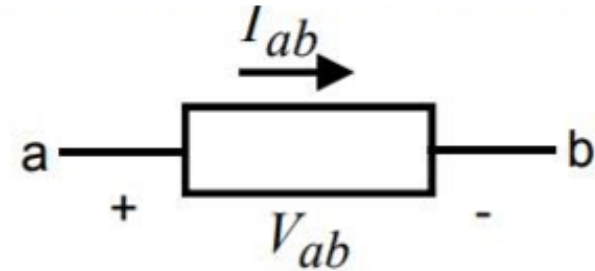
- For calculating absorbed power: The power absorbed by any circuit element with terminals A and B is equal to the voltage drop from A to B multiplied by the current through the element from A to B, i.e., $P = V_{ab} \times I_{ab}$



- With this convention if $P \geq 0$, then the element is absorbing (consuming) power. Otherwise (i.e., $P < 0$) is absorbing negative power or actually generating (delivering) power.

Passive Sign Convention

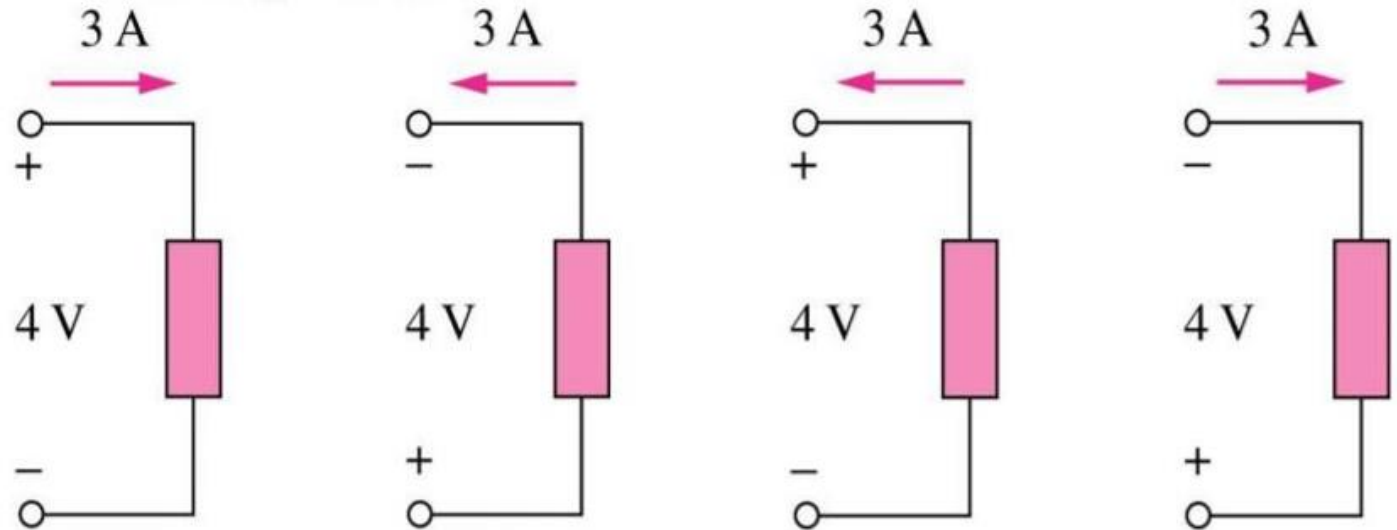- Calculate the power absorbed or supplied by each of the following elements:



Assign polarities to all passive elements (resistors and other loads); for passive elements, current always flows into the positive terminal.

Compute the power dissipated by each element according to the following rule: If positive current flows into the positive terminal of an element, then the power dissipated is positive (i.e., the element absorbs power); if the current leaves the positive terminal of an element, then the power dissipated is negative (i.e., the element delivers power).

Example


- Find: Power dissipated or generated by each element.

$$P_B = -v_B \times i = -12 \text{ V} \times 0.1 \text{ A} = -1.2 \text{ W}$$

- that is, the battery generates 1.2 watts (W).
- The power dissipated by the two loads will be a positive quantity in both cases, since current flows from plus to minus:



$$P_1 = v_1 \times i = 8 \text{ V} \times 0.1 \text{ A} = 0.8 \text{ W}$$
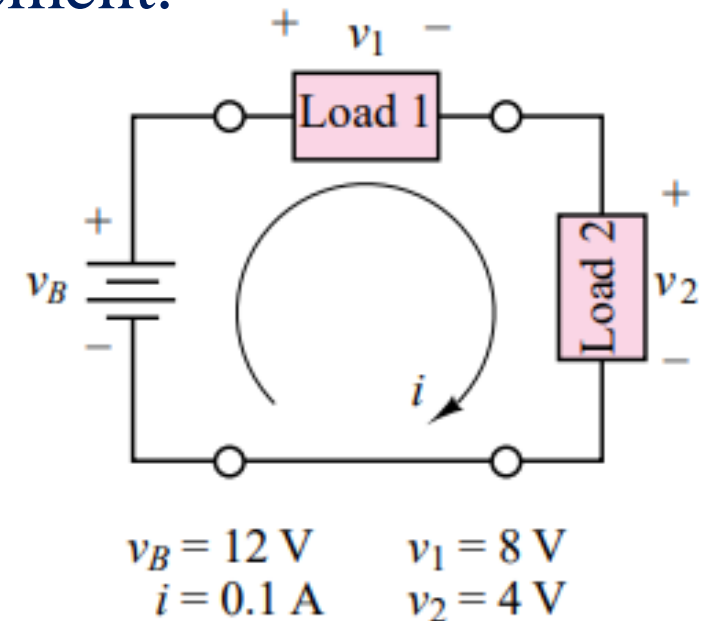
$$P_2 = v_2 \times i = 4 \text{ V} \times 0.1 \text{ A} = 0.4 \text{ W}$$



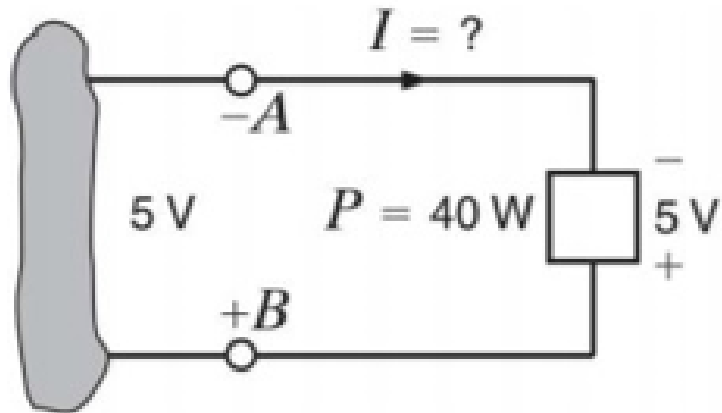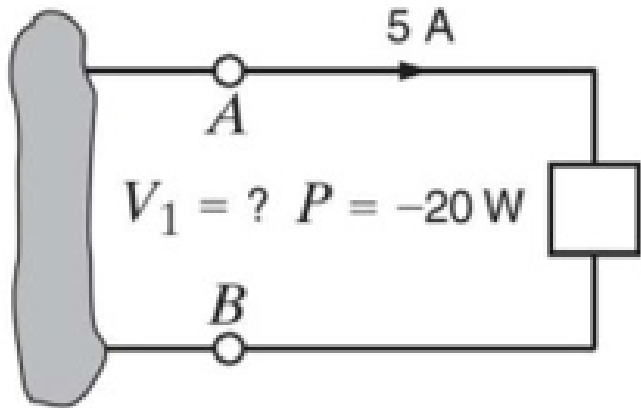
Example

- Determine the unknown voltage or the unknown current.




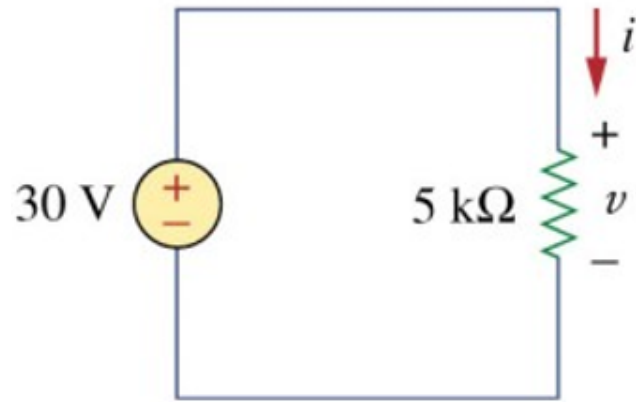Example

In the circuit shown, calculate the current (i), the conductance (G) and power (p) dissipated in the load (resistor).



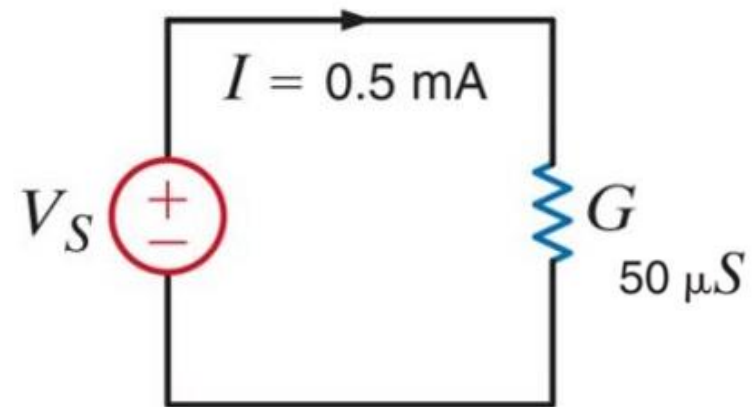- Given the following circuit, find the value of the voltage source and the power absorbed by the resistance.



Example

- Determine which components are absorbing power and which are delivering power. Is conservation of power satisfied? Explain your answer.

A supplies $(12\text{ V})(5\text{ A}) = 60\text{ W}$

B supplies $(3\text{ V})(5\text{ A}) = 15\text{ W}$

C absorbs $(5\text{ V})(5\text{ A}) = 25\text{ W}$


D absorbs $(10\text{ V})(3\text{ A}) = 30\text{ W}$

E absorbs $(10\text{ V})(2\text{ A}) = 20\text{ W}$

Total power supplied = $60\text{ W} + 15\text{ W} = 75\text{ W}$


Total power absorbed = $25\text{ W} + 30\text{ W} + 20\text{ W} = 75\text{ W}$

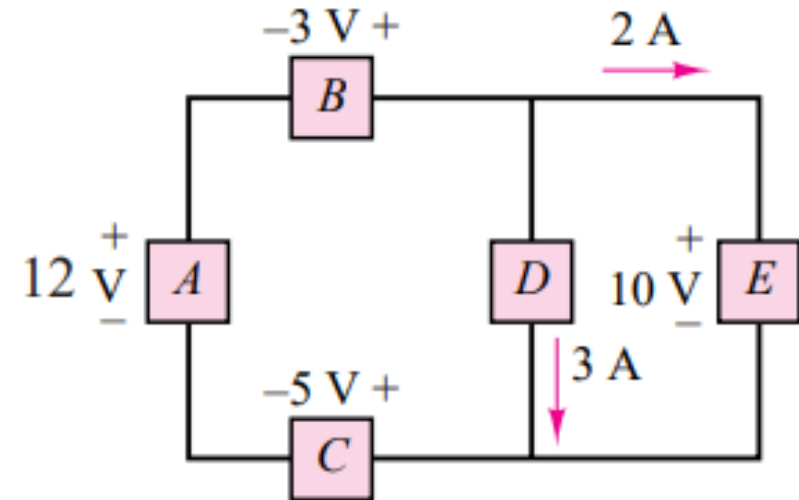Total power supplied = Total power absorbed, so conservation of power is satisfied



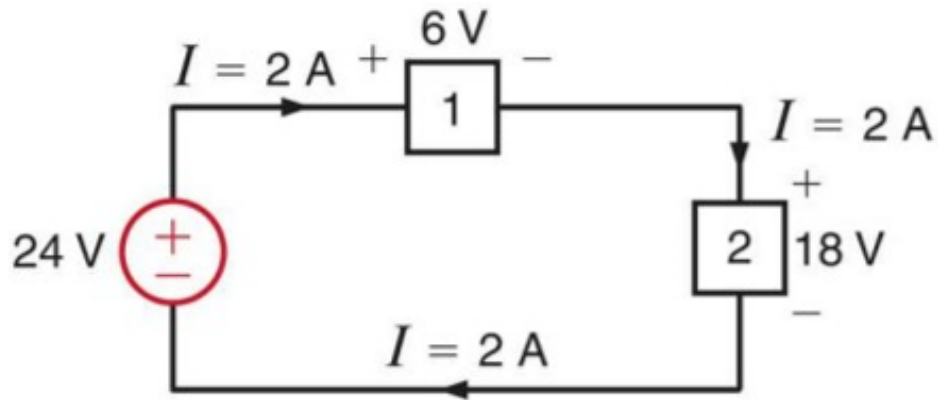Example



- Determine the power absorbed or supplied by the elements of the following network:



A resistor absorbs an instantaneous power of $p=20\cos^2 t$ mW when connected to a voltage source $v=10\cos t$ V. Find i and R .

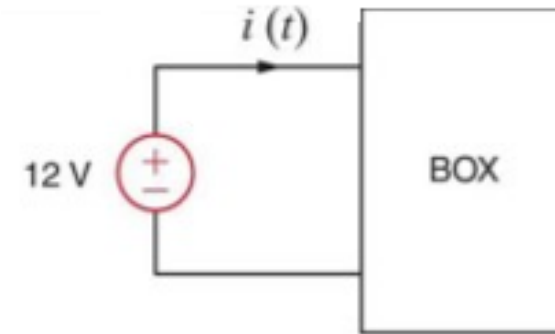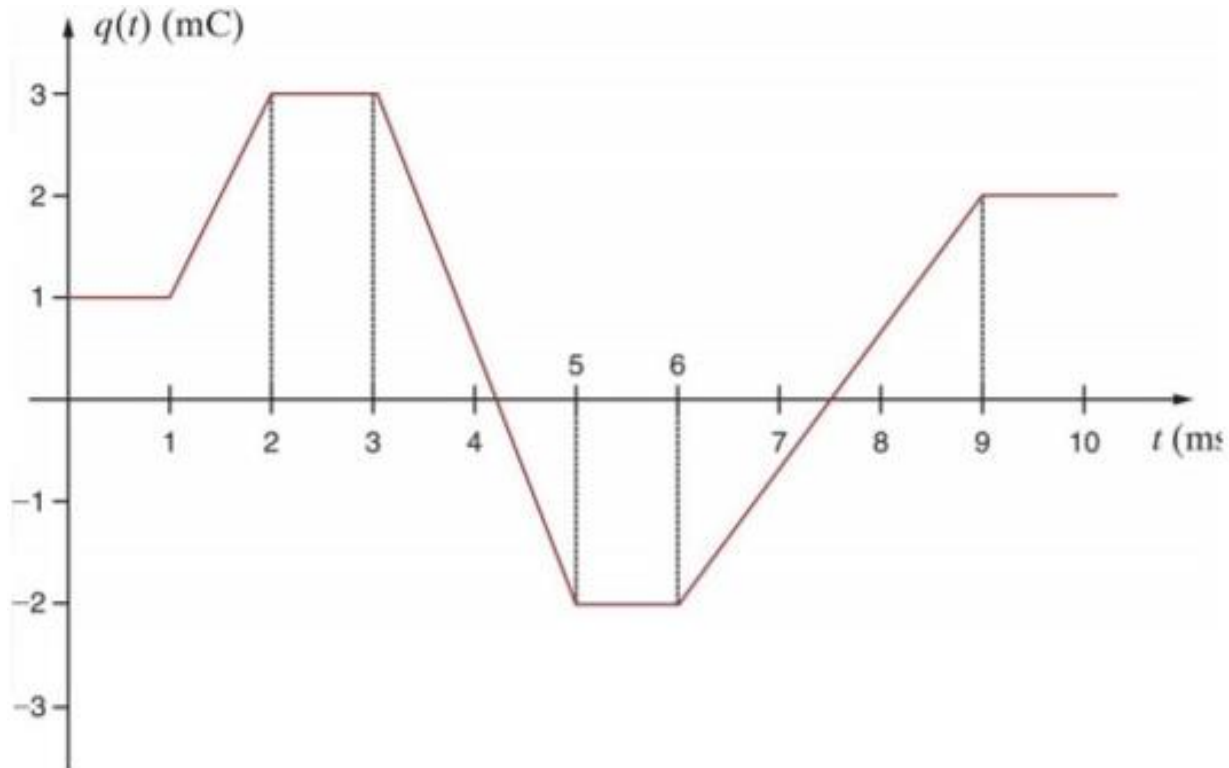Example

- The charge that enters the BOX is shown below. Calculate and sketch the current flowing into the BOX and the power absorbed by the BOX between 0 and 10 milliseconds.



Example

- A third-generation iPod® with a 630 mAh Lithium-ion battery is to be recharged from a high-power USB port supplying 150 mA of current. At the beginning of the recharge, 7.8 C of charge are stored in the battery. The recharging process halts when the stored charge reaches 35.9 C. How long does it take to recharge the battery?

