
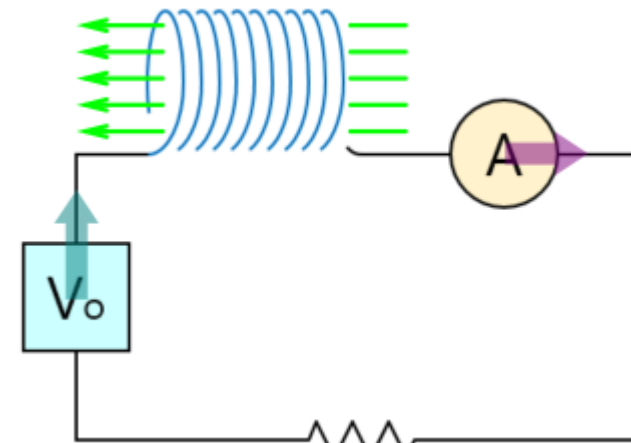
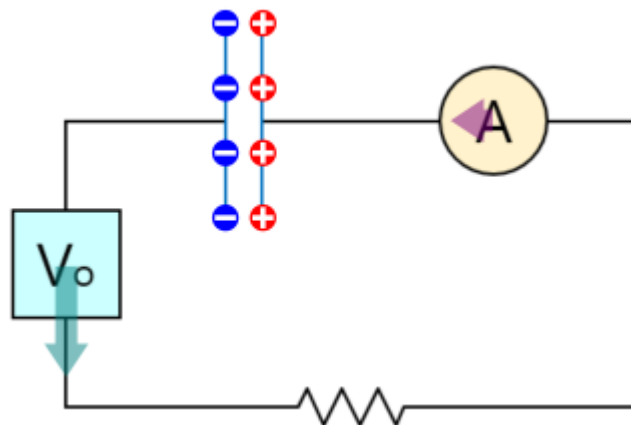
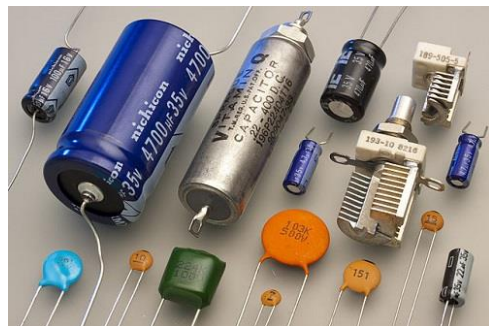
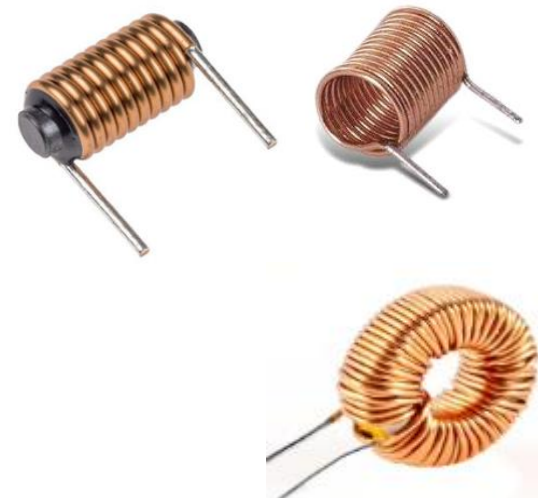
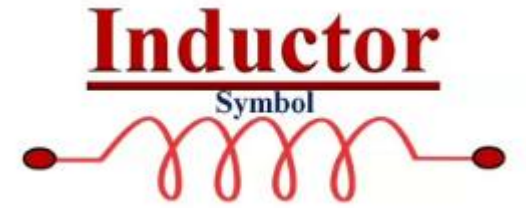
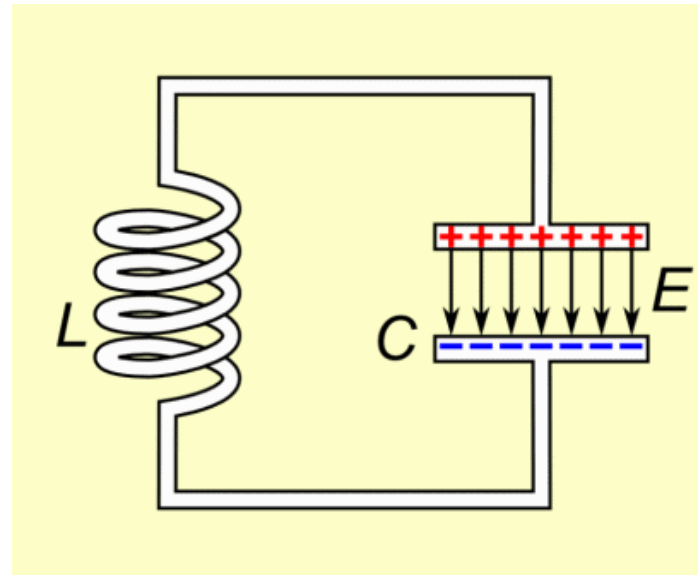


Capacitor

Capacitors and Inductors

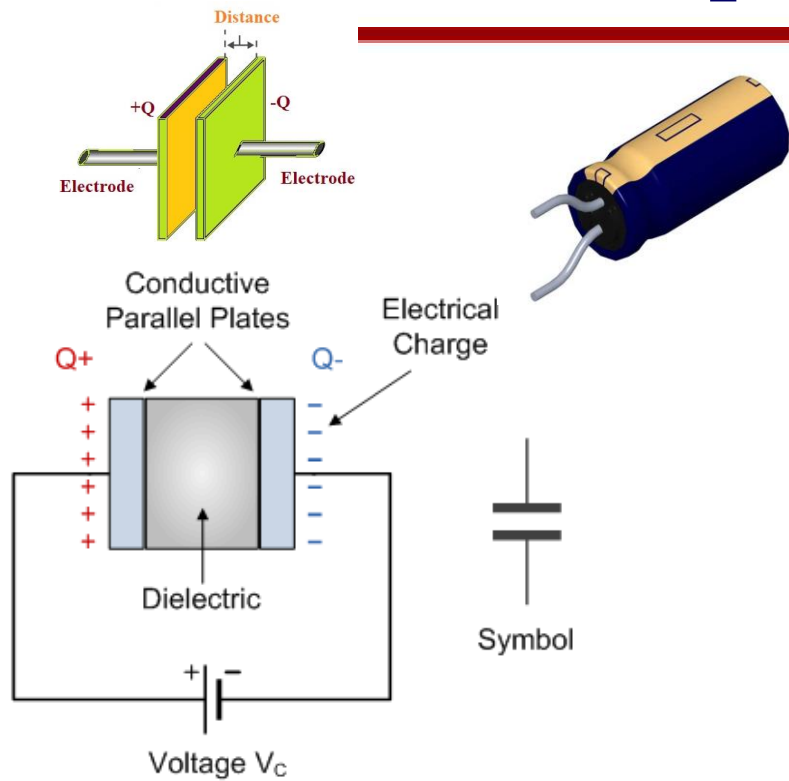

Capacitors and Inductors

- **Passive elements:**

- **Resistors**
- **Capacitors**
- **Inductors**



Resistor



Capacitor



Inductor



Resistor



Capacitor



Inductor

- **Resistors** are passive elements which **dissipate energy** only.
- Two important **passive** linear circuit elements:
- Capacitors and inductors do not dissipate but **store energy**, which can be retrieved at a later time. Capacitors and inductors are called **energy storage elements**.



➤ **Capacitors: Series and Parallel Capacitors**

➤ **Inductors: Series and Parallel Inductors**


1- Capacitors

- A capacitor is a passive element designed to store energy in its electric field.
- A capacitor consists of two conducting plates separated by an insulator (or dielectric).
- **Capacitance C** is the ratio of the charge q on one plate of a capacitor to the voltage difference v between the two plates, measured in farads (F).
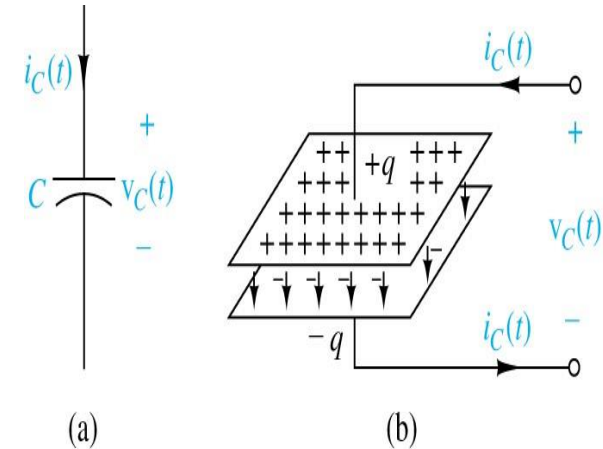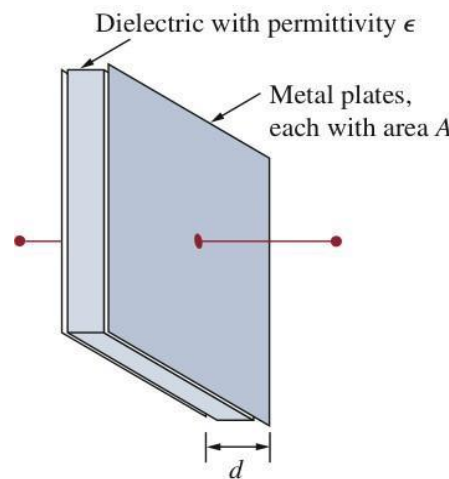
$$q = C v \quad C = \frac{\epsilon A}{d}$$





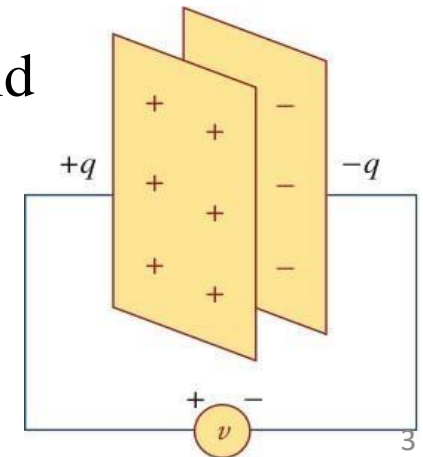- The plate charge increases as the voltage increases. Also, the electric field intensity between two plates increases.
- Where ϵ is the permittivity of the dielectric material between the plates, A is the surface area of each plate, d is the distance between the plates.
- Unit: F, pF (10^{-12}), nF (10^{-9}), and μF (10^{-6}).



1- Capacitors

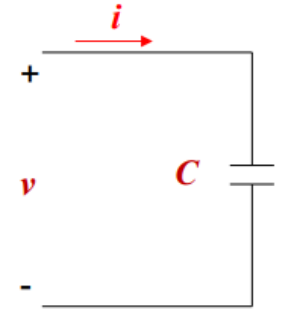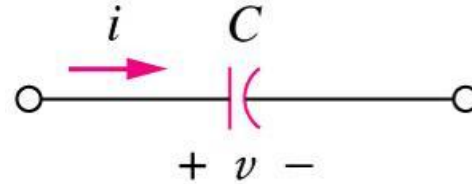
- If i is flowing into the +ve terminal of C
 - **Charging** $\Rightarrow i$ is +ve
 - **Discharging** $\Rightarrow i$ is -ve



- The current-voltage relationship of capacitor according to above convention is

$$i = C \frac{d v}{d t} \quad \text{and} \quad v = \frac{1}{C} \int_{t_0}^t i d t + v(t_0)$$

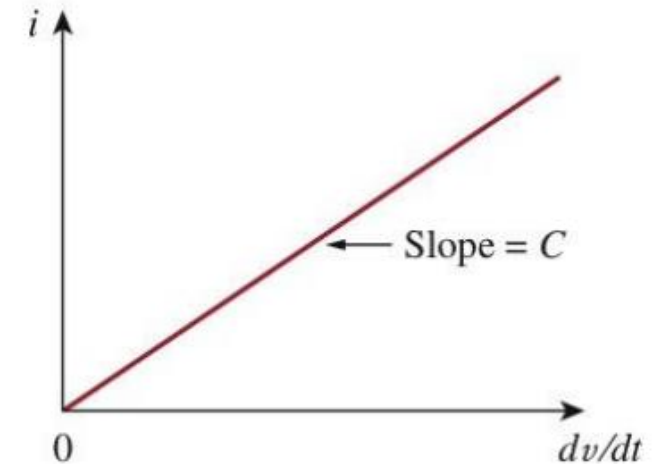
- The **energy**, w , stored in the capacitor is: $w = \frac{1}{2} C v^2$
- A capacitor is
 - an **open circuit** to dc ($dv/dt = 0$).
 - its voltage **cannot change abruptly**.



1- Capacitors

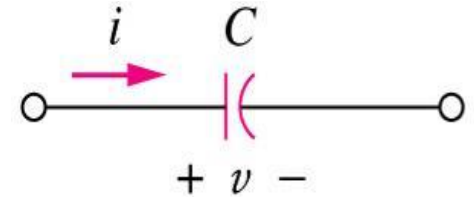Example 1

- Calculate the charge stored on a 3-pF capacitor with 20 V across it.
- Find the energy stored in the capacitor.



$$q = Cv$$

$$q = 3 \times 10^{-12} \times 20 = 60 \text{ pC}$$

$$w = \frac{1}{2} Cv^2$$

$$w = \frac{1}{2} \times 3 \times 10^{-12} \times 400 = 600 \text{ pJ}$$

Answer:

$$q = 60 \text{ pC}$$

$$w = 600 \text{ pJ}$$


1- Capacitors

Example 2

The current through a 100- μF capacitor is

$$i(t) = 50 \sin(120 \pi t) \text{ mA.}$$

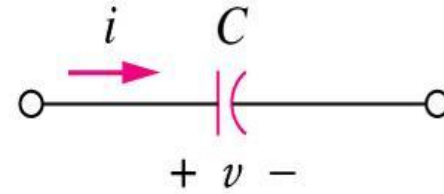Calculate the voltage across it at $t = 1 \text{ ms}$ and $t = 5 \text{ ms}$. Take $v(0) = 0$.



Answer:


$$v(1\text{ms}) = 93.14 \text{ mV}$$

$$v(5\text{ms}) = 1.74 \text{ V}$$

1- Capacitors

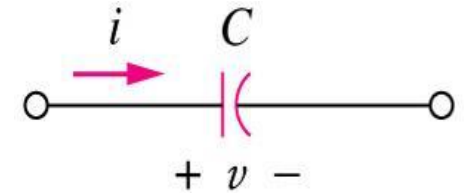Example 3

The voltage across a 5- μF capacitor is: $v(t) = 10\cos(6000t)$ V.
Calculate the current through it.



$$i = C \frac{dv}{dt}$$

$$i = C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt} (10 \cos 6000t)$$


$$i = -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t$$

$$i = -0.3 \sin 6000t \text{ A}$$

1- Capacitors

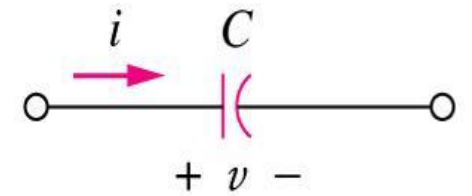Example 4

Determine the voltage across a 2- μF capacitor if the current through it is: $i(t) = 6e^{-3000t}$ A. Assume that the initial capacitor voltage is zero.



$$v = \frac{1}{C} \int_0^t i dt + v(0) \text{ and } v(0) = 0,$$


$$v = \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000t} dt \cdot 10^{-3} = \frac{3 \times 10^3}{-3000} e^{-3000t} \Big|_0^t$$

$$v = (1 - e^{-3000t}) \text{V}$$

1- Capacitors

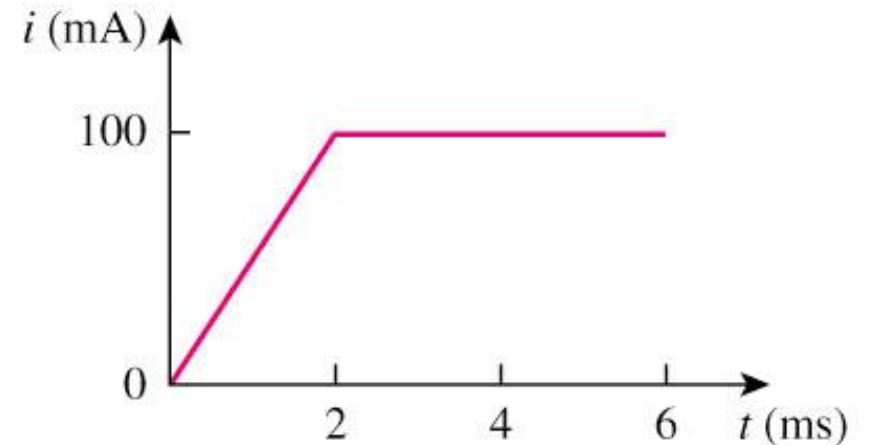Exercise

An initially uncharged 1-mF capacitor has the current shown below across it. Calculate the voltage across it at $t = 2 \text{ ms}$ and $t = 5 \text{ ms}$.



Answer:


$$v(2\text{ms}) = 100 \text{ mV}$$

$$v(5\text{ms}) = 500 \text{ mV}$$

1- Capacitors

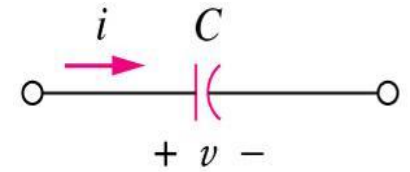Example 5

Determine the current through a 200- μF capacitor whose voltage is shown below.



Solution



The voltage waveform can be described mathematically as:

$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

Since $i = C \, dv/dt$ and $C = 200 \, \mu\text{F}$, we take the derivative of $v(t)$ to obtain:

$$i(t) = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

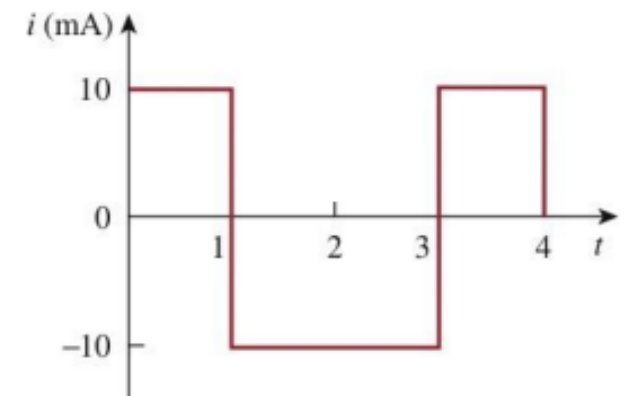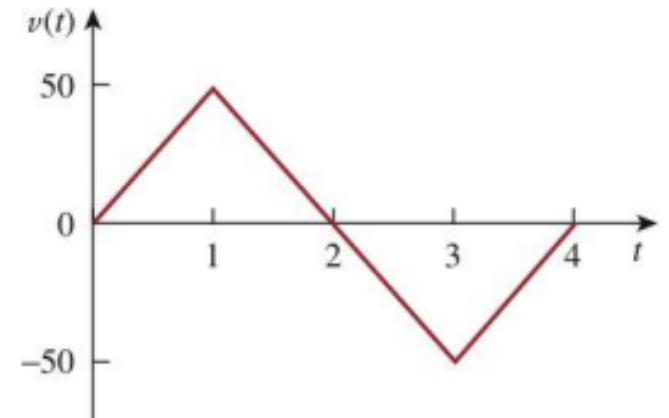
$$i(t) = \begin{cases} 10\text{mA} & 0 < t < 1 \\ -10\text{mA} & 1 < t < 3 \\ 10\text{mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$



1- Capacitors

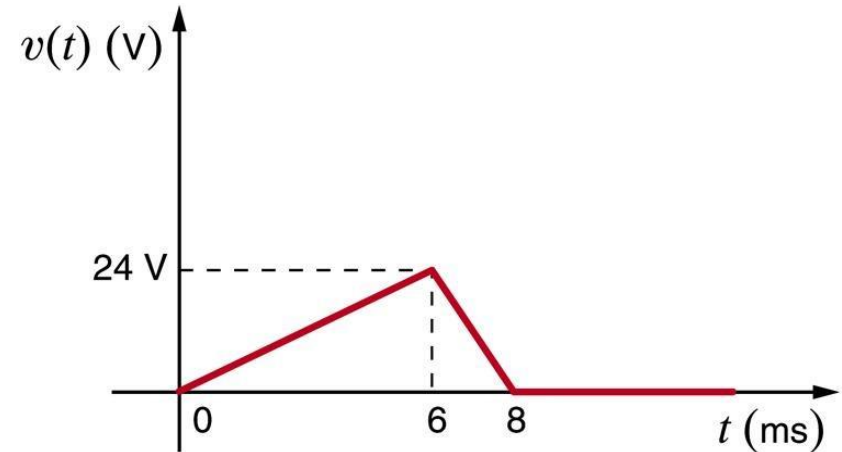Exercise

The voltage across a $5\text{-}\mu\text{F}$ capacitor is given below. Determine the current of the capacitor.



1- Capacitors

Exercise: Obtain the energy stored in each capacitor in circuit below under dc condition.

Solution



Under **dc condition**, we replace each capacitor with an **open circuit**. By current division,

$$\therefore v_1 = 2000i = 4\text{ V}, \quad v_2 = 4000i = 8\text{ V}$$

$$i = \frac{3}{3+2+4}(6\text{ mA}) = 2\text{ mA}$$

$$\therefore w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} (2 \times 10^{-3}) (4)^2 = 16\text{ mJ}$$

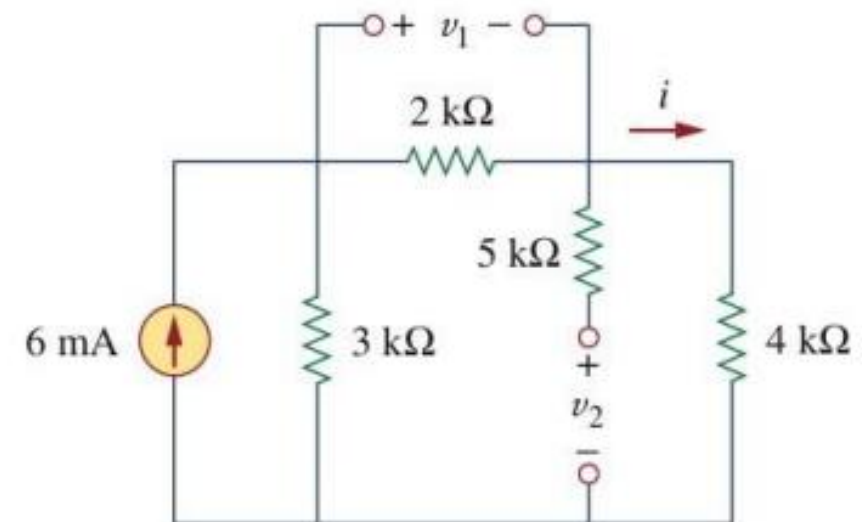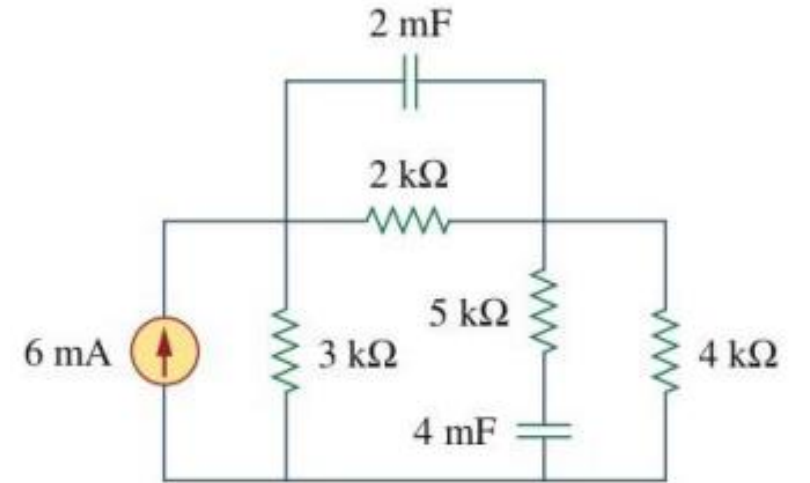
$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} (4 \times 10^{-3}) (8)^2 = 128\text{ mJ}$$




1- Capacitors

Series and Parallel Capacitors

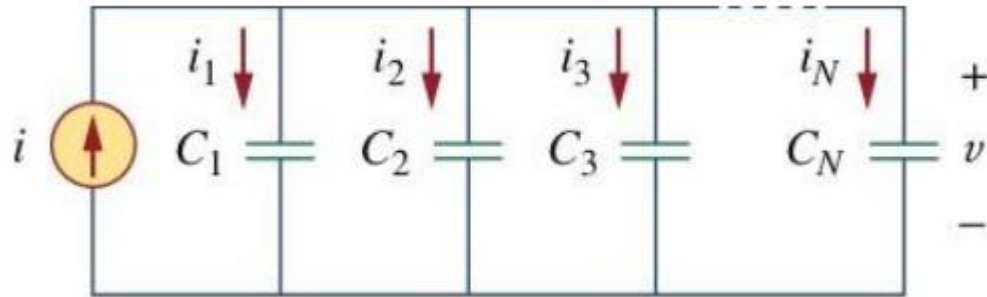
- The equivalent capacitance of N **parallel-connected** capacitors is the sum of the individual capacitances.


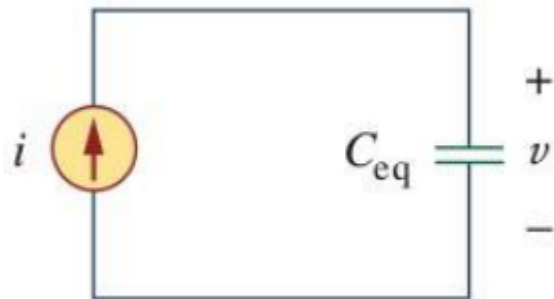
$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$




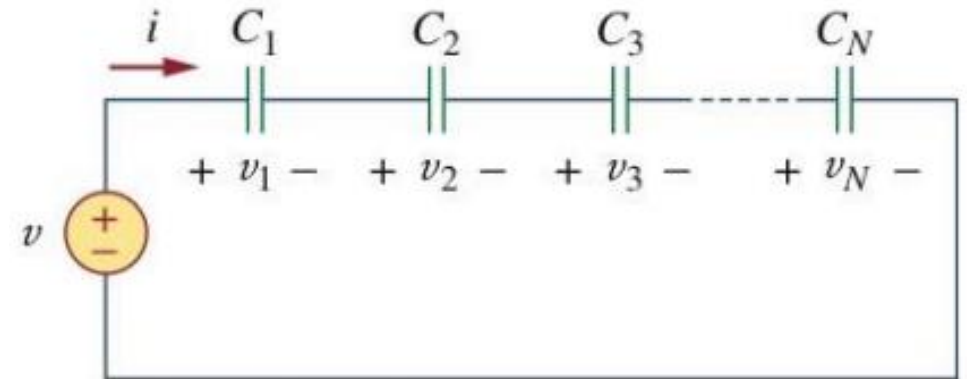- The equivalent capacitance of N **series-connected** capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

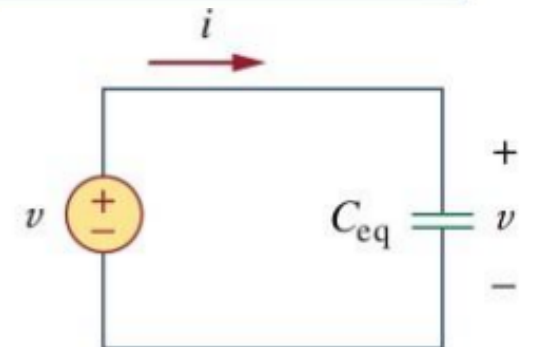For $N=2$:
$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$




1- Capacitors

Series and Parallel Capacitors

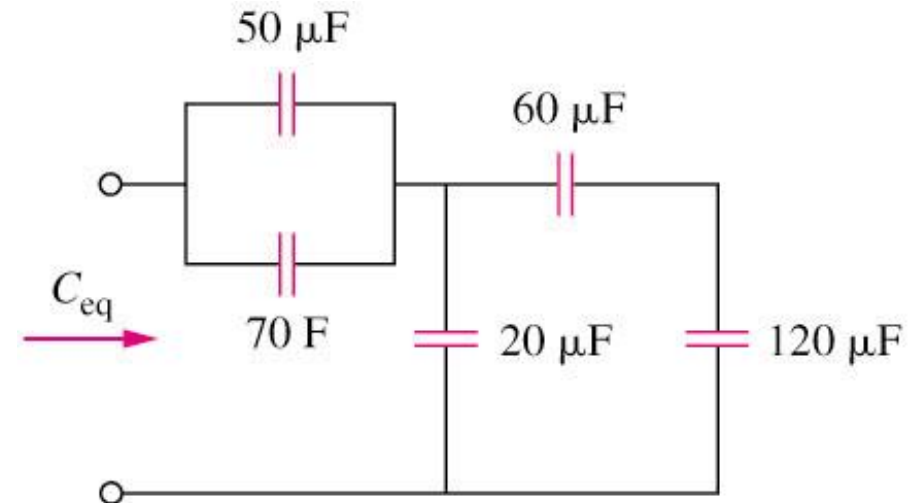Example 6

Find the equivalent capacitance seen at the terminals of the circuit in the circuit shown below:



Answer:

$$C_{eq} = \underline{40 \mu\text{F}}$$

1- Capacitors

Series and Parallel Capacitors

Example 7: Find the equivalent capacitance seen between terminals a and b of the circuit in the figure below.

Solution

- $20\mu\text{F}$ and $5\mu\text{F}$ capacitors are in series:


$$\therefore \frac{20 \times 5}{20 + 5} = 4\mu\text{F}$$

- $4\mu\text{F}$ capacitor is in parallel with the $6\mu\text{F}$ and $20\mu\text{F}$ capacitors

$$\therefore 4 + 6 + 20 = 30\mu\text{F}$$

- $30\mu\text{F}$ capacitor is in series with the $60\mu\text{F}$ capacitor.
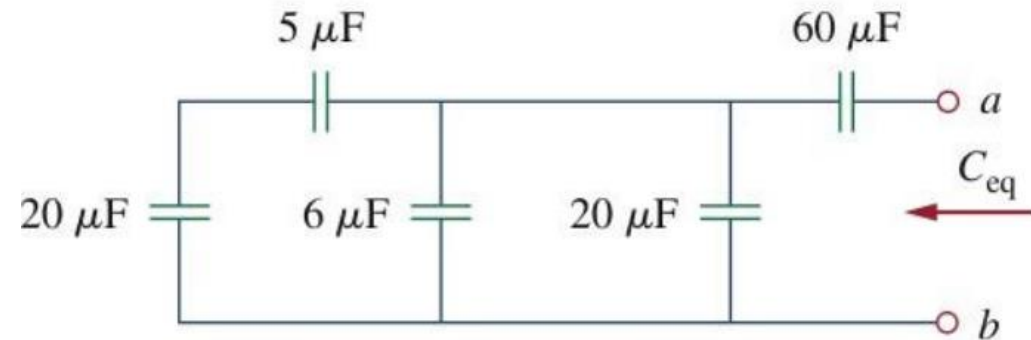
$$C_{eq} = \frac{30 \times 60}{30 + 60} \mu\text{F} = 20\mu\text{F}$$




1- Capacitors


Series and Parallel Capacitors

Example 8: For the circuit given below, find the voltage across each capacitor.

Solution

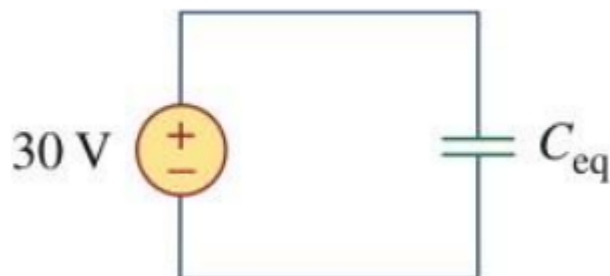
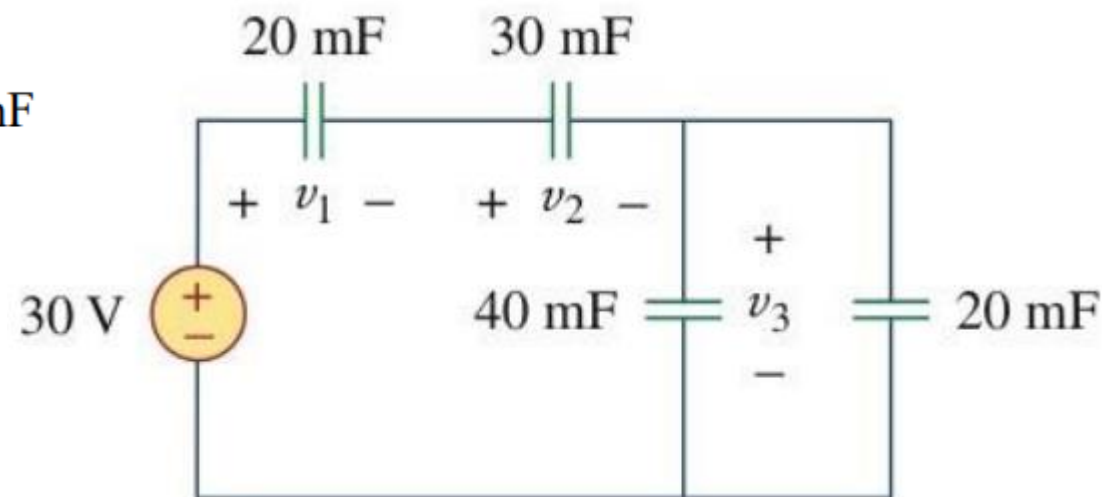
$$\therefore C_{eq} = \frac{1}{\frac{1}{(40+20)} + \frac{1}{30} + \frac{1}{20}} \text{ mF} = 10 \text{ mF}$$



Total charge

$$q = C_{eq} v = 10 \times 10^{-3} \times 30 = 0.3 \text{ C}$$

This is the charge on the 20 mF and 30 mF capacitors, because they are in series with the 30 V source. (A crude way to see this is to imagine that charge acts like current, since $i = dq/dt$)

Therefore,

$$v_1 = \frac{q}{C_1} = \frac{0.3}{20 \times 10^{-3}} = 15 \text{ V},$$

$$v_2 = \frac{q}{C_2} = \frac{0.3}{30 \times 10^{-3}} = 10 \text{ V}$$

1- Capacitors

Series and Parallel Capacitors



Example 8: For the circuit given below, find the voltage across each capacitor.

Having determined v_1 and v_2 ,
we can use KVL to determine v_3 by

$$v_3 = 30 - v_1 - v_2 = 5V$$

Alternatively, since the 40-mF and 20-mF capacitors
are in parallel, they have the same voltage v_3 and
their combined capacitance is $40+20=60\text{mF}$.
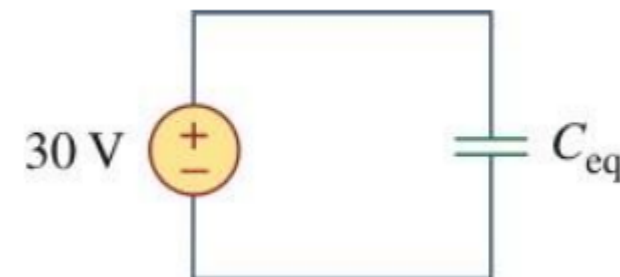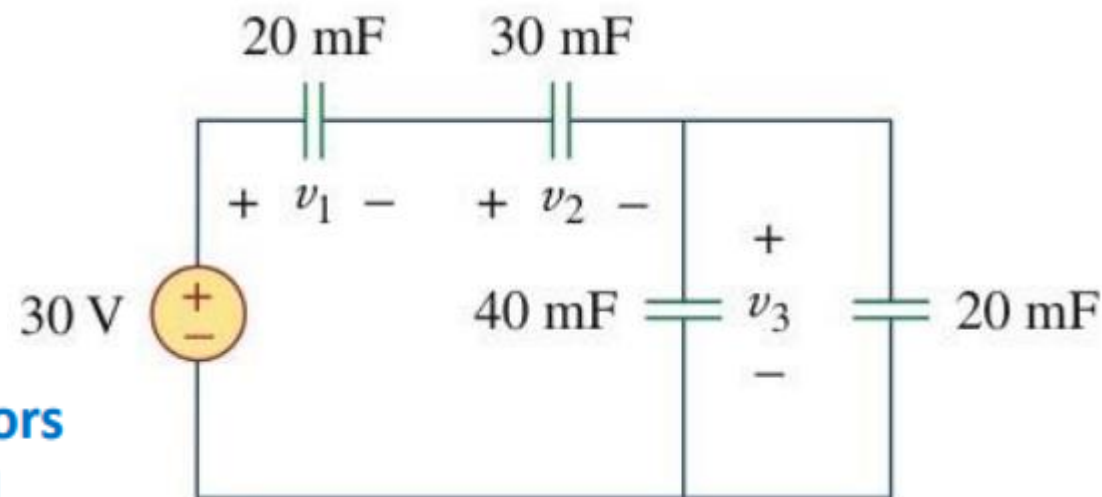
$$\therefore v_3 = \frac{q}{60\text{mF}} = \frac{0.3}{60 \times 10^{-3}} = 5V$$




1- Capacitors

Series and Parallel Capacitors

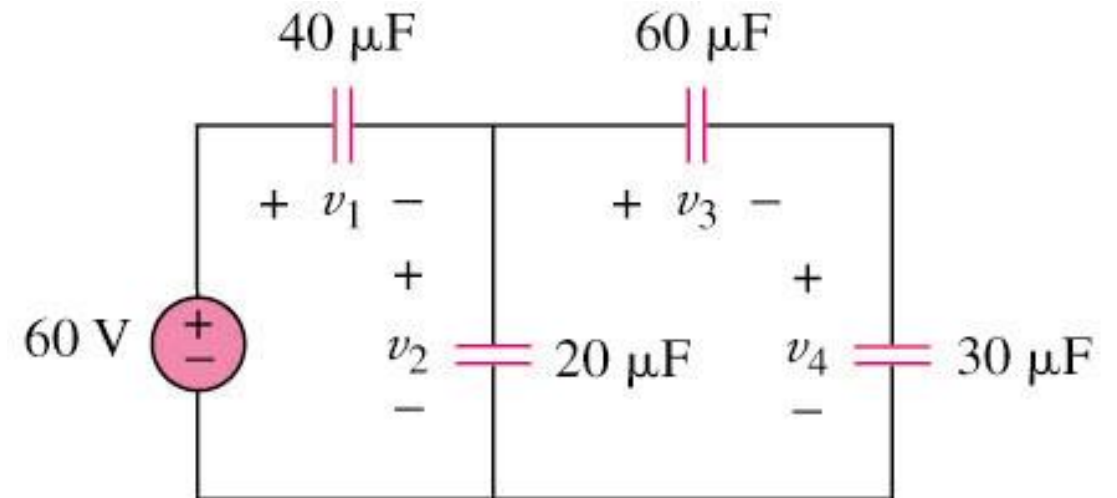Example 9

Find the voltage across each of the capacitors in the circuit shown below:



Answer:

$$v_1 = 30\text{V}, \quad v_2 = 30\text{V}$$


$$v_3 = 10\text{V}, \quad v_4 = 20\text{V}$$

1- Capacitors

Series and Parallel Capacitors

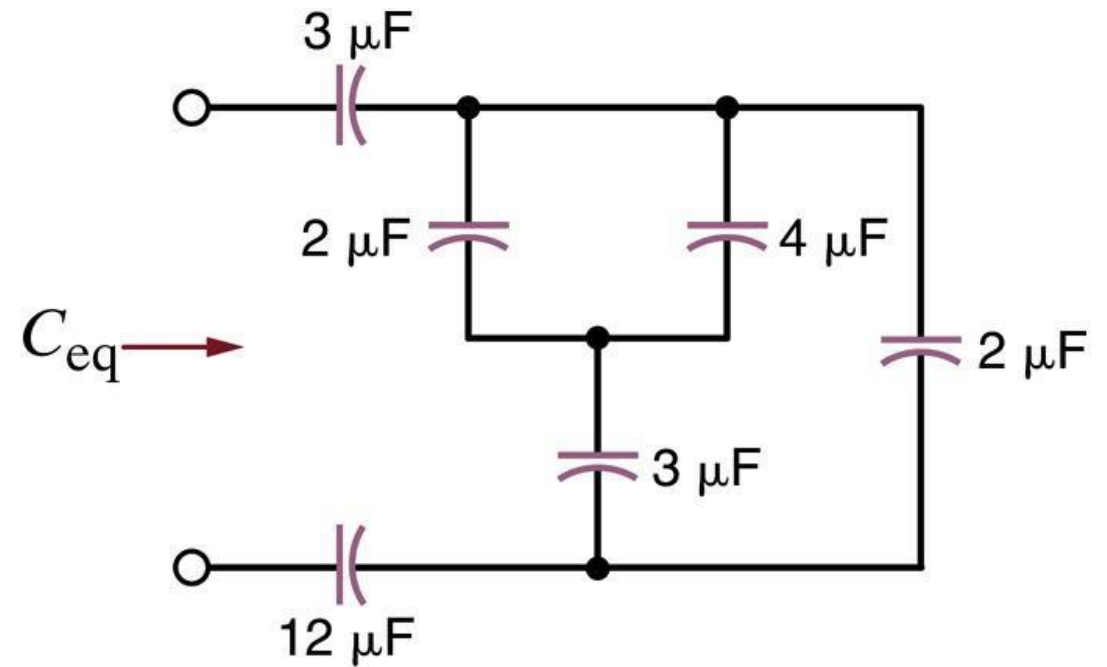Exercise

Compute the equivalent capacitance of the following network:



2- Inductors

- An inductor is a passive element designed to store energy in its magnetic field.
- An inductor consists of a coil of conducting wire.
- Inductance is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).

$$v = L \frac{d i}{d t} \quad \text{and} \quad L = \frac{N^2 \mu A}{l}$$

$$\mu = \mu_r \mu_0$$



$$\mu_0 = 4\pi \times 10^{-7} \text{ (H/m)}$$

N : number of turns.

l : length.

A : cross – sectional area.

μ : permeability of the core

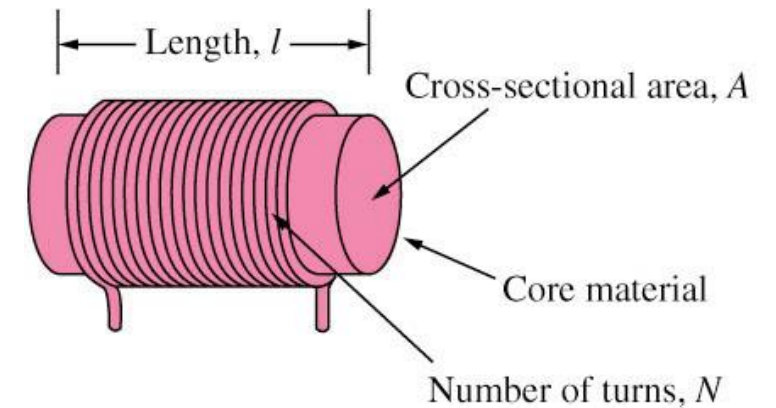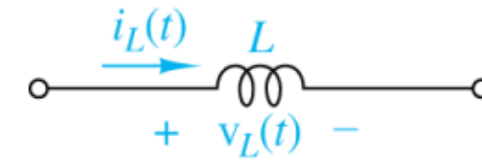


- The unit of inductors is Henry (H), mH (10^{-3}), and μ H (10^{-6}).

2- Inductors


- The current-voltage relationship of an inductor:
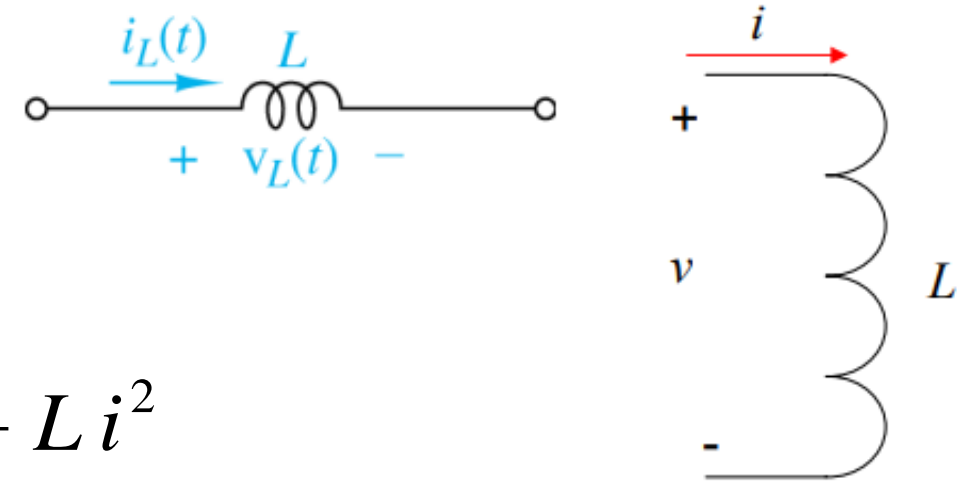
$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$



- The energy w stored by an inductor is: $w = \frac{1}{2} L i^2$

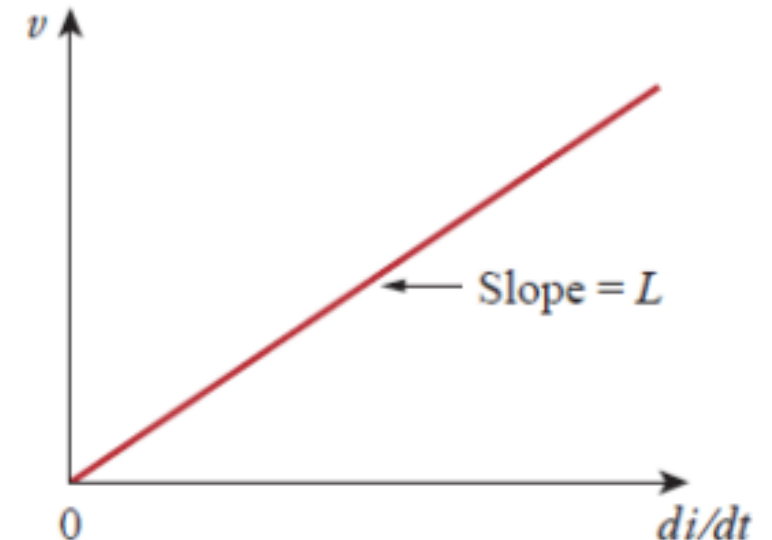- An inductor acts like a short circuit to dc ($di/dt = 0$) and its current cannot change abruptly.




voltage-current relationship of an inductor

2- Inductors

Example 10

The current through a 0.1-H inductor is $i(t) = 10te^{-5t}$ A. Find the voltage across the inductor and the energy stored in it.

Solution

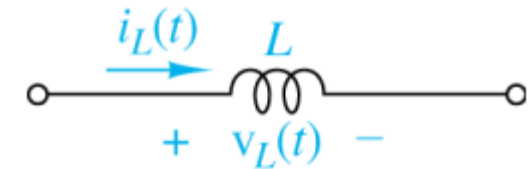

Since $v = L \frac{di}{dt}$ and $L = 0.1\text{H}$,

$$v = 0.1 \frac{d}{dt}(10te^{-5t}) = e^{-5t} + t(-5)e^{-5t} = e^{-5t}(1 - 5t)\text{V}$$


The energy stored is

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(0.1)100t^2e^{-10t} = 5t^2e^{-10t}\text{J}$$

2- Inductors

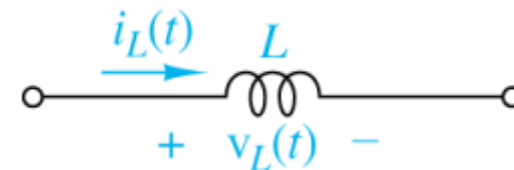Example 11

Find the current through a 5-H inductor if the voltage across it is:



Also find the energy stored within $0 < t < 5$ s. Assume $i(0)=0$.

$$v(t) = \begin{cases} 30t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$

Solution

Since $i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$ and $L = 5$ H.

$$i = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A}$$

Solution

The power $p = vi = 60t^5$, and the energy stored is then

$$w = \int p dt = \int_0^5 60t^5 dt = 60 \left. \frac{t^6}{6} \right|_0^5 = 156.25 \text{ kJ}$$

Alternatively

$$w(5) - w(0) = \frac{1}{2} Li^2(5) - \frac{1}{2} Li(0)$$

$$w = \frac{1}{2} (5)(2 \times 5^3)^2 - 0 = 156.25 \text{ kJ}$$

2- Inductors

Example 12

Consider the circuit below in (a). Under dc conditions, find:



- i , v_C , and i_L .
- the energy stored in the capacitor and inductor.

Solution (a) Under dc condition : capacitor \rightarrow open circuit
inductor \rightarrow short circuit

$$i = i_L = \frac{12}{1+5} = 2A, \quad v_c = 5i = 10V$$

$$(b) \quad w_c = \frac{1}{2} C v_c^2 = \frac{1}{2} (1)(10^2) = 50J,$$
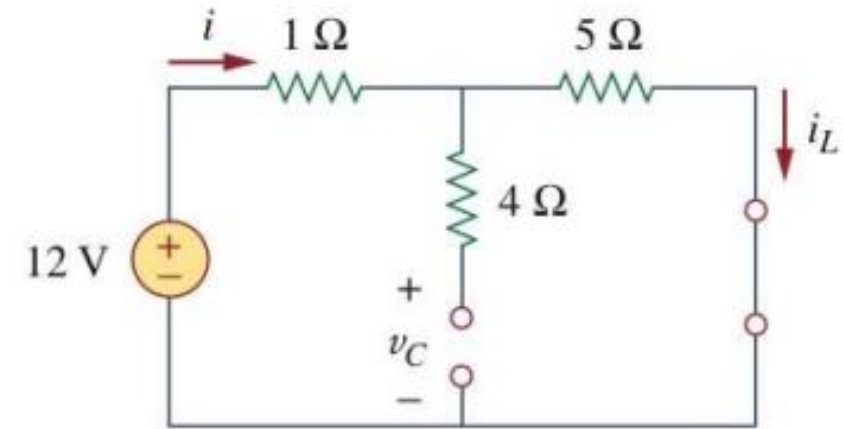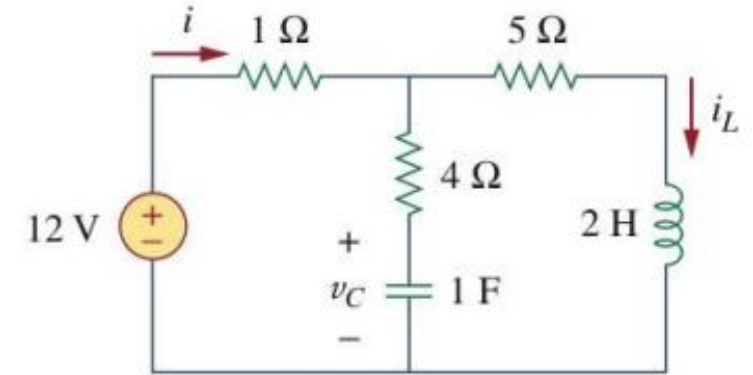
$$w_L = \frac{1}{2} L i^2 = \frac{1}{2} (2)(2^2) = 4J$$




2- Inductors

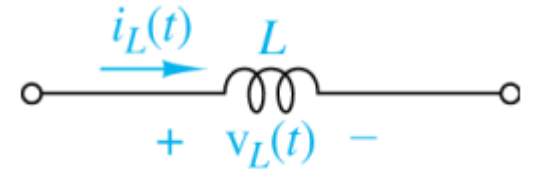Exercise

The terminal voltage of a 2-H inductor is: $v = 10(1-t)$ V

Find the current flowing through it at $t = 4$ s and the energy stored in it within $0 < t < 4$ s. Assume $i(0) = 2$ A.



Answer:



$$i(4s) = -18V$$

$$w(4s) = 320J$$

2- Inductors

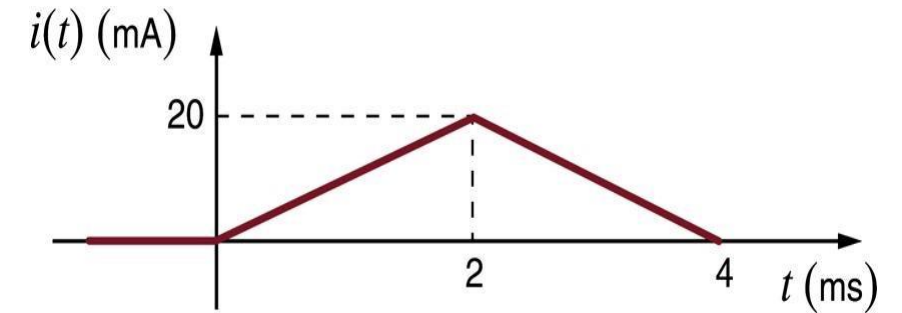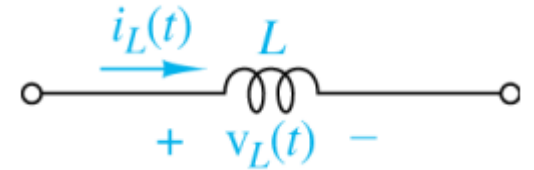Exercise


The current $i(t)$ in a 10-mH inductor has the following waveform. Find the voltage $v(t)$ of the inductor.



2- Inductors

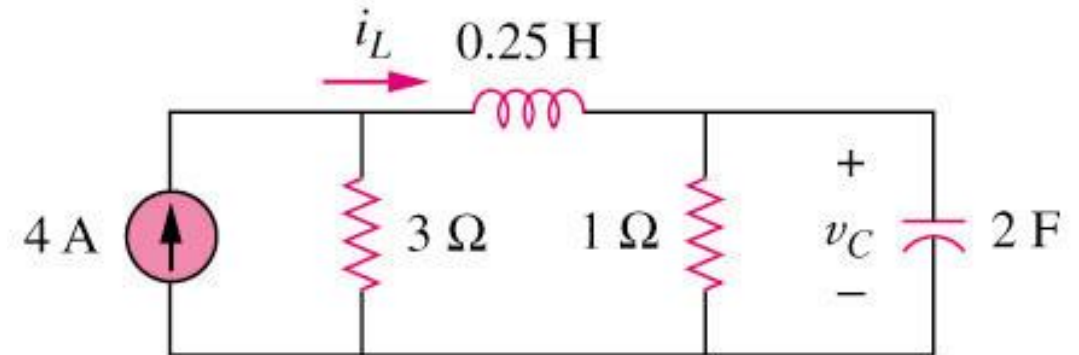Exercise

Determine v_C , i_L , and the energy stored in the capacitor and inductor in the circuit of circuit shown below under dc conditions.




Answer:

$$i_L = 3\text{A}, v_C = 3\text{V}$$


$$w_L = 1.125\text{J}, w_C = 9\text{J}$$

2- Inductors

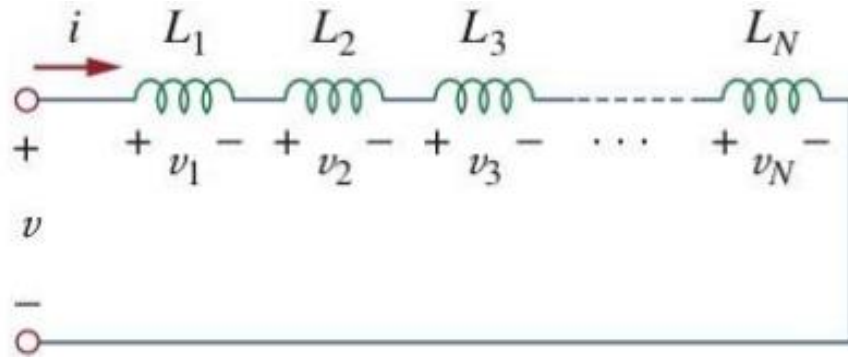
- The equivalent inductance of N **series-connected** inductors is the sum of the individual inductances.



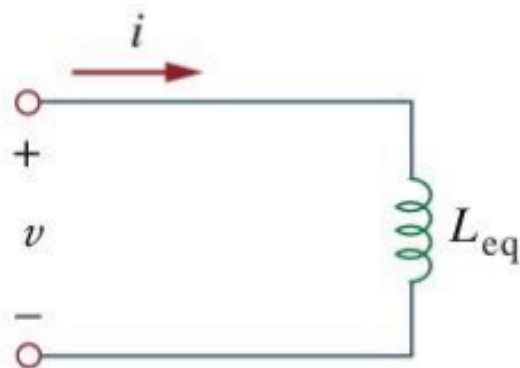
$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



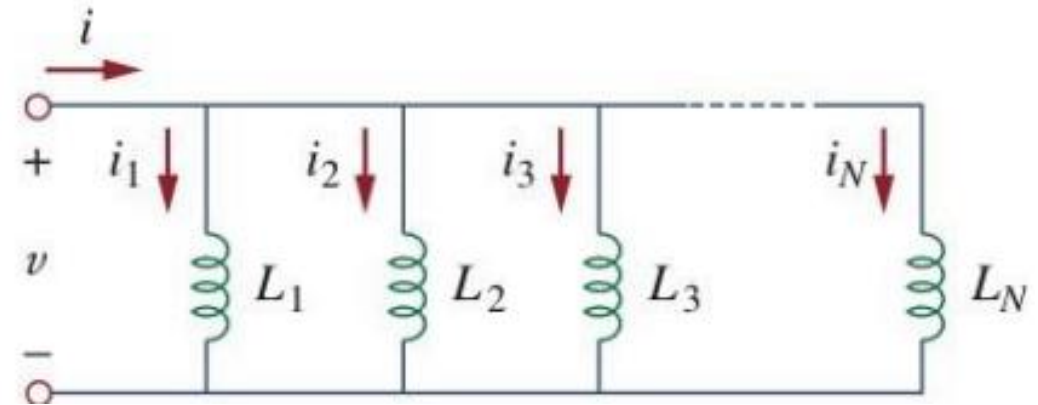- The equivalent capacitance of N **parallel-connected** inductors is the reciprocal of the sum of the reciprocals of the individual inductances.


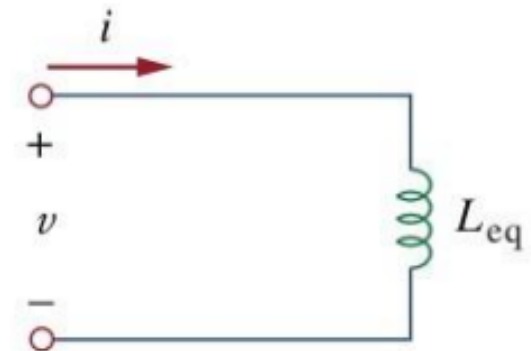
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$



2- Inductors

Series and Parallel Inductors


Example 13: Find the equivalent inductance of the circuit given below.

Solution:

Series: 20H, 12H, 10H \rightarrow 42H

Parallel: $\frac{7 \times 42}{7 + 42} = 6\text{H}$

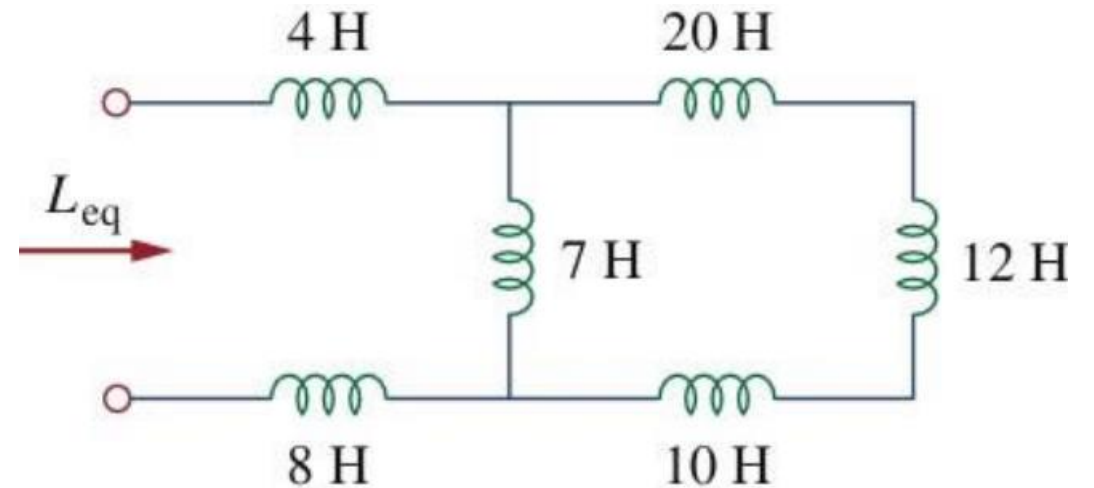$\therefore L_{eq} = 4 + 6 + 8 = 18\text{H}$




2- Inductors

Series and Parallel Inductors

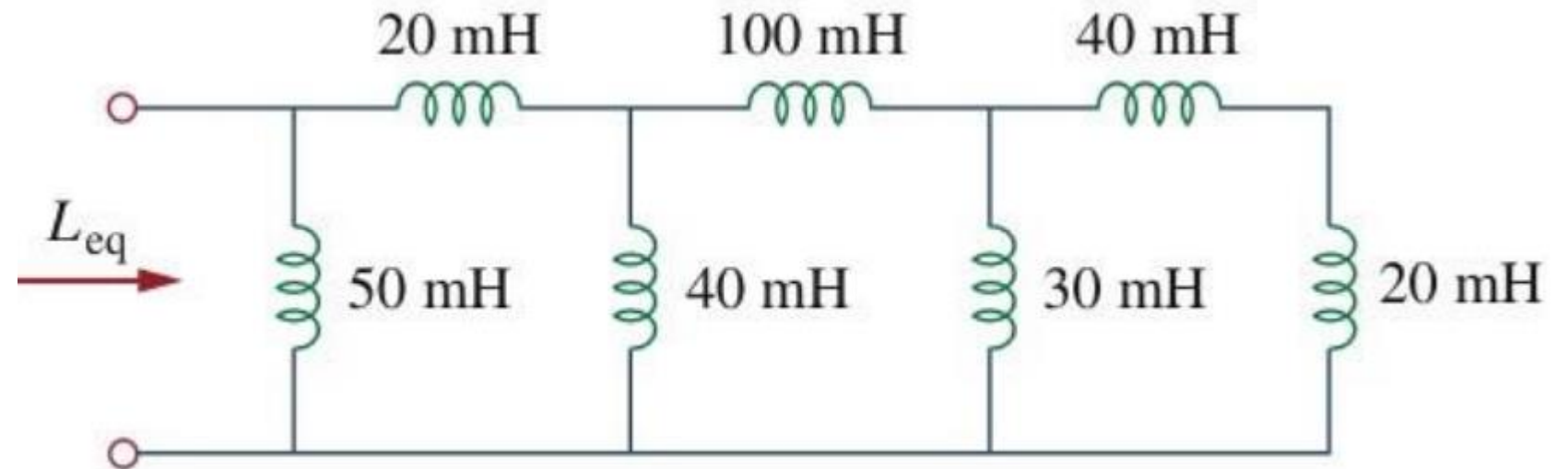Exercise

Calculate the equivalent inductance for the inductive ladder network in the circuit shown below:



Answer:


$$L_{eq} = \underline{25 \text{ mH}}$$

2- Inductors

Series and Parallel Inductors

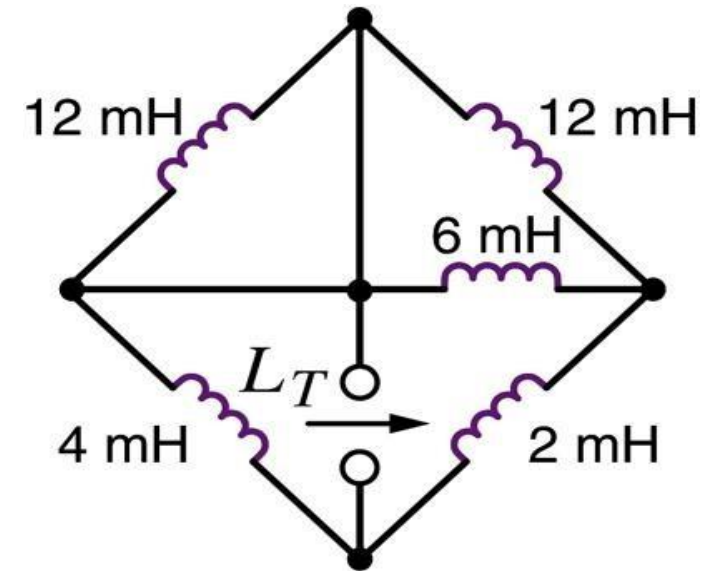Exercise

Find the equivalent inductance (L_T) of the following network:



2- Inductors

Series and Parallel Inductors

Example 14


For the circuit given below, $i(t) = 4(2 - e^{-10t})$ mA.

If, $i_2(0) = -1$ mA,

Find: (a) $i_1(0)$

(b) $v(t)$, $v_1(t)$, and $v_2(t)$;

(c) $i_1(t)$ and $i_2(t)$

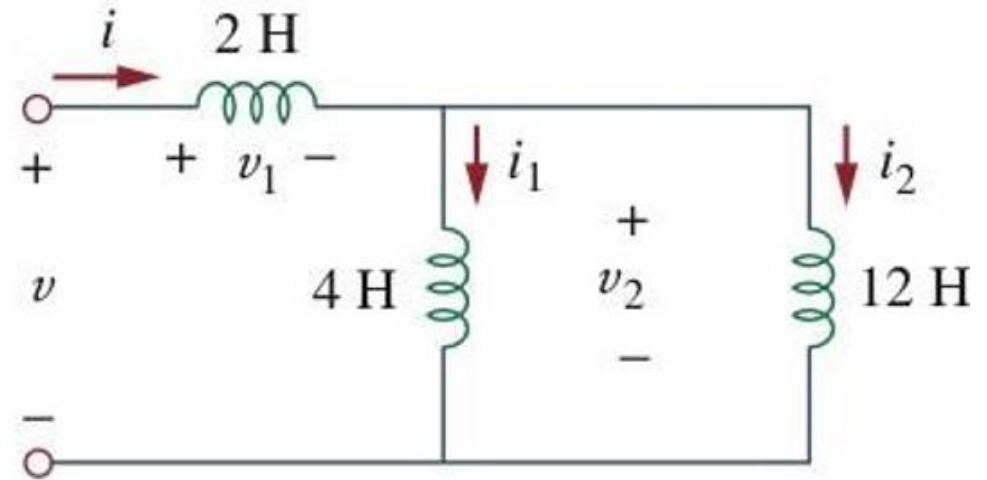

Solution:

$$(a) i(t) = 4(2 - e^{-10t}) \text{ mA} \rightarrow i(0) = 4(2 - 1) = 4 \text{ mA.}$$

$$\therefore i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5 \text{ mA}$$

$$\therefore v(t) = L_{eq} \frac{di}{dt} = 5(4)(-1)(-10)e^{-10t} \text{ mV} = 200e^{-10t} \text{ mV}$$

$$v_1(t) = 2 \frac{di}{dt} = 2(-4)(-10)e^{-10t} \text{ mV} = 80e^{-10t} \text{ mV}$$

$$\therefore v_2(t) = v(t) - v_1(t) = 120e^{-10t} \text{ mV}$$

(b) The equivalent inductance is

$$L_{eq} = 2 + 4 \parallel 12 = 2 + 3 = 5 \text{ H}$$

2- Inductors

Series and Parallel Inductors

Example 14


For the circuit given below, $i(t) = 4(2 - e^{-10t})$ mA.

If, $i_2(0) = -1$ mA,

Find: (a) $i_1(0)$

(b) $v(t)$, $v_1(t)$, and $v_2(t)$;

(c) $i_1(t)$ and $i_2(t)$

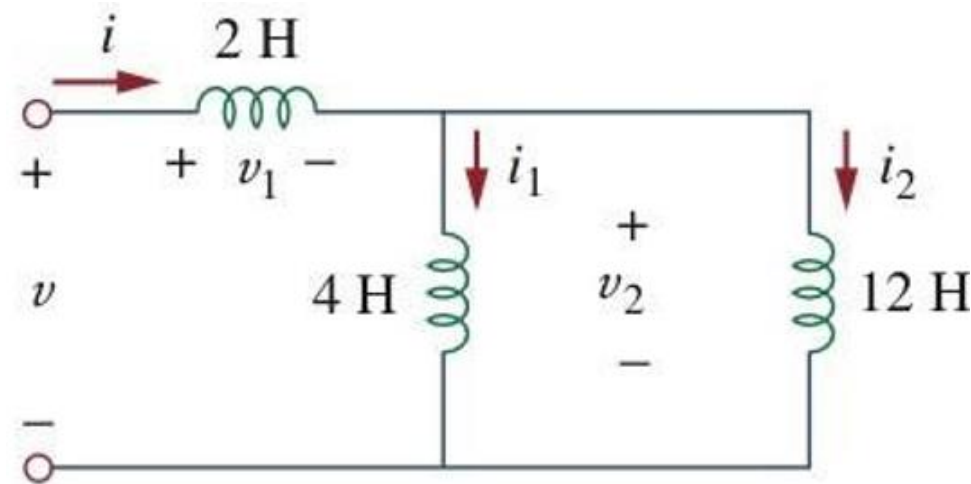

Solution:

$$\begin{aligned} i_1(t) &= \frac{1}{4} \int_0^t v_2 dt + i_1(0) = \frac{120}{4} \int_0^t e^{-10t} dt + 5 \text{ mA} \\ &= -3e^{-10t} \Big|_0^t + 5 \text{ mA} = -3e^{-10t} + 3 + 5 = 8 - 3e^{-10t} \text{ mA} \end{aligned}$$

Note that $i_1(t) + i_2(t) = i(t)$


$$\begin{aligned} i_2(t) &= \frac{1}{12} \int_0^t v_2 dt + i_2(0) = \frac{120}{12} \int_0^t e^{-10t} dt - 1 \text{ mA} \\ &= -e^{-10t} \Big|_0^t - 1 \text{ mA} = -e^{-10t} + 1 - 1 = -e^{-10t} \text{ mA} \end{aligned}$$

2- Inductors

Series and Parallel Inductors

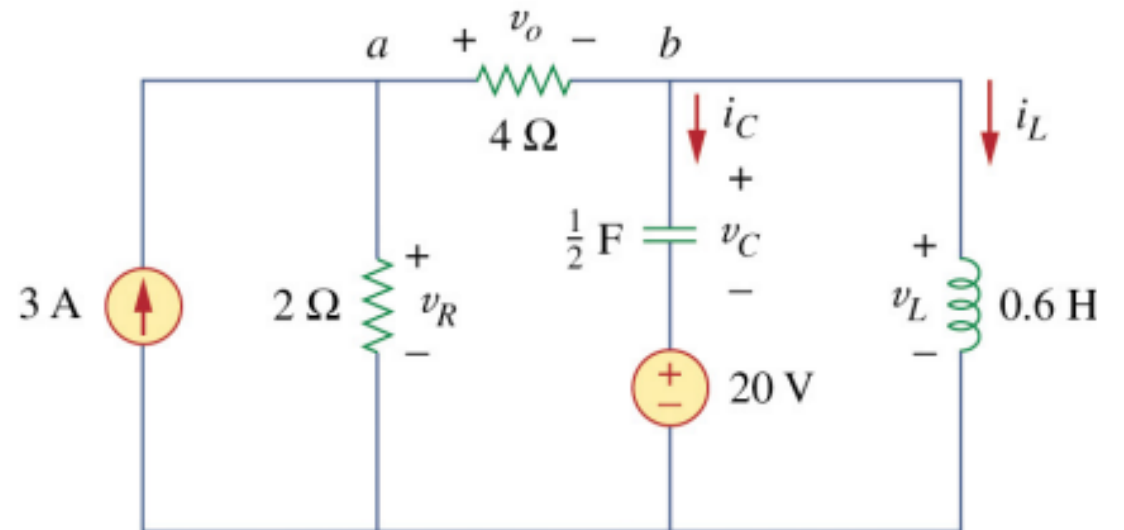Exercise

In the following circuit find the energy that is stored in the inductor and capacitor.






Capacitors and Inductors

Important characteristics of the basic elements.[†]

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
$v-i$:	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$	$v = L \frac{di}{dt}$
$i-v$:	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{\text{eq}} = R_1 + R_2$	$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{\text{eq}} = L_1 + L_2$
Parallel:	$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{\text{eq}} = C_1 + C_2$	$L_{\text{eq}} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

Capacitors and Inductors

- Current and voltage relationship for R, L, C

Elements Symbol	RESISTOR 	CAPACITOR 	INDUCTOR 
Denoted by	R	C	L
Equation	$R = \frac{V}{I}$	$C = \frac{Q}{V}$	$L = \frac{V_L}{(di/dt)}$
Series	$R_T = R_1 + R_2$	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$	$L_T = L_1 + L_2$
Parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$	$C_T = C_1 + C_2$	$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2}$