

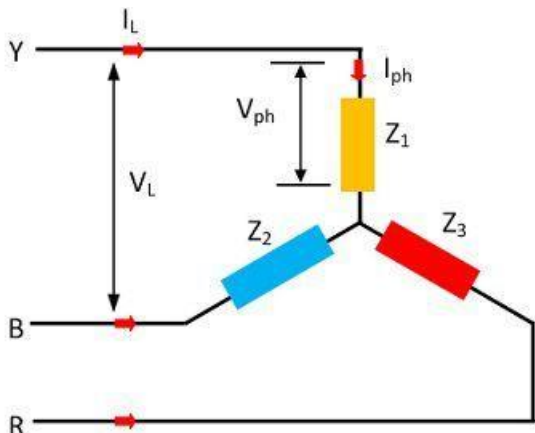
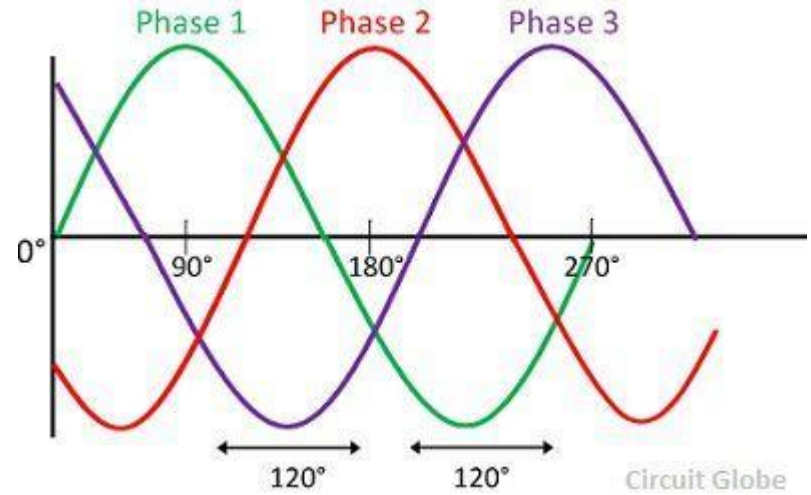
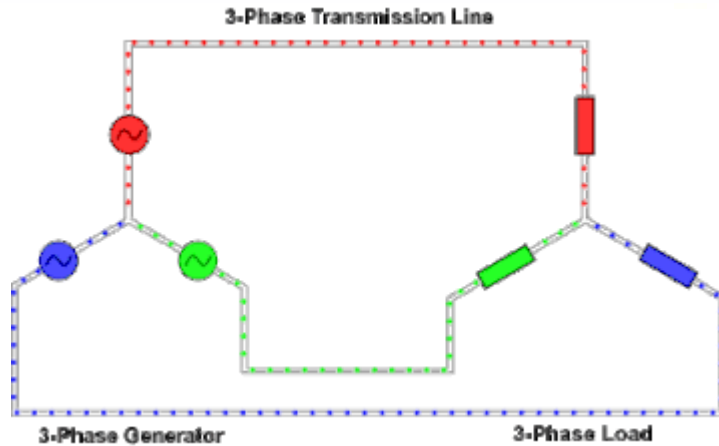


Topic 9: 3-Phase Circuit Analysis

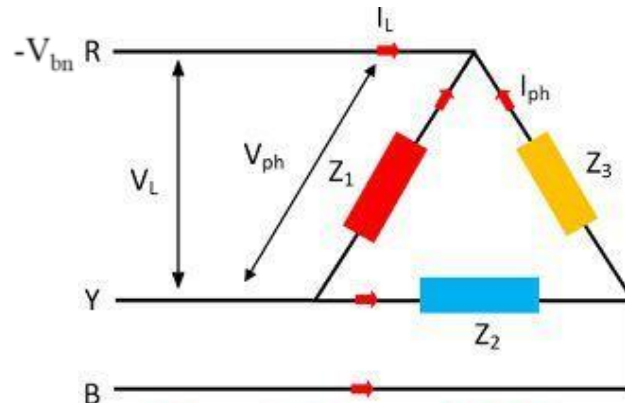


3 - Phase Load Connected in Star

Circuit Globe

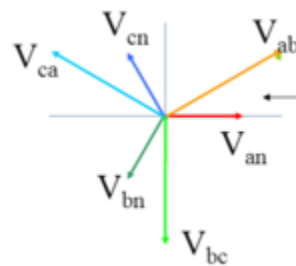

3 - Phase Load Connected in Delta

Circuit Globe

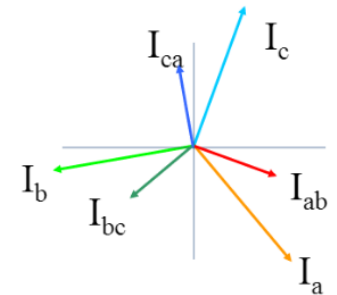


Three phase Circuits

- An AC generator designed to develop a single sinusoidal voltage for each rotation of the shaft (rotor) is referred to as a **single-phase AC generator**.
- If the number of coils on the rotor is increased in a specified manner, the result is a **Polyphase AC generator**, which develops more than one AC phase voltage per rotation of the rotor
- In general, **three-phase systems are preferred over single-phase systems for the transmission of power** for many reasons.
 1. Thinner conductors can be used to transmit the same kVA at the same voltage, which reduces the amount of copper required (typically about 25% less).
 2. The lighter lines are easier to install, and the supporting structures can be less massive and farther apart.
 3. Three-phase equipment and motors have preferred running and starting characteristics compared to single-phase systems because of a more even flow of power to the transducer than can be delivered with a single-phase supply.
 4. In general, most larger motors are three phase because they are essentially self-starting and do not require a special design or additional starting circuitry.

Single-Phase, Two-Phase, Three phase Circuits




(a)

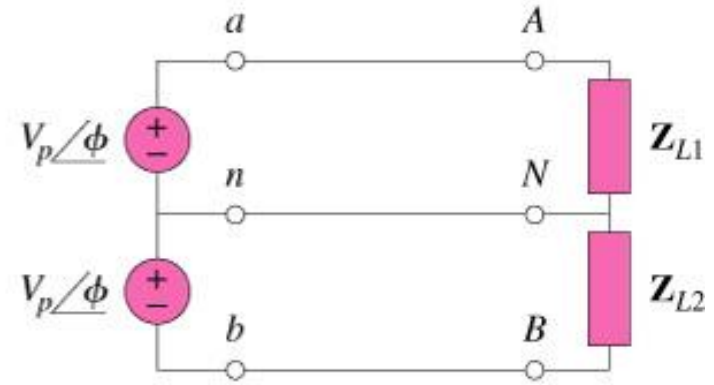

(b)

a) Single phase systems two-wire type

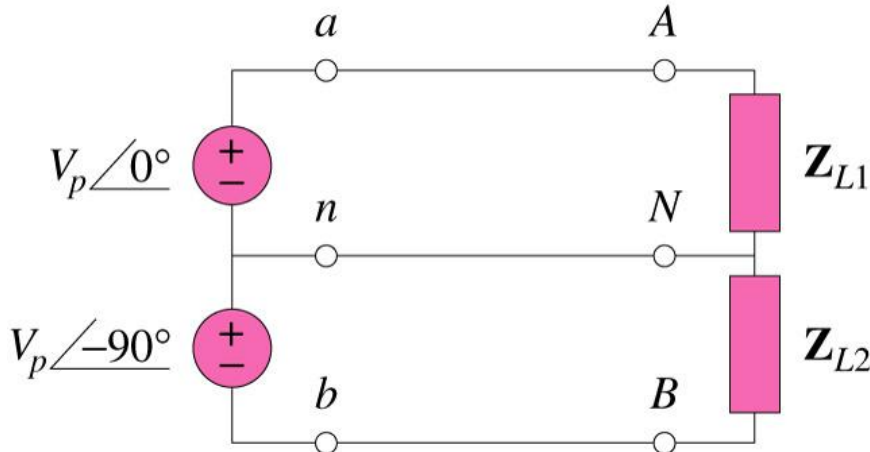b) Single phase systems three-wire type.
Allows connection to both 120 V and 240 V.




Two-phase three-wire system.

The AC sources operate at different phases.


Three-phase Generator

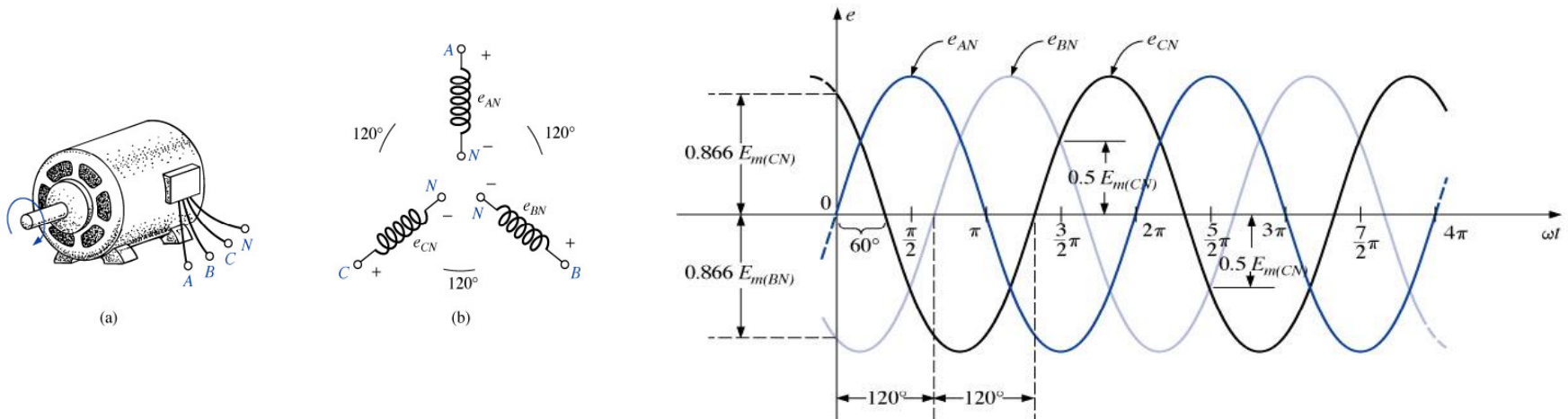- The three-phase generator has three induction coils placed 120° apart on the stator.
- The three coils have an equal number of turns, the voltage induced across each coil will have the same peak value, shape and frequency.




Balanced Three-phase Voltages

Three-phase four-wire system

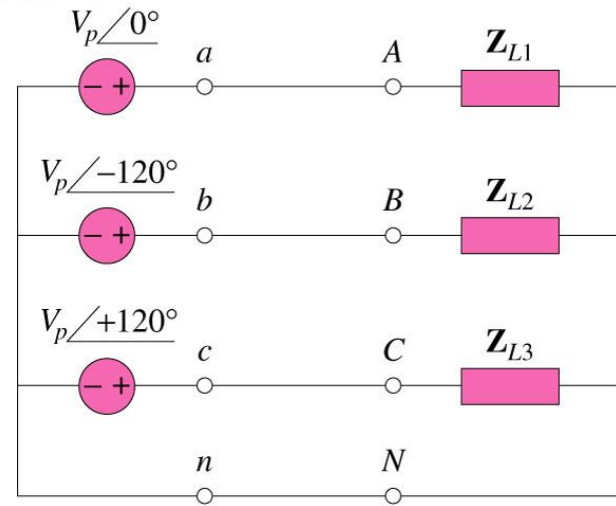


Neutral Wire


A Three-phase Generator

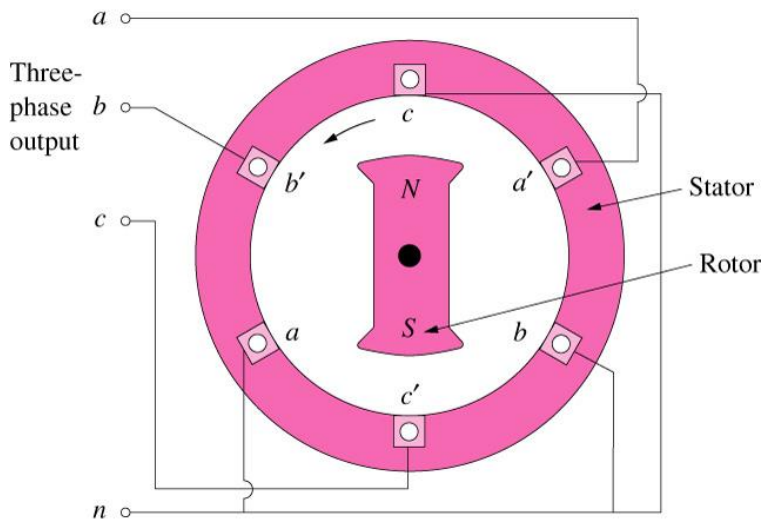


Voltages having 120° phase difference

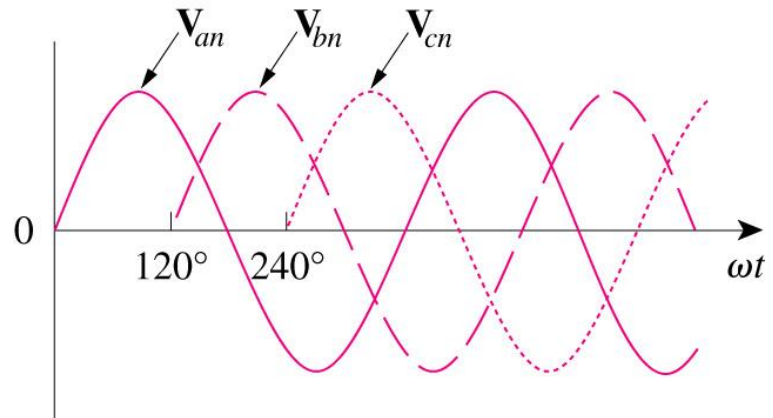


Balanced Three phase Voltages

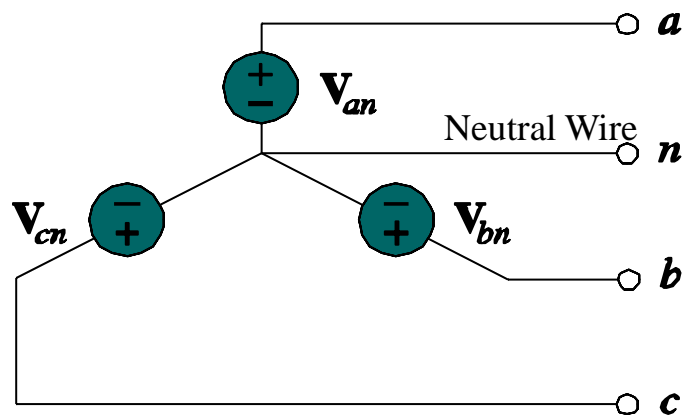


a) Wye Connected Source

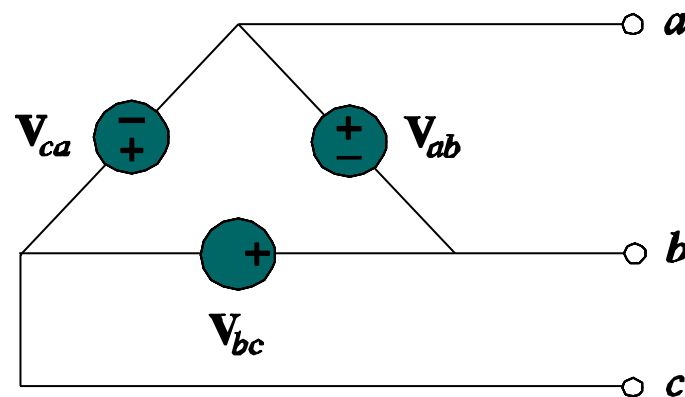

b) Delta Connected Source

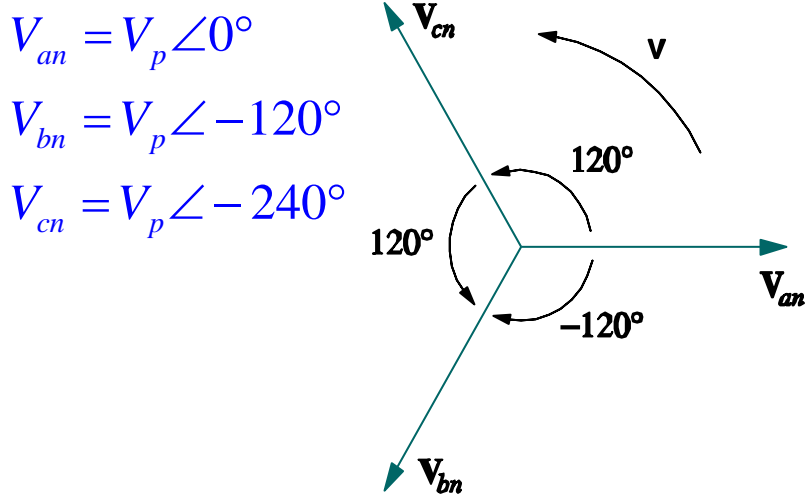


a) abc or positive sequence

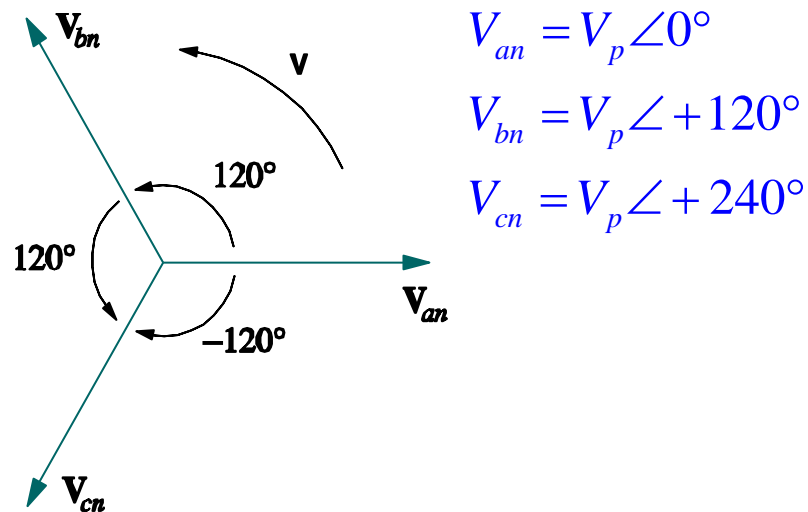

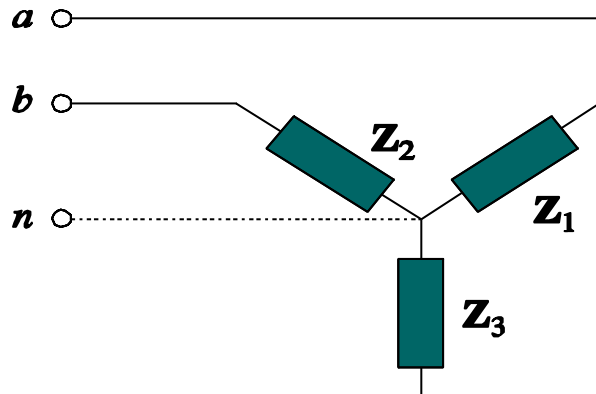
b) acb or negative sequence

Balanced Three phase Loads

- A Balanced load has equal impedances on all the phases



a) Wye-connected load

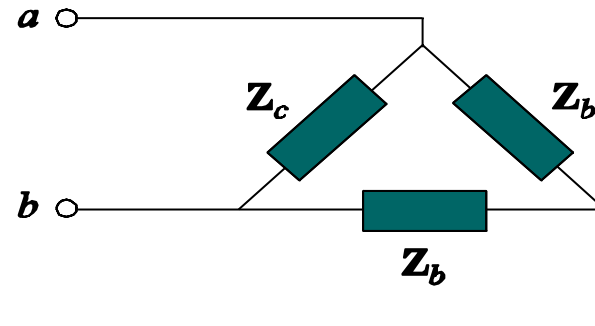

b) Delta-connected load

Balanced Impedance Conversion:

Conversion of Delta circuit to Wye or Wye to Delta.

$$Z_Y = Z_1 = Z_2 = Z_3$$


$$Z_\Delta = Z_a = Z_b = Z_c$$

$$Z_\Delta = 3Z_Y \quad Z_Y = \frac{1}{3}Z_\Delta$$

Three phase Connections Y-Y Connection

➤ Both the three phase source and the three phase load can be connected Wye Wye.


➤ Y-Y connection

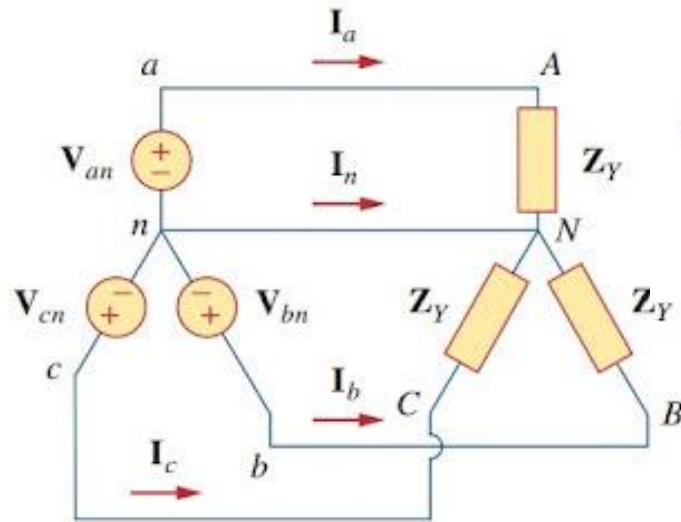


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$

$$V_L = \sqrt{3}V_p$$

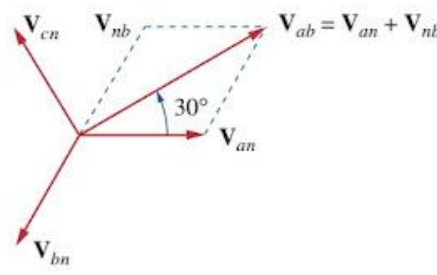


(a)

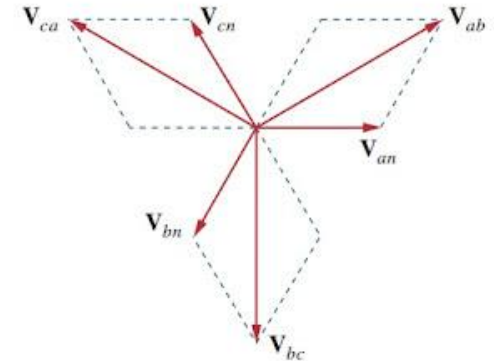

b)

$$I_a = \frac{V_{an}}{Z_Y}, \quad I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle -120^\circ}{Z_Y} = I_a \angle -120^\circ$$
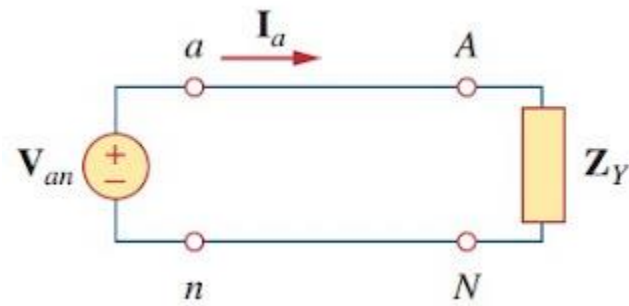
$$I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle -240^\circ}{Z_Y} = I_a \angle -240^\circ$$



$$I_a = \frac{V_{an}}{Z_Y}$$


Three phase Connections Y-Y Connection

➤ Example: Calculate the line currents in the three-wire Y-Y system shown below.

$$\mathbf{I}_a = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ = 6.81 \angle -141.8^\circ \text{ A}$$
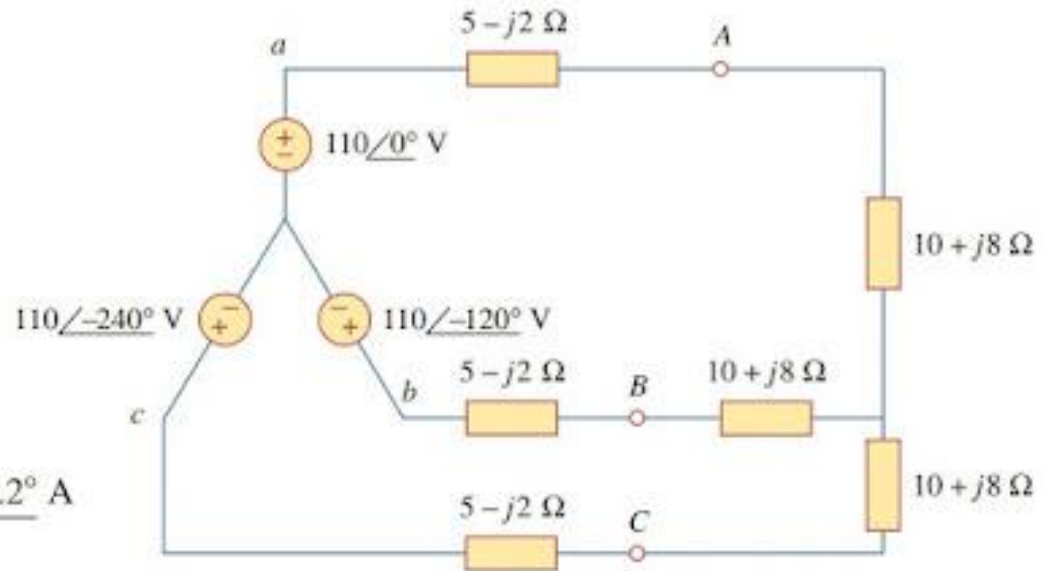
$$\mathbf{I}_c = \mathbf{I}_a \angle -240^\circ = 6.81 \angle -261.8^\circ \text{ A} = 6.81 \angle 98.2^\circ \text{ A}$$



Three phase Connections Y-Δ Connection

➤ Both the three phase source and the three phase load can be connected Wye Wye.

➤ Y-Δ connection

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}, \quad I_{BC} = \frac{V_{BC}}{Z_{\Delta}}, \quad I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$



$$I_a = I_{AB} - I_{CA}, \quad I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC}$$

$$I_a = I_{AB} - I_{CA} = I_{AB}(1 - 1\angle -240^\circ) \\ = I_{AB}(1 + 0.5 - j0.866) = I_{AB}\sqrt{3}\angle -30^\circ$$

$$I_L = \sqrt{3}I_p$$

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

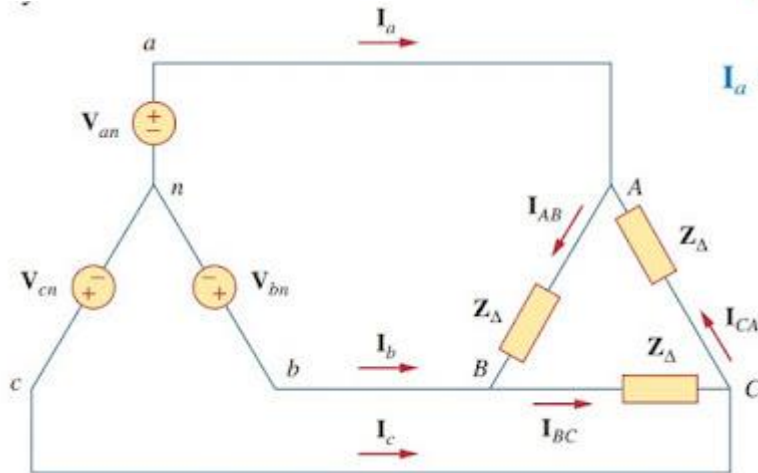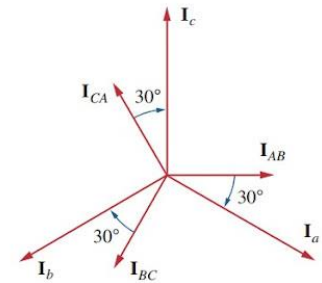


$$V_{an} = V_p\angle 0^\circ$$

$$V_{bn} = V_p\angle -120^\circ, \quad V_{cn} = V_p\angle +120^\circ$$

$$V_{ab} = \sqrt{3}V_p\angle 30^\circ = V_{AB}, \quad V_{bc} = \sqrt{3}V_p\angle -90^\circ = V_{BC}$$
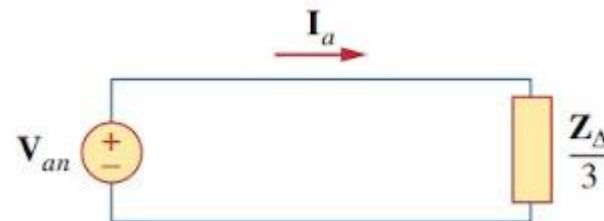
$$V_{ca} = \sqrt{3}V_p\angle -150^\circ = V_{CA}$$



$$Z_Y = \frac{Z_{\Delta}}{3}$$

Three phase Connections Y-Δ Connection

➤ Example: A balanced *abc*-sequence Y-connected source with $\mathbf{V}_{an} = 100\angle 10^\circ$ V is connected to a Δ -connected balanced load $(8 + j4) \Omega$ per phase. Calculate the phase and line currents.

The load impedance is $\mathbf{Z}_{\Delta} = 8 + j4 = 8.944\angle 26.57^\circ \Omega$

If the phase voltage $\mathbf{V}_{an} = 100\angle 10^\circ$, then the line voltage is

$$\mathbf{V}_{ab} = \mathbf{V}_{an} \sqrt{3} \angle 30^\circ = 100 \sqrt{3} \angle 10^\circ + 30^\circ = \mathbf{V}_{AB} \quad \mathbf{V}_{AB} = 173.2 \angle 40^\circ \text{ V}$$

The phase currents are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}} = \frac{173.2 \angle 40^\circ}{8.944 \angle 26.57^\circ} = 19.36 \angle 13.43^\circ \text{ A}$$

$$\mathbf{I}_{BC} = \mathbf{I}_{AB} \angle -120^\circ = 19.36 \angle -106.57^\circ \text{ A}$$

$$\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle +120^\circ = 19.36 \angle 133.43^\circ \text{ A}$$

The line currents are

$$\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ = \sqrt{3}(19.36) \angle 13.43^\circ - 30^\circ = 33.53 \angle -16.57^\circ \text{ A}$$



$$\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ = 33.53 \angle -136.57^\circ \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ = 33.53 \angle 103.43^\circ \text{ A}$$

Alternatively, using single-phase analysis,

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_{\Delta}/3} = \frac{100 \angle 10^\circ}{2.981 \angle 26.57^\circ} = 33.54 \angle -16.57^\circ \text{ A}$$

THREE PHASE CIRCUITS

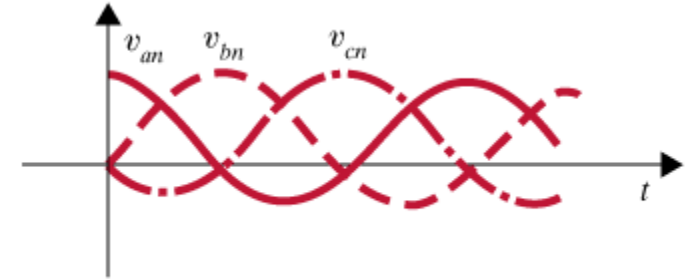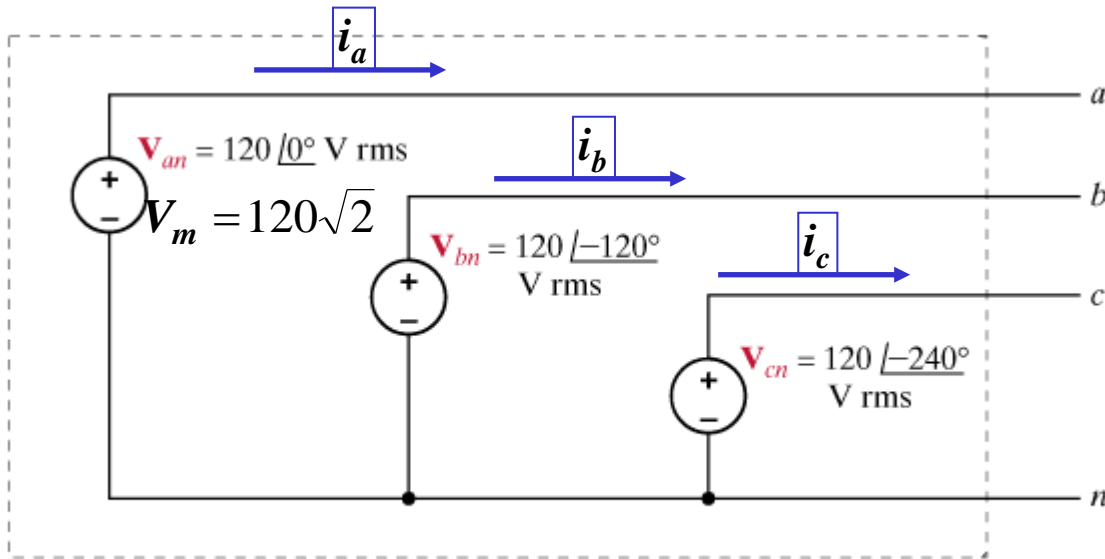

Instantaneous Phase Voltages

$$v_{an}(t) = V_m \cos(\omega t)(V)$$

$$v_{bn}(t) = V_m \cos(\omega t - 120^\circ)(V)$$

$$v_c(t) = V_m \cos(\omega t - 240^\circ)(V)$$

Balanced Phase Currents

$$i_a(t) = I_m \cos(\omega t - \theta)$$

$$i_b(t) = I_m \cos(\omega t - \theta - 120^\circ)$$

$$i_c(t) = I_m \cos(\omega t - \theta - 240^\circ)$$

Instantaneous power

$$p(t) = v_{an}(t)i_a(t) + v_{bn}(t)i_b(t) + v_{cn}(t)i_c(t)$$

Theorem

For a balanced three phase circuit the instantaneous power is constant

$$p(t) = 3 \frac{V_m I_m}{2} \cos \theta \quad W$$

Proof of Theorem

For a balanced three phase circuit the instantaneous power is constant

$$p(t) = 3 \frac{V_m I_m}{2} \cos \theta \text{ (W)}$$

Instantaneous power

$$p(t) = v_{an}(t)i_a(t) + v_{bn}(t)i_b(t) + v_{cn}(t)i_c(t)$$

$$p(t) = V_m I_m \left[\begin{array}{l} \cos \omega t \cos(\omega t - \theta) \\ + \cos(\omega t - 120) \cos(\omega t - 120 - \theta) \\ + \cos(\omega t - 240) \cos(\omega t - 240 - \theta) \end{array} \right]$$

$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$

$$p(t) = V_m I_m \left[\begin{array}{l} 3 \cos \theta + \cos(2\omega t - \theta) \\ + \cos(2\omega t - 240 - \theta) \\ + \cos(2\omega t - 480 - \theta) \end{array} \right]$$

$$\phi = \omega t - \theta$$

$$\cos(\phi - 240) = \cos(\phi + 120)$$

$$\cos(\phi - 480) = \cos(\phi - 120)$$

$$\cos(120) = -0.5$$

Lemma

$$\cos \phi + \cos(\phi - 120) + \cos(\phi + 120) = 0$$

Proof

$$\cos \phi = \cos \phi$$


$$\cos(\phi - 120) = \cos \phi \cos(120) + \sin \phi \sin(120)$$

$$\cos(\phi + 120) = \cos \phi \cos(120) - \sin \phi \sin(120)$$

$$\cos \phi + \cos(\phi - 120) + \cos(\phi + 120) = 0$$

SOURCE/LOAD CONNECTIONS

BALANCED Y-Y CONNECTION

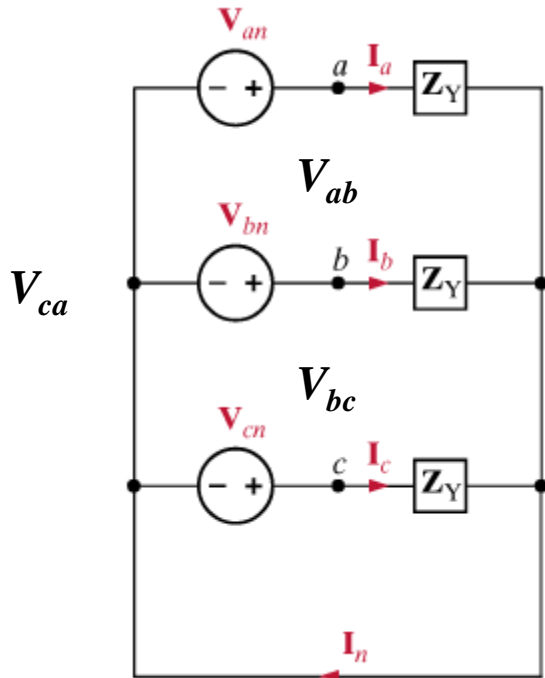

$$I_a = \frac{V_{an}}{Z_Y}; I_b = \frac{V_{bn}}{Z_Y}; I_c = \frac{V_{cn}}{Z_Y}$$

$$I_a = |I_L| \angle \theta^\circ; I_b = |I_L| \angle \theta - 120^\circ; I_c = |I_L| \angle \theta + 120^\circ$$


$$I_a + I_b + I_c = I_n = 0 \quad \text{For this balanced circuit it is enough to analyze one phase}$$

$$V_{an} = |V_p| \angle 0^\circ$$


$$V_{bn} = |V_p| \angle -120^\circ$$

$$V_{cn} = |V_p| \angle 120^\circ$$

Positive sequence phase voltages

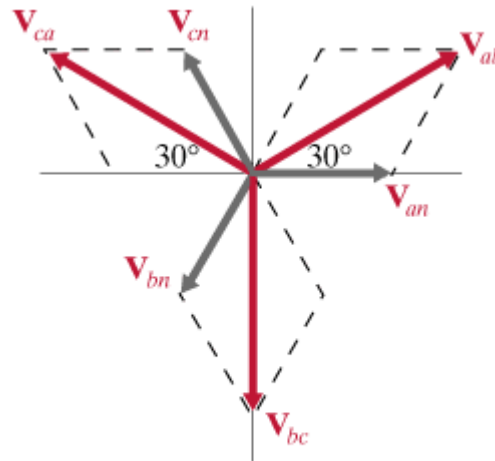

Line voltages

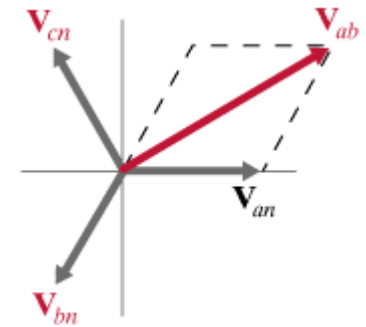

$$V_{ab} = V_{an} - V_{bn}$$

$$= |V_p| \angle 0^\circ - |V_p| \angle -120^\circ$$

$$= |V_p| (1 - (\cos 120 - j \sin 120))$$

$$= |V_p| \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right)$$

$$= \sqrt{3} |V_p| \angle 30^\circ$$


$$V_{bc} = \sqrt{3} |V_p| \angle -90^\circ$$

$$V_{ca} = \sqrt{3} |V_p| \angle -210^\circ$$

$$V_L = \sqrt{3} |V_p| = \text{Line Voltage}$$

Example: For an abc sequence, balanced Y-Y three phase circuit $V_{ab} = 208 \angle -30^\circ$

Determine the phase voltages.

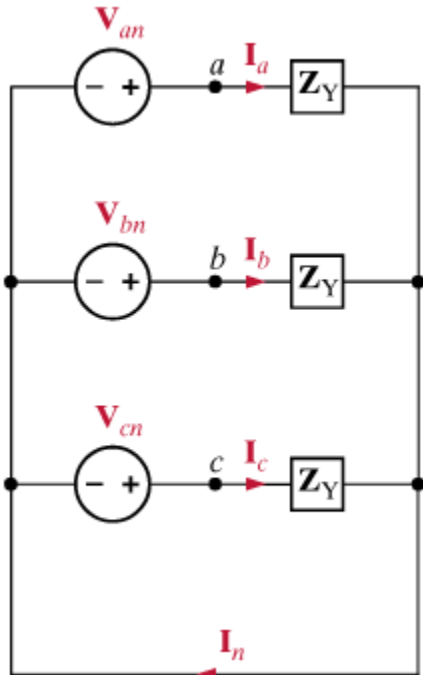


Balanced Y - Y

$$V_{an} = 120 \angle -60^\circ$$

$$V_{bn} = 120 \angle -180^\circ$$

$$V_{cn} = 120 \angle 60^\circ$$

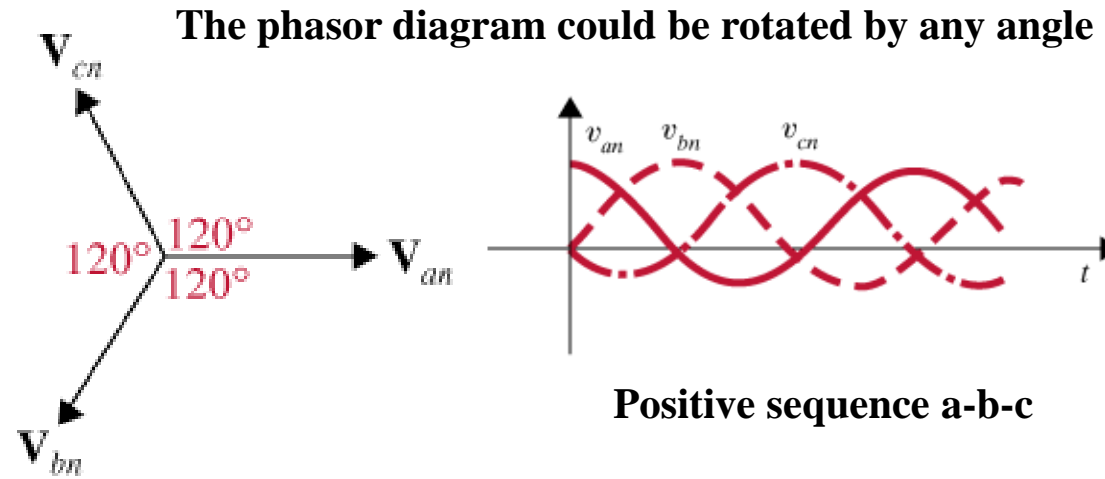


$$V_{an} = |V_p| \angle 0^\circ$$

$$V_{bn} = |V_p| \angle -120^\circ$$

$$V_{cn} = |V_p| \angle 120^\circ$$

**Positive sequence
phase voltages**

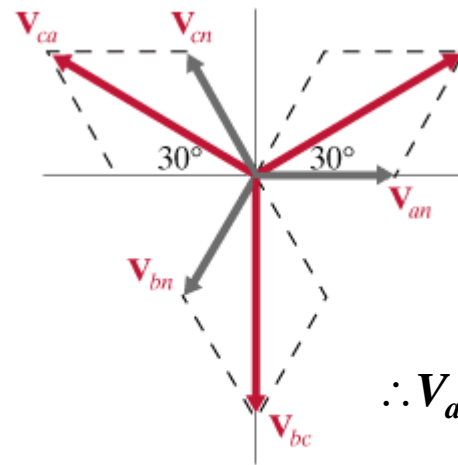

$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$$

V_{an} lags V_{ab} by 30°

$$V_{ab} = 208 \angle -30^\circ$$


$$\therefore V_{an} = \frac{|V_{ab}|}{\sqrt{3}} \angle (-30^\circ - 30^\circ)$$

Relationship between phase and line voltages

Example: For an abc sequence, balanced Y - Y three phase circuit

source $|V_{phase}| = 120(V)_{rms}$, $Z_{line} = 1 + j1\Omega$, $Z_{phase} = 20 + j10\Omega$

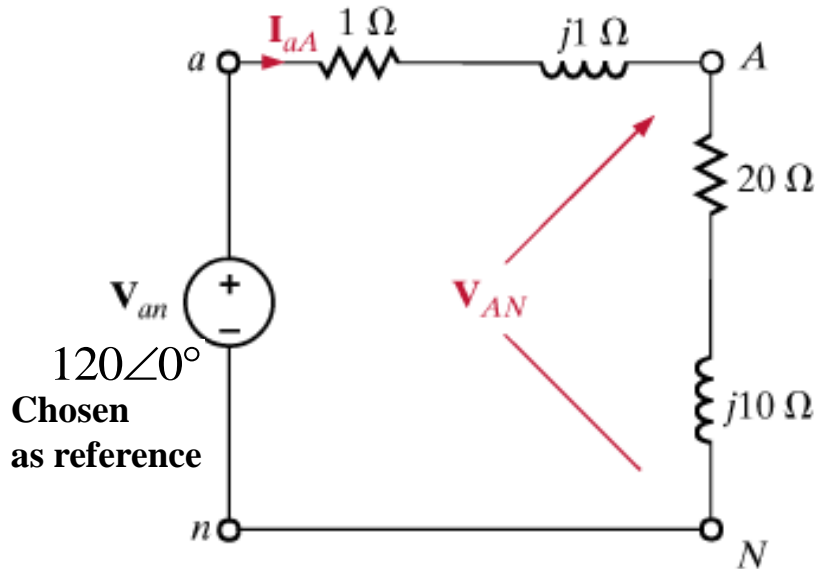Determine line currents and load voltages.



$120\angle 0^\circ$
Chosen
as reference

$$V_{an} = 120 \angle 0^\circ$$

$$V_{bn} = 120 \angle -120^\circ$$

$$V_{cn} = 120 \angle 120^\circ$$

Abc sequence

$$I_{aA} = \frac{V_{an}}{21 + j11} = \frac{120 \angle 0^\circ}{23.71 \angle 27.65^\circ}$$

$$= 5.06 \angle -27.65^\circ (A)_{rms}$$

Because circuit is balanced data on any one phase are sufficient

$$I_{bB} = 5.06 \angle -120 - 27.65^\circ (A)_{rms}$$

$$I_{cC} = 5.06 \angle 120 - 27.65^\circ (A)_{rms}$$

$$V_{AN} = I_{aA} \times (20 + j10) = I_{aA} \times 22.36 \angle 26.57^\circ$$

$$V_{AN} = 113.15 \angle -1.08^\circ (V)_{rms}$$

$$V_{BN} = 113.15 \angle -121.08^\circ (V)_{rms}$$

$$V_{CN} = 113.15 \angle 118.92^\circ (V)_{rms}$$

Example: For an abc sequence, balanced Y - Y three phase circuit


$V_{an} = 120 \angle 90^\circ (\text{V})_{rms}$. Find the line voltages

V_{ab} leads V_{an} by 30°

$$V_{ab} = \sqrt{3} \times 120 \angle 120^\circ (\text{V})_{rms}$$

$$V_{bc} = \sqrt{3} \times 120 \angle 0^\circ (\text{V})_{rms}$$
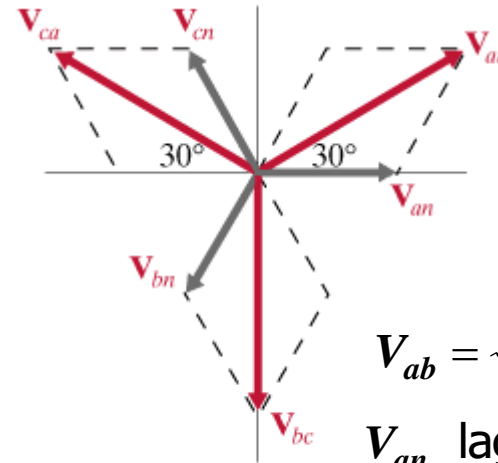
$$V_{ca} = \sqrt{3} \times 120 \angle 240^\circ (\text{V})_{rms}$$



$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$$

V_{an} lags V_{ab} by 30°

$V_{ab} = 208 \angle 0^\circ (\text{V})_{rms}$. Find the phase voltages

V_{an} lags V_{ab} by 30°

$$V_{an} = \frac{208}{\sqrt{3}} \angle -30^\circ (\text{V})_{rms}$$

$$V_{bn} = \frac{208}{\sqrt{3}} \angle -150^\circ (\text{V})_{rms}$$


$$V_{cn} = \frac{208}{\sqrt{3}} \angle 90^\circ (\text{V})_{rms}$$

**Relationship between
phase and line voltages**

Example: For an abc sequence, balanced Y - Y three phase circuit

load, $|V_{phase}| = 104.02 \angle 26.6^\circ (V)_{rms}$, $Z_{line} = 1 + j1 \Omega$, $Z_{phase} = 8 + j3 \Omega$

Determine source phase voltages

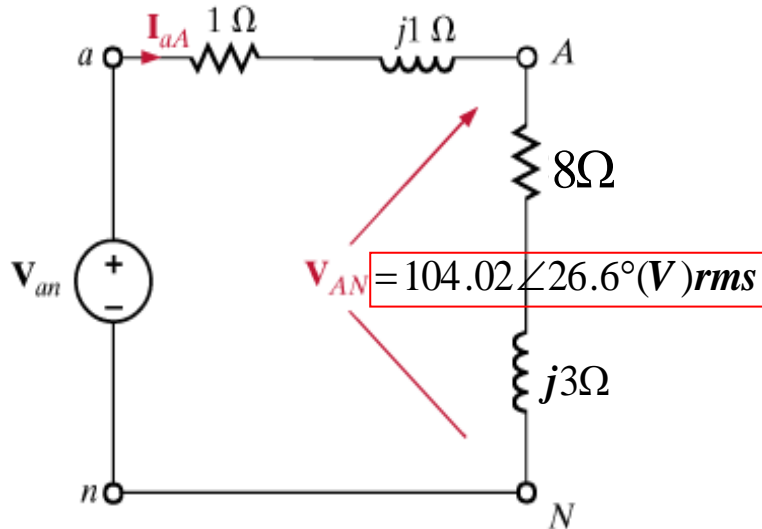

Currents are not required. Use inverse voltage divider


$$V_{an} = \frac{(8 + j3) + (1 + j1)}{8 + j3} V_{AN}$$

$$\frac{9 + j4}{8 + j3} \times \frac{8 - j3}{8 - j3} = \frac{84 + j5}{73} = 1.15 \angle 3.41^\circ$$

$$V_{an} = 120 \angle 30^\circ$$


$$V_{bn} = 120 \angle -90^\circ$$

$$V_{cn} = 120 \angle 150^\circ$$

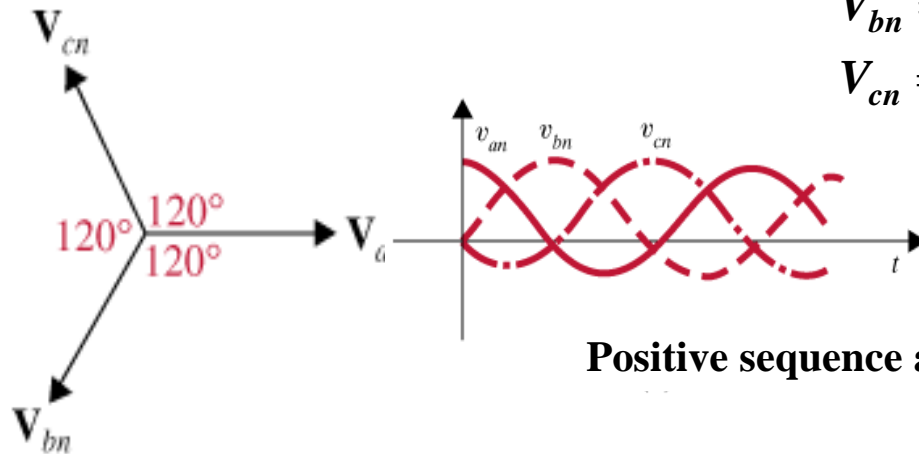

Positive sequence a-b-c

DELTA-CONNECTED LOAD

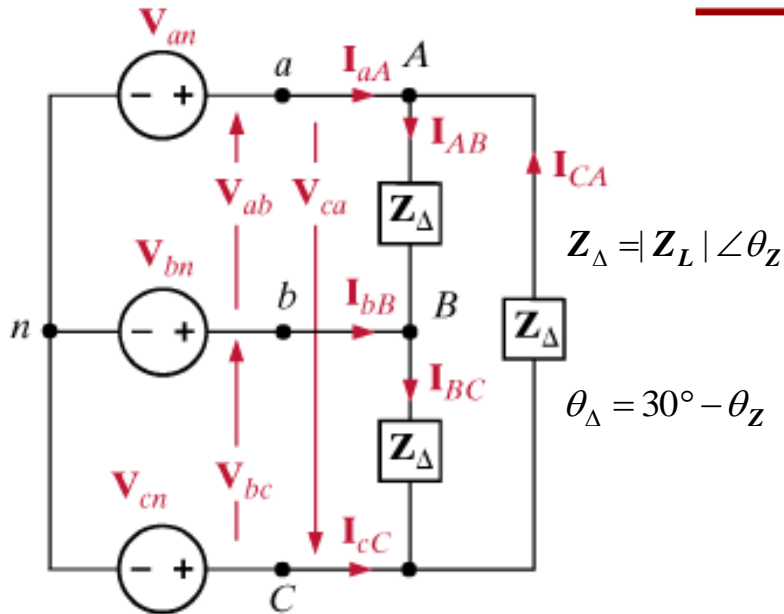

Method 1: Solve directly

$$\begin{aligned} V_{an} &= |V_p| \angle 0^\circ & V_{ab} &= \sqrt{3} |V_p| \angle 30^\circ \\ V_{bn} &= |V_p| \angle -120^\circ & V_{bc} &= \sqrt{3} |V_p| \angle -90^\circ \\ V_{cn} &= |V_p| \angle 120^\circ & V_{ca} &= \sqrt{3} |V_p| \angle -210^\circ \end{aligned}$$

Positive sequence
phase voltages

$$\begin{aligned} |I_{line}| &= \sqrt{3} |I_\Delta| \\ \theta_{line} &= \theta_\Delta - 30^\circ \end{aligned}$$

Line-phase current
relationship

Load phase currents

$$I_{AB} = \frac{V_{AB}}{Z_\Delta} = |I_\Delta| \angle \theta_\Delta$$

$$I_{BC} = \frac{V_{BC}}{Z_\Delta} = |I_\Delta| \angle \theta_\Delta - 120^\circ$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta} = |I_\Delta| \angle \theta_\Delta + 120^\circ$$

Line currents

$$I_{aA} = I_{AB} - I_{CA}$$

$$I_{bB} = I_{BC} - I_{AB}$$

$$I_{cC} = I_{CA} - I_{BC}$$

Method 2: We can also convert the delta connected load into a Y connected one.

The same formulas derived for resistive circuits are applicable to impedances


Balanced case $Z_Y = \frac{Z_\Delta}{3}$

$$I_{aA} = \frac{V_{an}}{Z_Y} = |I_{aA}| \angle \theta_L \Rightarrow \begin{cases} |I_{aA}| = \frac{|V_{AB}| / \sqrt{3}}{|Z_\Delta| / 3} \\ \theta_L = -\theta_Z \end{cases}$$

REVIEW OF

$\Delta \leftrightarrow Y$

Transformations

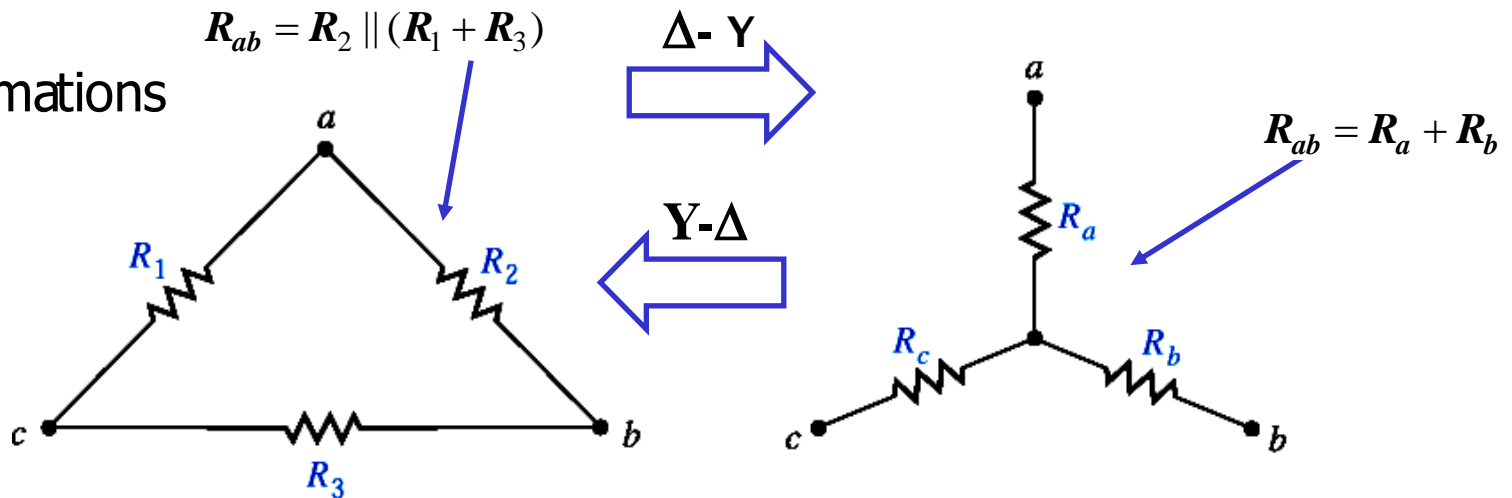

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$\Delta \rightarrow Y$


$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$


$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$Y - \Delta$
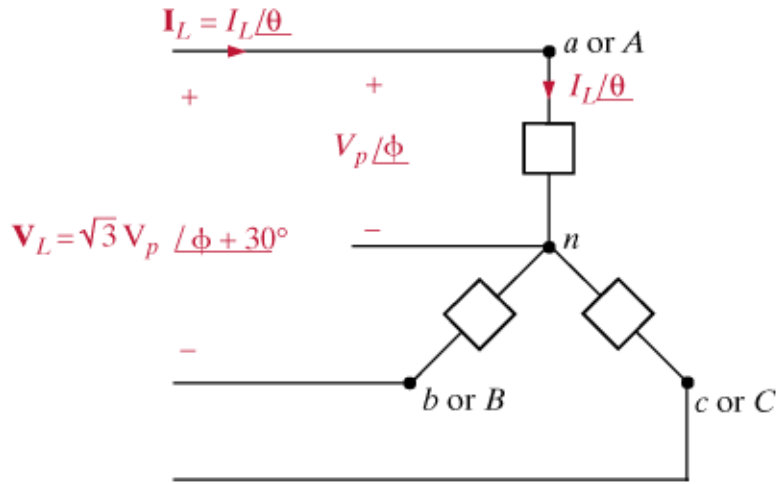
$$R_{\Delta} = R_1 = R_2 = R_3 \Rightarrow R_Y = \frac{R_{\Delta}}{3}$$




(a)

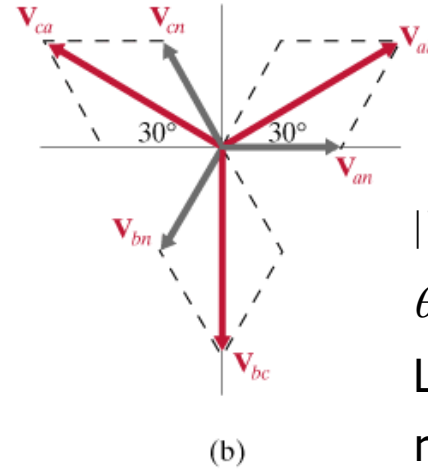

(b)

$|V_{\Delta}| = \sqrt{3} |V_{phase}|$
 $\theta_{\Delta} = \theta_{phase} + 30^\circ$
 Line - phase voltage relationship

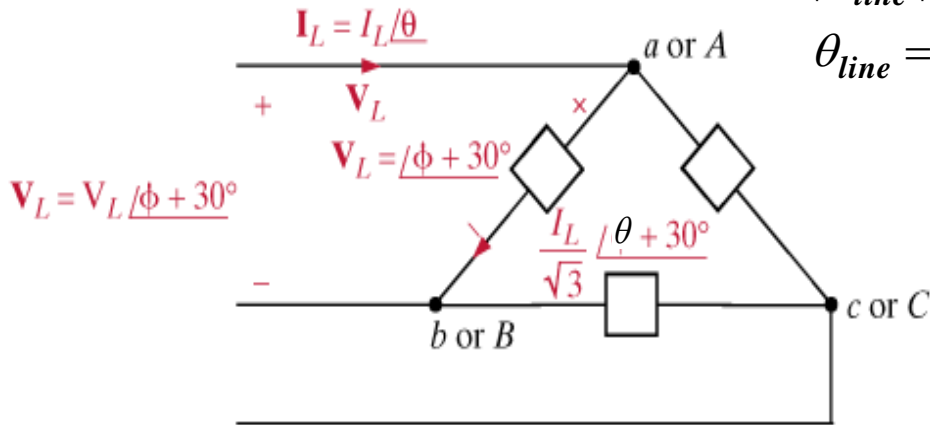

(b)

$|I_{line}| = \sqrt{3} |I_{\Delta}|$
 $\theta_{line} = \theta_{\Delta} - 30^\circ$
 Line-phase current relationship

Example:

$I_{aA} = 12 \angle 40^\circ$


Find the phase currents

$I_{AB} = 6.93 \angle 70^\circ$

$I_{BC} = 6.93 \angle -50^\circ$

$I_{CA} = 6.93 \angle 190^\circ$

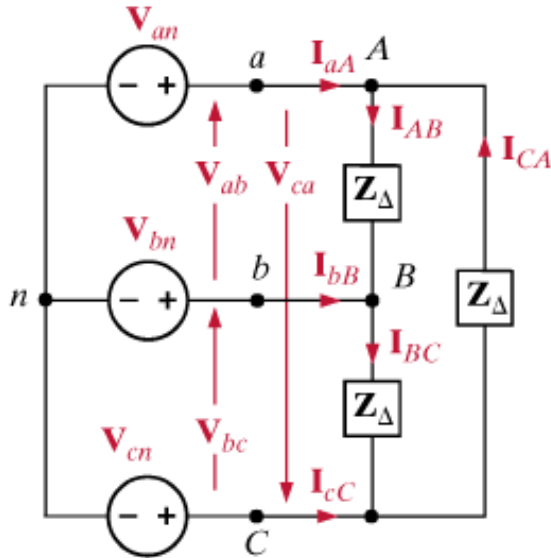Example: Delta-connected load consists of 10-Ohm resistance in series with 20-mH inductance. Source is Y-connected, abc sequence, 120-V rms, 60Hz. Determine all line and phase currents



$$V_{an} = 120 \angle 30^\circ (\text{V})_{rms}$$

$$Z_{\text{inductance}} = 2\pi \times 60 \times 0.020 = 7.54 \Omega$$

$$Z_{\Delta} = 10 + j7.54 \Omega = 12.52 \angle 37.02^\circ \Rightarrow Z_Y = 4.17 \angle 37.02^\circ$$

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{120\sqrt{3} \angle 60^\circ}{10 + j7.54} = 16.60 \angle 22.98^\circ (\text{A})_{rms}$$

$$I_{BC} = 16.60 \angle -97.02^\circ (\text{A})_{rms}$$

$$I_{CA} = 16.60 \angle 142.98^\circ (\text{A})_{rms}$$

$$I_{aA} = 28.75 \angle -7.02^\circ (\text{A})_{rms}$$

$$I_{bB} = 28.75 \angle -127.02^\circ (\text{A})_{rms}$$

$$I_{cC} = 28.75 \angle 112.98^\circ (\text{A})_{rms}$$

$$|V_{\Delta}| = \sqrt{3} |V_{\text{phase}}|$$

$$\theta_{\Delta} = \theta_{\text{phase}} + 30^\circ$$

Line - phase voltage relationship


$$|I_{\text{line}}| = \sqrt{3} |I_{\Delta}|$$

$$\theta_{\text{line}} = \theta_{\Delta} - 30^\circ$$

Line-phase current relationship

Alternatively, determine first the line currents and then the delta currents

POWER RELATIONSHIPS

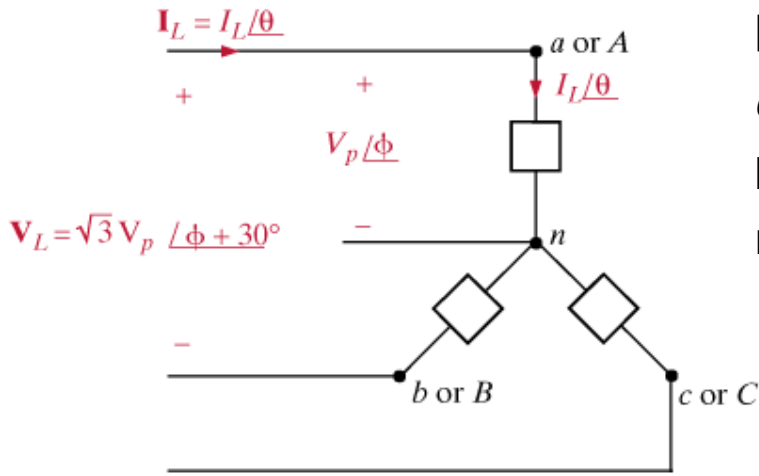


(a)


$|V_{\Delta}| = \sqrt{3} |V_{phase}|$
 $\theta_{\Delta} = \theta_{phase} + 30^{\circ}$
 Line - phase voltage relationship

$$S_{Total} = 3 \times V_{phase} \times I_{phase}^*$$
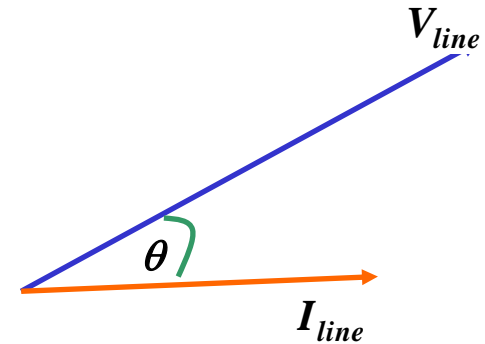
$$S_{Total} = \sqrt{3} V_{line} I_{line}^*$$



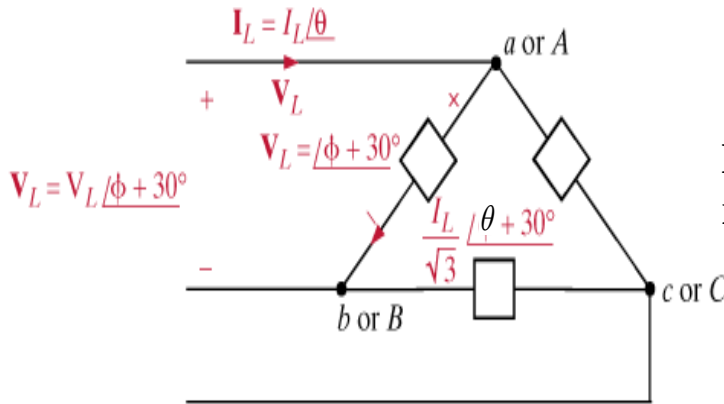θ **Impedance angle**
 θ **Power factor angle**



(b)

$|I_{line}| = \sqrt{3} |I_{\Delta}|$
 $\theta_{line} = \theta_{\Delta} - 30^{\circ}$
 Line-phase current relationship


$$S_{total} = 3 V_{line} \times I_{\Delta}^*$$

$$S_{Total} = \sqrt{3} V_{line} I_{line}^*$$

$$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f$$

$$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$$

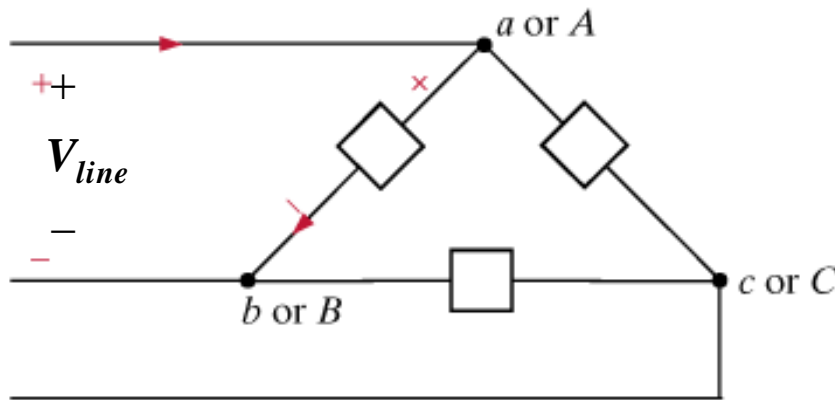EXAMPLE: Determine the magnitude of the line currents and the value of load impedance per phase in the delta



$$|V_{line}| = 208(V)_{rms}$$

$$P_{total} = 1200W$$

power factor angle = 20° lagging

$$|I_{line}| = \sqrt{3} |I_{\Delta}|$$

$$\theta_{line} = \theta_{\Delta} - 30^\circ$$

Line-phase current relationship

$$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f$$

$$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$$


$$\frac{P_{total}}{3} = \frac{|V_{line}| |I_{line}|}{\sqrt{3}} \cos \theta_f \Rightarrow |I_{line}| = 3.54(A)_{rms}$$

$$\Rightarrow |I_{\Delta}| = 2.05(A)_{rms} \Rightarrow |Z_{\Delta}| = \frac{|V_{line}|}{|I_{\Delta}|} = 101.46\Omega$$

Example: For an abc sequence, balanced Y - Y three phase circuit

$$\text{source } |V_{\text{phase}}| = 120(\text{V})_{\text{rms}}, \mathbf{Z}_{\text{line}} = 1 + j1\Omega, \mathbf{Z}_{\text{phase}} = 20 + j10\Omega$$

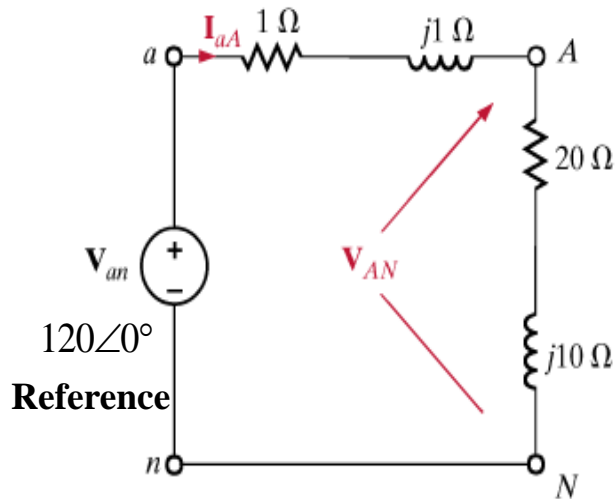Determine real and reactive power per phase at the load and total real, reactive and complex power at the source



$$V_{AN} = I_{aA} \times (20 + j10) = I_{aA} \times 22.36 \angle 26.57^\circ$$

$$V_{AN} = 113.15 \angle -1.08^\circ (\text{V})_{\text{rms}}$$

$$S_{\text{phase}} = V_{AN} I_{aA}^* = 113.15 \angle -1.08^\circ \times 5.06 \angle 27.65^\circ$$

$$S_{\text{phase}} = 572.54 \angle 26.57^\circ = 512 + j256.09 (\text{VA})_{\text{rms}}$$

$$S_{\text{source phase}} = V_{an} \times I_{aA}^* = 120 \angle 0^\circ \times 5.06 \angle 27.65^\circ$$

$$S_{\text{source phase}} = 607.2 \angle 27.65^\circ$$

$$= 537.86 + j281.78 \text{VA}$$

$$P_{\text{total source}} = 3 \times 537.86 (\text{W})$$

$$Q_{\text{total source}} = 3 \times 281.78 (\text{VA})$$

$$S_{\text{total source}} = P_{\text{total source}} + jQ_{\text{total source}} \\ = 1613.6 + j845.2 (\text{VA})$$

$$|S_{\text{total source}}| = 1821.6 (\text{VA})$$

$$V_{an} = 120 \angle 0^\circ$$

$$V_{bn} = 120 \angle -120^\circ$$


$$V_{cn} = 120 \angle 120^\circ$$

Because circuit is balanced data on any one phase are sufficient

Abc sequence

$$I_{aA} = \frac{V_{an}}{21 + j11} = \frac{120 \angle 0^\circ}{23.71 \angle 27.65^\circ} \\ = 5.06 \angle -27.65^\circ (\text{A})_{\text{rms}}$$

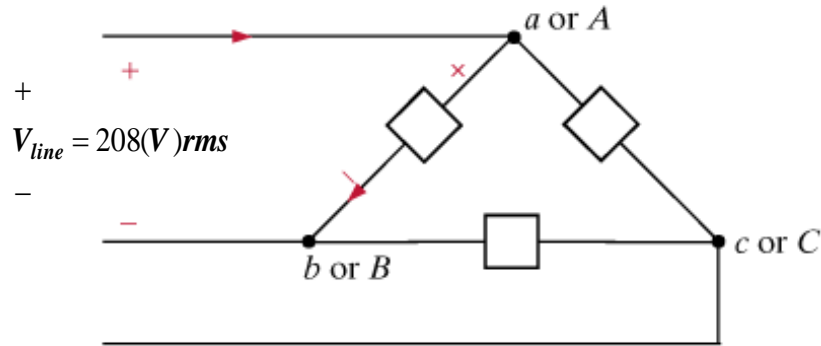Example: Determine the line currents and the combined power factor



Circuit is balanced

Load 1: 24kW at pf = 0.6 lagging

Load 2: 10kW at pf = 1

Load 3: 12kVA at pf = 0.8 leading

$$\left. \begin{array}{l} P_1 = 24kW \\ pf = 0.6 \text{ lagging} \end{array} \right\} \Rightarrow |S_1| = 40kVA$$

$$|Q_1| = \sqrt{|S_1|^2 - |P_1|^2} = 32kVA$$

lagging \Rightarrow inductive $\therefore S_1 = 24 + j32kVA$

Load 2

$$\left. \begin{array}{l} P_2 = 10kW \\ pf = 1 \end{array} \right\} \Rightarrow S_2 = 10 + j0kVA$$

Load 3

$$\left. \begin{array}{l} |S_3| = 12kVA \\ pf = 0.8 \end{array} \right\} \Rightarrow \begin{cases} P_3 = 9.6kW \\ |Q_3| = 7.2kVA \end{cases}$$

leading pf \Rightarrow capacitive $\therefore S_3 = 9.6 - j7.2kVA$


$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$S_{total} = S_1 + S_2 + S_3$$

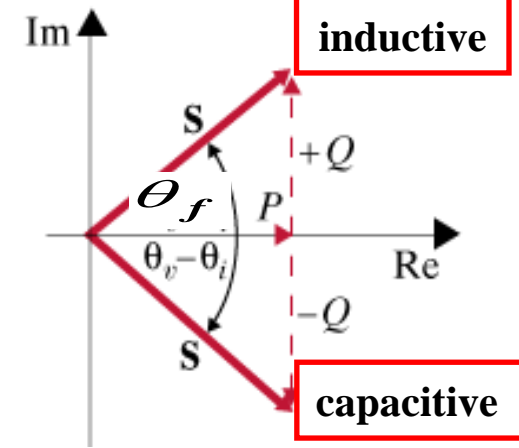

$$S_{TOTAL} = S_1 + S_2 + S_3 = 43.6 + j24.8kVA = 50.160 \angle 29.63^\circ kVA$$

$$\left. \begin{array}{l} P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f \\ Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f \end{array} \right\} \Rightarrow \begin{cases} |S_{total}| = \sqrt{3} |V_{line}| |I_{line}| \\ \theta_f = 29.63^\circ \end{cases}$$

pf = 0.869 lagging


$$|I_{line}| = 139.23(A)rms$$

Continued ...

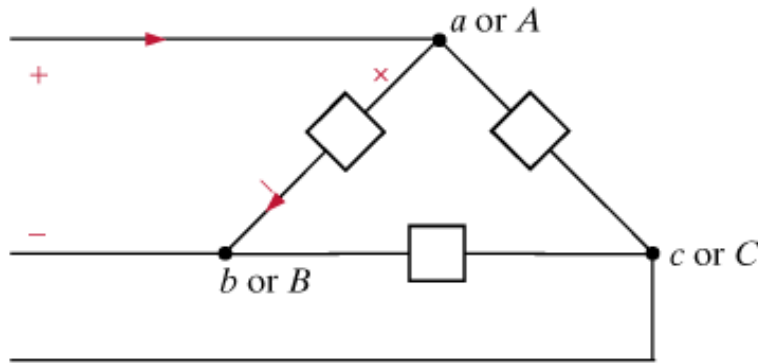EXAMPLE

continued

If the line impedances are $Z_{line} = 0.05 + j0.02\Omega$
determine line voltages and power factor at the source



$$S_{load\ total} = 43.6 + j24.8\text{kVA} = 50.160 \angle 29.63^\circ\text{kVA}$$

$$S_{source\ total} = 46.508 + j25.963 = 53.264 \angle 29.17^\circ\text{kVA}$$

$$\begin{cases} |S_{total}| = \sqrt{3} |V_{line}| \times |I_{line}| \\ \theta_f = 29.17^\circ \end{cases}$$

$$|I_{line}| = 139.23(\text{A})_{rms}$$


$$S_{line} = 3 \times (Z_{line} I_{line}) I_{line}^* = 3 \times Z_{line} |I_{line}|^2$$

$$S_{line} = 2908 + j1163(\text{VA})$$

$$V_{line} = \frac{53,264}{\sqrt{3} \times 139.13} = 220.87(\text{V})_{rms}$$

$$pf = \cos \theta_f = \cos(29.17^\circ) = 0.873\text{lagging}$$

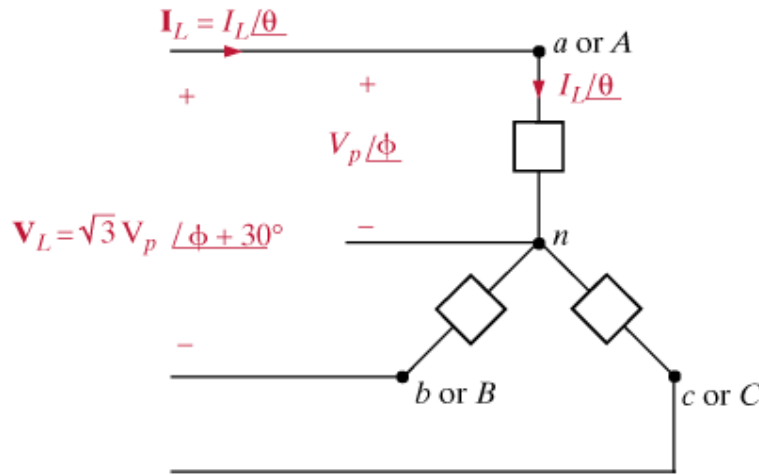Example: A Y-Y balanced three-phase circuit has a line voltage of 208-Vrms. The total real power absorbed by the load is 12kW at pf=0.8 lagging. Determine the per-phase impedance of the load



(a)

$$\Rightarrow |V_{phase}| = \frac{208}{\sqrt{3}} = 120(V)_{rms}$$

$$S_{total} = 3V_{phase} \times \left(\frac{V_{phase}}{Z_{phase}} \right)^* = 3 \times \frac{|V_{phase}|^2}{Z_{phase}^*}$$

$$pf = 0.8 = \cos \theta_f \Rightarrow \theta_f = 36.87^\circ$$

$$|S_{total}| = \frac{P_{total}}{pf} = 15kVA$$

$$|V_{\Delta}| = \sqrt{3} |V_{phase}|$$

$$\theta_{\Delta} = \theta_{phase} + 30^\circ$$

Line - phase voltage relationship

$$S_{Total} = 3 \times V_{phase} \times I_{phase}^*$$

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$|Z_{phase}| = \frac{3 \times |V_{phase}|^2}{|S_{total}|} = 2.88\Omega$$

$$Z_{pahse} = 2.88 \angle 36.87^\circ \Omega$$

Example: A 480-V rms line feeds two balanced 3-phase loads. The loads are rated
Load 1: 5kVA at 0.8 pf lagging Load 2: 10kVA at 0.9 pf lagging.

Determine the magnitude of the line current from the 408-V rms source

$$|S_1| = 5kVA = \frac{P}{0.8} \Rightarrow P_1 = 4kW$$

$$Q_1 = \sqrt{|S_1|^2 - P_1^2} = 3.0kVA$$

$$pf \text{ lagging} \Rightarrow S_1 = 4 + j3kVA$$

$$|S_2| = 10kVA = \frac{P}{0.9} \Rightarrow P = 9kW$$

$$Q_2 = \sqrt{|S_2|^2 - P_2^2} = 4.36kVA$$

$$S_2 = 9 + j4.36kVA$$

$$S_{total} = 13 + j7.36kVA$$

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$S_{total} = S_1 + S_2$$


$$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f$$

$$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$$

$$|S_{total}| = \sqrt{3} |V_{line}| |I_{line}|$$

$$|I_{lineq}| = \frac{|S_{total}|}{\sqrt{3} \times |V_{line}|} = \frac{14,939}{706.68} = 21.14(A)_{rms}$$

POWER FACTOR CORRECTION

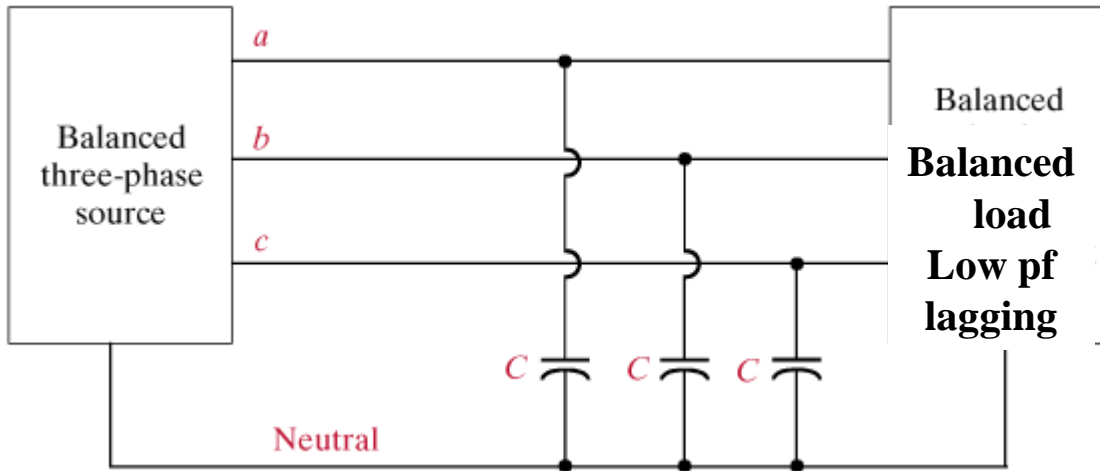

Similar to single phase case.
Use capacitors to increase the power factor

Keep clear about total/phase power, line/phase voltages

$$\left. \begin{matrix} S_{old} \\ pf_{old} \end{matrix} \right\} \rightarrow Q_{old}$$

$$\Delta Q = Q_{new} - Q_{old}$$

Reactive Power to be added

$$Q_{Cnphase} = \omega C V_{nh}^2$$

$$\left. \begin{matrix} P_{old} \\ pf_{new} \end{matrix} \right\} \rightarrow Q_{new}$$

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$pf = \cos \theta_f \Rightarrow \sin \theta_f = \sqrt{1 - pf^2}$$


$$\tan \theta_f = \frac{pf}{\sqrt{1 - pf^2}} \quad Q = P \tan \theta_f$$

$$Q_{\text{per capacitor}} = -\omega C V^2$$

The voltage depends on how the capacitors are connected

$$\text{lagging} \Rightarrow Q > 0$$

EXAMPLE:

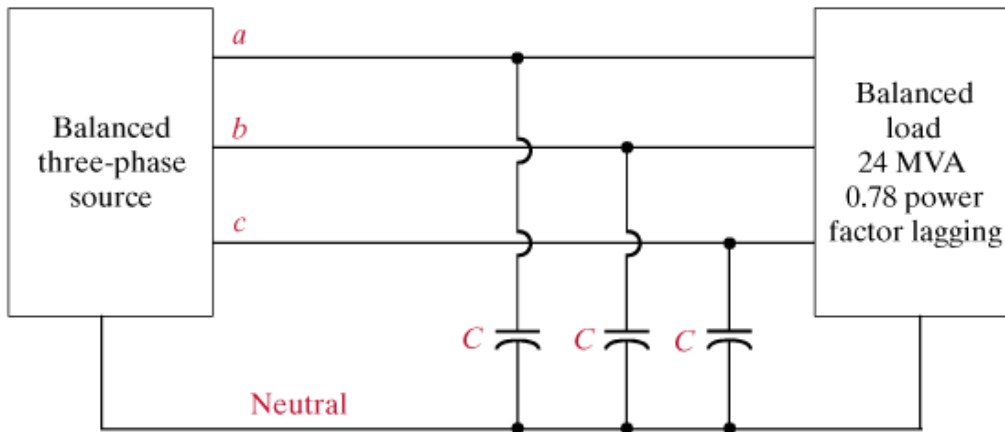

$$f=60 \text{ Hz}, V_{line}=34.5 \text{ kV}_{\text{rms}}$$

Required $pf=0.94$ lagging.

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$Q = P \tan \theta_f$$

$$\tan \theta_f = \frac{pf}{\sqrt{1 - pf^2}}$$

$$\text{lagging} \Rightarrow Q_{old} > 0$$

$$pf = \cos \theta_f \Rightarrow \sin \theta_f = \sqrt{1 - pf^2} = 0.626$$

$$|Q_{old}| = 15.02 \text{ MVA}$$

$$P_{old} = 18.72 \text{ MW}$$

$$\left. \begin{array}{l} P_{old} = 18.72 \text{ MW} \\ pf_{new} = 0.90 \text{ lagging} \end{array} \right\} \Rightarrow Q_{new} = -9.067 \text{ MVA}$$

$$\Delta Q = 9.067 - 15.02 = -5.953 \text{ MVA}$$

$$Q_{\text{per capacitor}} = -1.984 \text{ MVA}$$

$$Y\text{-connection} \Rightarrow V_{\text{capacitor}} = \frac{34.5}{\sqrt{3}} \text{ kV}_{\text{rms}}$$

$$Q_{\text{Cphase}} = \omega C V_{ph}^2$$

$$-1.984 \times 10^6 = -2\pi \times 60 \times C \times \left(\frac{34.5 \times 10^3}{\sqrt{3}} \right)^2$$

$$C = 13.26 \mu\text{F}$$